
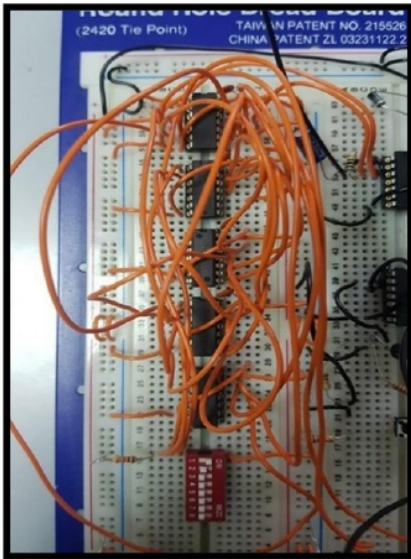



BREADBOARD CIRCUITS

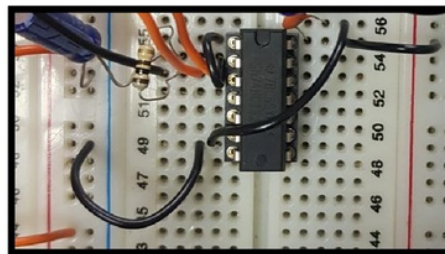


State Machine circuit.



Clocking circuit.

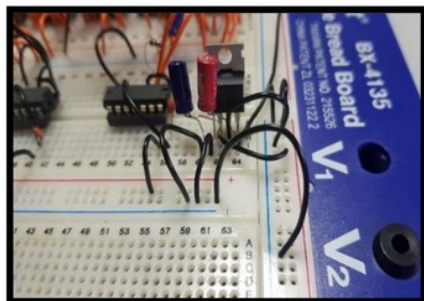


Power Supply Circuit.

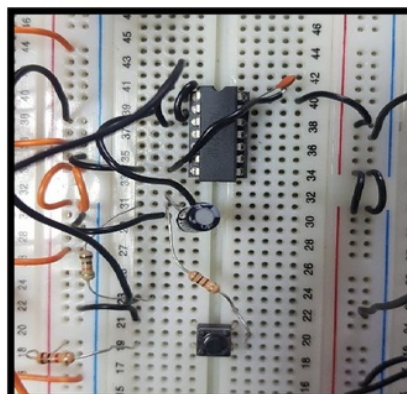


De-bouncing Circuit.

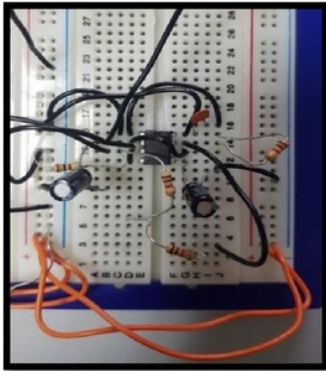Deliverable 6: Final design report - Proreverse Enterprise – Team D



555 Timer circuit.

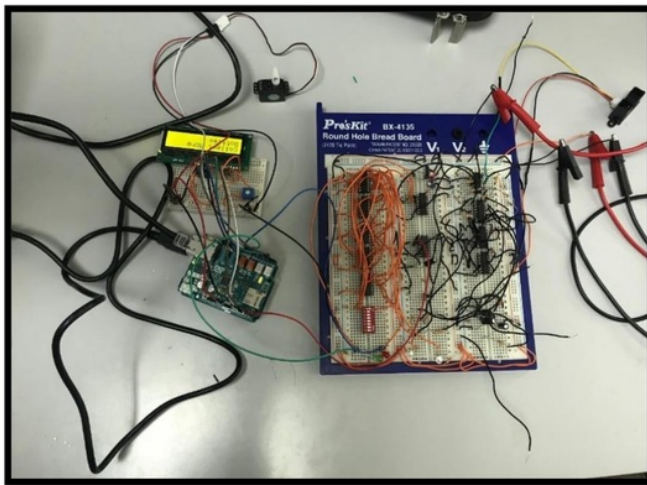

Integrated circuits on breadboard.