

Questo sito fa uso di cookies.

Cliccando un qualunque link accetti al loro utilizzo.

OK No

Varesano.net

[Home](#) [About](#) [Topics](#) [Projects](#) [Socialize](#) [Contact](#)[Home](#) » [Blogs](#) » [fabio's blog](#)


Diodes, Transistors and Optocouplers: what they are, some theory and simple usages examples with Arduino

Last updated on Sun, 2012-10-07 11:08. Originally submitted by fabio on 2010-07-22 10:39.

In this post I'll experience with three kind of components available in the [Arduino Base Workshop KIT](#): diodes (model 1n4007), transistors (models BC547 Transistor and MOS Irf540) and optocouplers (model 4N35). I'll briefly describe them and we'll see some simple examples of circuits built upon an Arduino Duemilanove board which make use of them.

Diodes: driving current only in one way

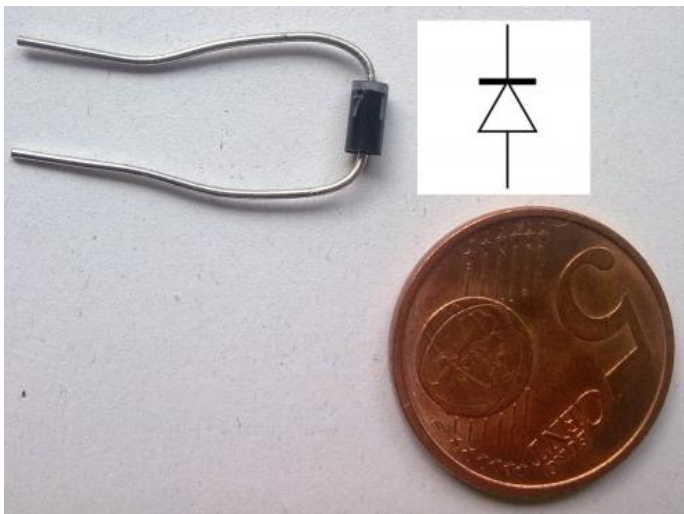Well, the title says it all. A **diode** is a two terminals electronic component that conducts electric current only in one direction.



The most common function of a diode is to allow an electric current to **pass** in one direction (called the diode's *forward* direction) while **blocking** current in the opposite direction (the *reverse* direction). Thus, the diode can be thought of as an electronic version of a check valve. This unidirectional behavior is called rectification, and is used to convert alternating current to direct current, and to extract modulation from radio signals in radio receivers.

A simple Arduino based circuit using a diode

We can build this simple circuit to show how diodes works:


Stickers




Popular content

All time:

- [Installing Flash Player Plugin on Firefox without having Administrator Access or Permissions](#)
- [FreeIMU: an Open Hardware Framework for Orientation and Motion Sensing](#)
- [Disable related videos on a embedded Youtube player](#)
- [h264 videos on Flash: cool example](#)
- [Serial RS232 connections in Python](#)
- [My first 6 DOF IMU Sensors Fusion Implementation: ADXL345, ITG3200, Arduino and Processing](#)
- [Serial communication with Arduino and Processing: simple examples and an Arduino based gamepad interfacing with Processing](#)
- [Multiple forums for Organic Groups: my patch committed](#)
- [An homebrew DIY breakout board for the ITG3200 gyroscope: tested with Arduino and Processing](#)
- [Digital Input/Output on custom CC430 board](#)

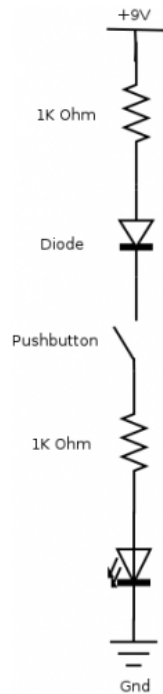

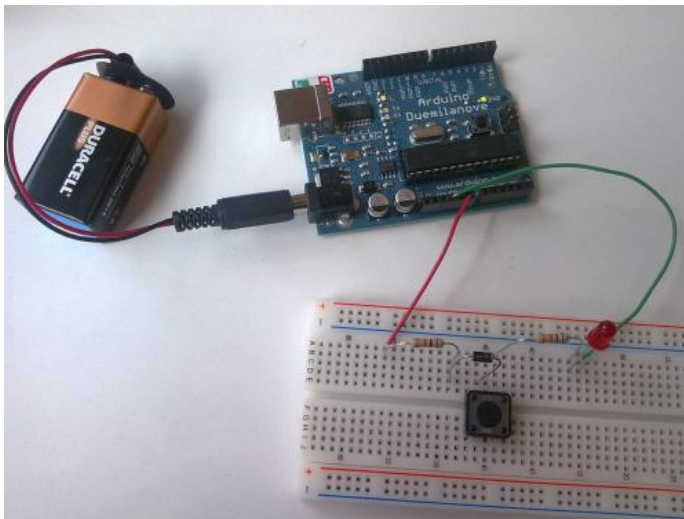Once assembled on the Arduino board, the circuit will look like:




What does this circuit do? Well, nothing complex or useful actually. But we can understand how diodes work with it. If we plug the diode as seen on the pictures above when we'll push the button the LED will turn on. Cool, uh?

Instead, if we revert the diode so that current now flows in the opposite direction, we'll see that the LED won't turn on when we press the button. This confirms the behaviour of a diode: it lets the current flow if it's passing in its forward direction while it blocks when it passes in the opposite direction. You can see a demo in the video below.

Recent comments

- [prom read address 0](#)
1 year 32 weeks ago
- [Sorry if this sounds stupid.](#)
1 year 32 weeks ago
- [Starting with MS5611](#)
1 year 32 weeks ago
- [problems in calibration mag data](#)
1 year 33 weeks ago
- [Code to test IMU \(The cube form\)](#)
1 year 37 weeks ago
- [error while compiling](#)
1 year 39 weeks ago
- [Re: Hi I have read that in](#)
1 year 39 weeks ago
- [wonderful!](#)
1 year 40 weeks ago
- [You may want to test if the](#)
1 year 41 weeks ago
- [Hello. Doing this in the](#)
1 year 41 weeks ago

Advertising

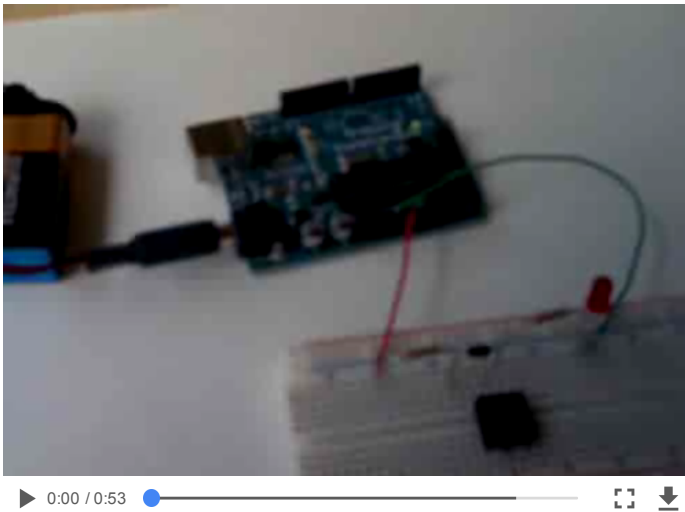


Transistors

A **transistor** is a semiconductor device which can be used to amplify or switch electronic signals. In the simple Arduino based circuits transistors are usually used as switch for electronic signals.

Transistors usually have 3 connectors called *collector*, *base* and *emitter*. In normal state the collector and emitter are disconnected but, when a current is applied to the base connector, the transistor change its state and the collector and emitter get connected thus current can flows between them.

This behaviour make the transistor the perfect component for interface two different circuits operating at different voltages. For example one circuit could be the one powered by Arduino: small current and low voltages. The other circuit could be the one operating a DC motor which needs a lot of voltage and current. Connecting the two circuits could be painful but with the transistor we could drive the second circuit by changing the state of the transistor trough the first circuit connected to the Arduino. Cool stuff.

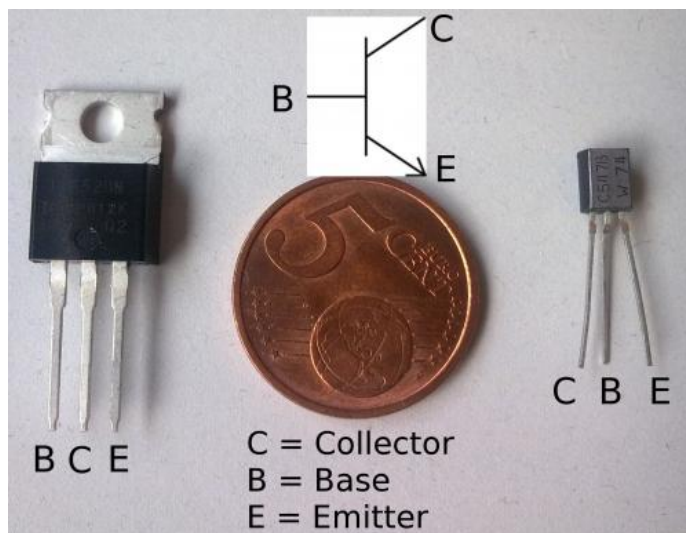


The Arduino Base Workshop KIT comes with two types of transistors displayed in the picture above: a MOS Irf540 (left) and a BC547 (right). They differs from the building technique which results in different specifics. For all the details have a look at the detailed specifics linked above but they mostly work the same way: they only differ in the amount of current they are capable of deliver. For bigger currents (eg powering motors) the MOS Irf540 will be perfect. The BC547 is not capable of delivering lot of current so use it with care.


A simple Arduino based circuit using transistors

We will use a transistor controlled by the Arduino board to act as a switch on an external circuit.

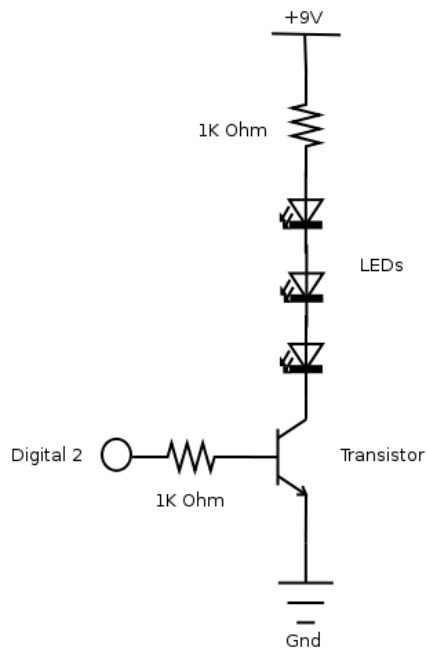The transistor base will be connected to an Arduino output pin. This is the circuit:



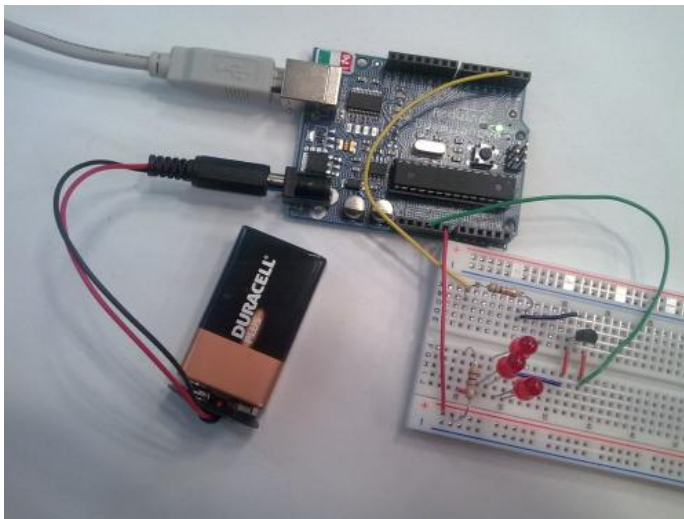
Once plugged into the Arduino board it will look like:



Note that the circuit coming from Vin (9V) is actually completely separated from the one coming from the Arduino board. They are two independent circuit. Only the transistor let them interact.

We will now use the [Hello World program](#) with a simple modification: we will use pin 2 as output (in the helloworld program we used pin 13). To get the code refer to the [Hello World blog post](#).

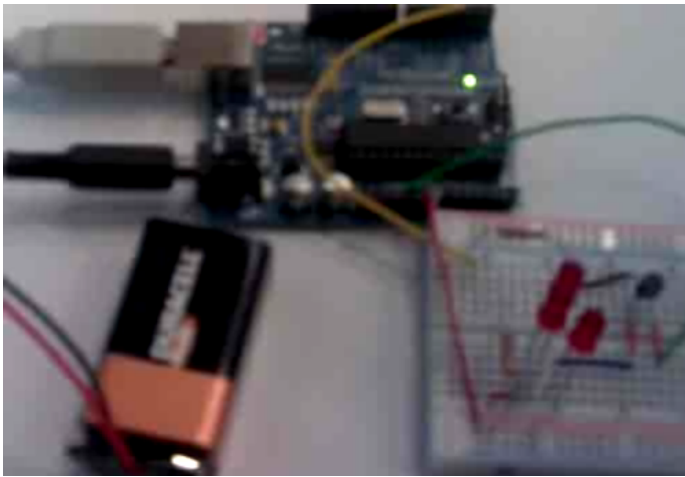What does the circuit we created do? Well, let's see in the video below:




As you can see each time the output on pin 2 is HIGH our transistor will get a voltage on its base connector resulting in the collector and the emitter getting connected. Current coming from the +9V source can then flow down through the resistor and the three series LEDs lighting them on.

A similar result could have been achieved using the MOS Irf540 transistor.

UPDATE 2012-10-07: Improvement

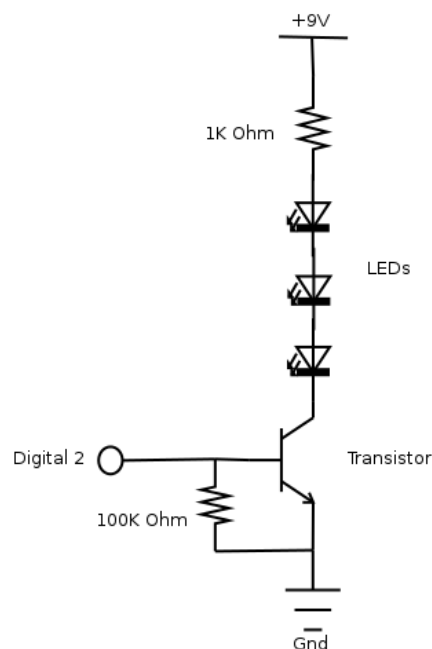
The circuit above can be improved by using this circuit:



This is preferable against the one explained before because it won't float when the microcontroller is shut off or when it is not actively drive the pins. Basically, the circuit explained above only works reliably when the microcontroller actively drives the pin high or low. When it is not doing so, the transistor may float randomly and close/open the circuit. The fixed circuit in this section, by using a pull-down resistor doesn't show this effect and works reliably.

Optocouplers

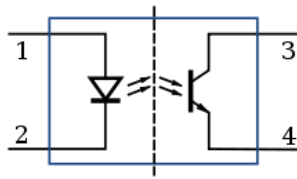
An **optocoupler**, also called *opto-isolator*, *optical isolator*, *optical coupling device*, *photocoupler*, or *photoMOS*, is an electronic device that usually contains both an infrared *light-emitting diode* (LED) and a *photodetector* and use them to transfer an electronic signal between element of circuits maintaining them electrically isolated.




When a voltage is applied to the LED, the LED lights and illuminate the photodetector which produces an output current on the photodetector: basically this means that now the photodetector circuit is now connected and current can flow in it.

4N35 Optocoupler DIL-6 package

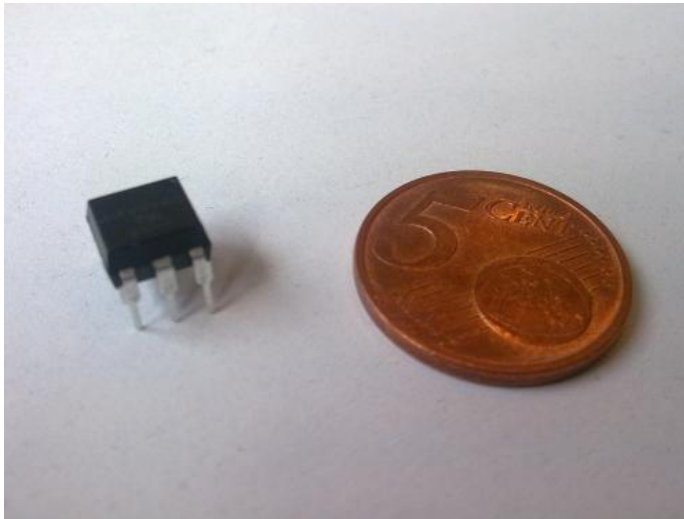The Arduino Base Workshop kit comes with two *4N35 Optocouplers* packaged as a *DIL-6 package*.



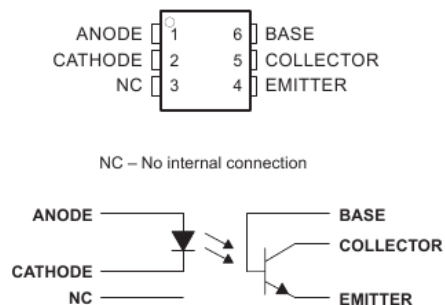This little component has 6 legs each of them having a different usage. It can be easily understood while looking at the following picture from the 4N35 datasheet which shows us the inside schematics of the 4N35:




So, we have leg 1 and 2 near the printed dot on the chip (that's visible on it if we look carefully) that acts respectively as anode and cathode. Leg 3 isn't connected to anything: it's just useless. We then have leg 4, 5, 6 respectively emitter, collector and base.


We already know these terms from the transistor introduction above. They do exactly the same of the legs of a transistor. The difference here is that we can leave the base unconnected and just use the LED (legs 1 and 2) to connect the collector and the base.

An Arduino based circuit using an 4N35 Optocoupler

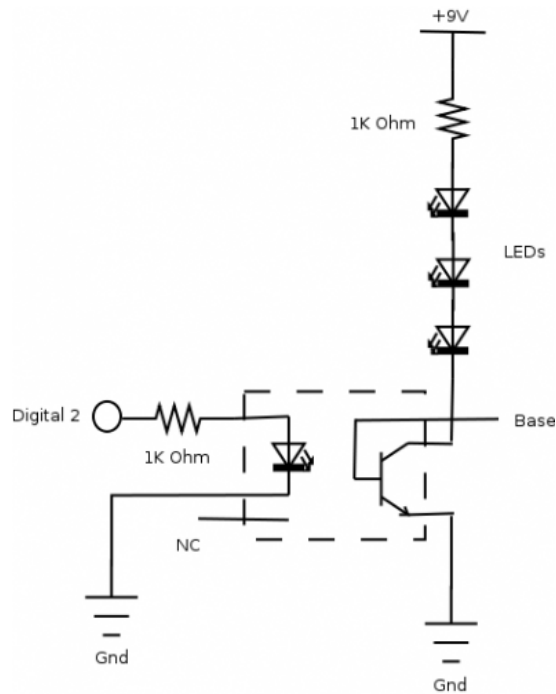Now that we know the theory behind optocouplers and that we know how to connect our 4N35 Optocoupler it's now time to create a simple circuit with it. Here it is:



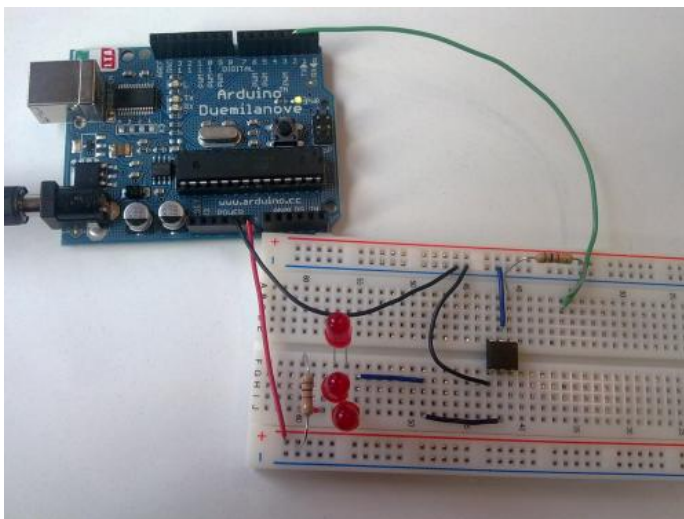The circuit above once created using the Arduino board will look like:



We can use the same program used for the transistor example above. This is the result:



0:00 / 0:28

So, it basically do the same of the transistor example above but this time we are using an optocoupler. Not bad, uh?

Conclusions

Now, I know how to use three new electronic components: diodes, transistors and optocouplers. The simple circuits I built will be used as base for more complex stuff. I'm pretty sure these components will be pretty useful when I'll build more complex stuff. Looking forward to it!

References

[Diode](#) on [Wikipedia](#)
[Transistor](#) on [Wikipedia](#)
[BC547 Nodatasheet](#) by [Daniel Soltis](#)
[BC547 Official Datasheet](#)
[Arduino Hello World](#) on [this blog](#)
[Opto-isolator](#) on [Wikipedia](#)
[Electus Distribution Reference Data Sheet: OPTOCOUP.PDF](#)
[4N35, 4N36, 4N37 OPTOCOUPPLERS Data sheet](#)

Attachment	Size
transistors_1.jpg	574.38 KB

[Login](#) to post comments 90161 reads

Posted in: [arduino](#) [diode](#) [optocoupler](#) [transistor](#)

Confused

Submitted by Hubschrauber (not verified) on Sun, 2015-05-10 07:39.

The section about the 4n35 says: "The difference here is that we can leave the base unconnected and just use the LED (legs 1 and 2) to connect the collector and the base." Doesn't the internal LED actually cause the collector and the emitter to connect?

[Login](#) to post comments

Hi I have read that in

Submitted by j (not verified) on Wed, 2014-06-04 00:09.

Hi

I have read that in nuclear industries, optical isolators should be used for acheiving independence (i.e. isolation so that if one part gets damaged other part is not affected) instead of resistors. Could you please explain to me why?

[Login](#) to post comments

Re: Hi I have read that in

Submitted by Anonymous (not verified) on Tue, 2015-06-09 17:36.

Hi J,

So the difference is that a resistor isn't directional and will therefore allow current to flow from either side. An optical isolator on the other hand works similar to a diode in that it only lets unidirectional transmission. This is good when you don't want a component further along in the system to affect previous components.

I suppose in this case, an optical isolator would prevent surges and other damaging events from passing to the parts that work well, while a resistor would let it pass right on through.

[Login](#) to post comments

Thanks a lot

Submitted by N. Blondel (not verified) on Mon, 2013-10-14 23:33.

Thanks for these precisions, it helped me to understand a lot too!

I studied electronics before going to IT embedded systems and I wanted to get back to electronic as a hobby. So I bought this base workshop kit with an Arduino Uno; but my memory of these components is a bit old and I was even wondering what was some of the components of the kit...

Whatever great article, thanks for sharing!

[Login](#) to post comments

Good article

Submitted by AN (not verified) on Sun, 2012-10-07 02:37.

Thank you for the good article!

Reading, I have noticed that looks like the terminals on the picture of transistors (specifically at left of the 5-cent coin) which is TO-220 packaging one are named incorrect: CBE should be read as BCE according to the specs

<http://www.datasheetcatalog.org/datasheet/stmicroelectronics/9387.pdf>

[Login](#) to post comments

That is right. Thanks for

Submitted by fabio on Sun, 2012-10-07 11:09.

That is right. Thanks for noticing and posting a comment. I have fixed the image and also added an improved circuit which should be better.

[Login](#) to post comments

Which to choose ?

Submitted by [Pierre-Alain Dorange](#) (not verified) on Tue, 2012-07-31 21:19.

Thanks for this simple explanation, very useful for a beginner like me.

But i'm a bit perplex when i'll have to choose between the last 2 techniques (transistor, opto and relay could be added)... I do not understand what is the difference and when it's better to choose a transistor, an opto or a relay.

I saw schematics using both relay and transistor... Probably related to power necessary.

[Login](#) to post comments

thank you very much for time

Submitted by anthony treacy (not verified) on Sat, 2011-03-26 14:09.

thank you very much for time to submit this web page. very helpfull. it helped me alot.

thank you again ;-)

[Login](#) to post comments

You are welcome. Thanks for

Submitted by fabio on Sat, 2011-03-26 14:19.

You are welcome. Thanks for stopping by and for saying thanks. ;-)

[Login](#) to post comments

Copyright © 2007-2013 Fabio Varesano - [Some rights reserved](#).

[Privacy Policy](#)