

TECHNO

GUMBO

At A Glance

Main

Projects

Tutorials

Resume

Blog

Poll

If I made a video series showing how to incorporate optocouplers into MIDI, use them with PIC, ATMEL, and ARM microcontrollers, and a few other applications, would you pay \$5 for it?

☐ Yes

☐ Depends on the content quality


☐ No

Vote

Learning to Use an Optocoupler or Optoisolator

An optocoupler or optoisolator is a cool little device that allows you to completely separate sections of an electrical circuit. From what I understand, the MIDI protocol requires the use of optocouplers in all devices. I want to use an optocoupler for separating a circuit powered by USB (5V) from one powered by a 7.2V RC Car battery. The idea behind this is that I want to protect the USB based circuit(and my computer) from the large amperages, inductance, higher voltages and other things going on in the RC Car side of the circuit, but still want to be able to control it using a USB device. I am writing this after successfully using a Fairchild 4N25 Optocoupler to deliver pulse width modulation from a USB based circuit to the 7.2V circuit in order to control a servo.

Functional Block Diagram

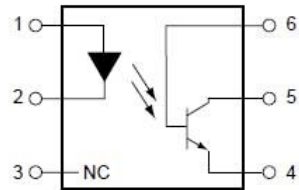

PIN 1. ANODE  
2. CATHODE  
3. NO CONNECTION  
4. EMITTER  
5. COLLECTOR  
6. BASE

RSS


Related Links

[MIDI Gameboy thing using 4N25](#)


[Great Optocoupler tutorial on speed control](#)

The following are a series of descriptions of ideas that I have learned while working with an optocoupler over the last month.

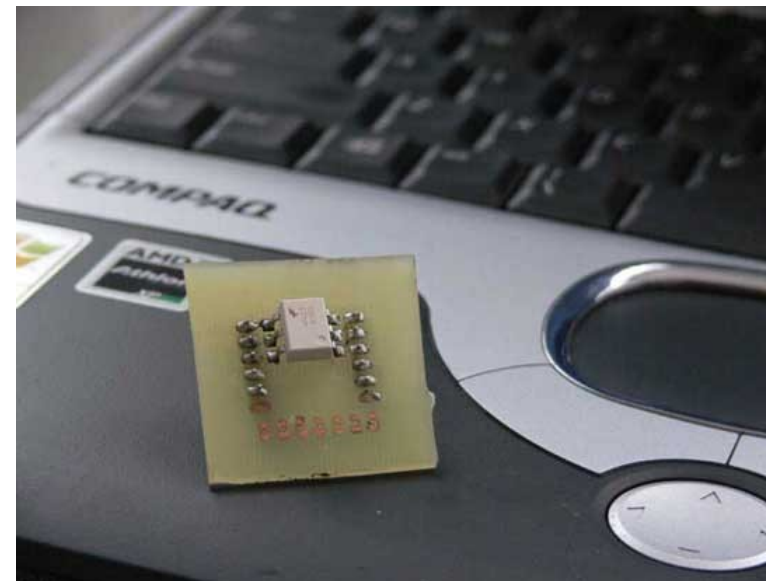1. Dont waste your time making or purchasing a breakout board for a package size that is large enough to directly solder wires to.



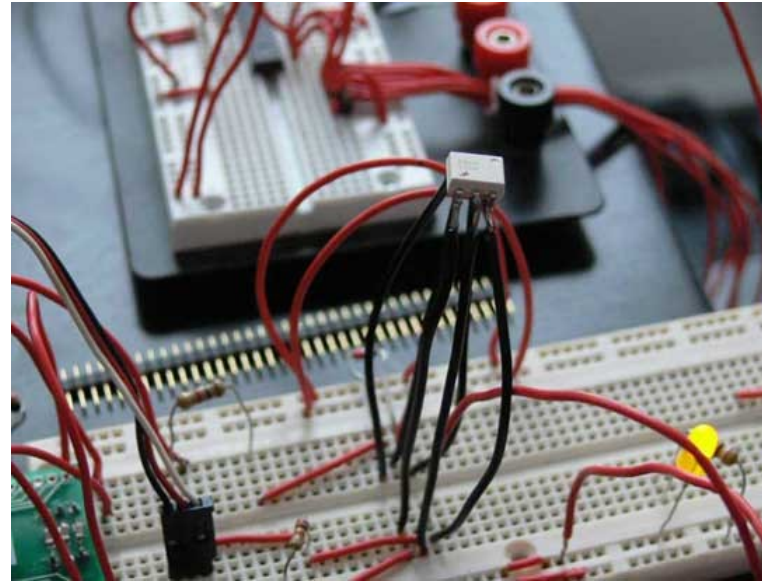The leads are far enough apart. This didnt need a breakout board made for it.



*This is the way I should have done it in the first place*

The Fairchild 4N25SM has large enough pin spacing despite being surface mount, that you can easily solder wires directly to the pins for experimentation. I made a breakout board for this part and after a week found out the that optocoupler was not performing as it should have. I think I got the pins on the optocoupler too hot while soldering them to the breakout board.

## 2. I'm not sure about other optocouplers, but the 4N25 works on the major principal of sinking current.

Before actually working with the part, I did not understand that you have to configure the optocoupler in such a way that when the signal you are trying to reproduce goes low, the optocoupler should turn ON. This is echoed in [Paul Hill's Speed Control Examples Using the 4N25](#) as well as the test diagram that is shown in the Fairchild datasheet:

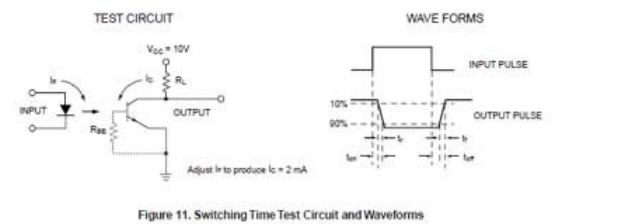


Figure 11. Switching Time Test Circuit and Waveforms

*See how the output is the inverse of the input according to the diagram on the right?*

In all of the configurations of the 4N25 I have always seen output tied in parallel to the transistor sides collector (pin 5). The transistor side of the 4N25 (pin 4, 5, and 6) reproduces a signal by always being high except for when the LED gets turned on. When the LED in the 4N25 turns on, it causes the input output to go LOW because there is a direct path opened to ground.

## 3. Pin 6 (the base of the transistor) is used to tweak the sensitivity of the optocoupler.


When doing research for working with the 4N25 I always saw diagrams of the base not being connected at all, or being connected to ground by a very large resistor in the 100k and above range. Initially I did not connect pin 6, the base to anything. However, after sending a pulse width modulation signal through the optocoupler to control a servo, I noticed the servo would not hold its position without rapidly jerking a small amount back and forth. I tested the output of the optocoupler with two servos and noticed the same behavior.

I then hooked a large range potentiometer between the base of the transistor (pin 6) and ground. As I ran the resistance on the base of the transistor from zero to around 80K ohms, I could visibly see the jerking motion on the servo increase and decrease to smooth operation.
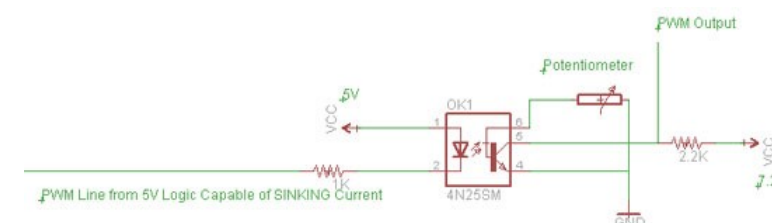
## 4. A simple test setup for an optocoupler can be constructed using a single power source, LED, resistors, and a pushbutton switch.

The diagram to the left is what I used to test the 4N25; You can click it for a higher resolution schematic. When I supplied power to the LED side of the optocoupler (pins 1, 2, 3), I would see the dimly lit LED turn OFF. The LED would turn back on again when I removed power from the LED side of the optocoupler.

The final diagram of the configuration I am currently using to smoothly control a servo as of writing this can be seen below:



If you found this helpful, please provide some feedback by quickly voting in the poll at the top left of the page under the menu. Thanks!

### Comments

john

March 7, 2016 07:53 am




Optocouplers can be used as either input or output devices. They can have additional functions such as intensification of a signal or Schmitt triggering (the output of a Schmitt trigger is either 0 or 1 - it changes slow rising and falling waveforms into definite low or high values). Optocouplers come as a single unit or in groups of two or more in one casing.

Read more: <http://romux.com/tutorials/pic-tutorial/optocouplers#ixzz42DjrPqb7>

Dr Manaf

March 5, 2016 04:23 am

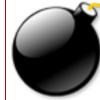

How to eliminate the effect of TV remote control from from IR photocoupler?

Aishwarya

February 17, 2016 05:47 am



Can you tell me where the base of the optocoupler connected?Also I wanna connect a source/sink to it.Does that go to the collector?

Tyeth

January 30, 2016 8:29 pm



Thanks, cleared up a similar situation with a high voltage opto-isolator from Maplin.co.uk

Abid

October 18, 2015 06:55 am



I want to connect optoisolator in a protection circuit where if i give 60v input from solar which will be scaled down to 7V but this 7V cant be constant since my input is changing, so i need it to change correspondingly with the input. is that possible using this optoisolator? please help me understand this

Alibaba

May 5, 2015 10:39 pm



Thanks :)

Sher

March 18, 2015 2:55 pm



Dear, Thx for the Pot. but i my output is highly disturbed at the operating frequency of 100 kHz..

sirisha

March 17, 2015 05:52 am



how to connect this ic (optocoupler) to a simple calculator?

from BE

March 7, 2015 11:01 pm



Your description of what to do with the 100k resistor, helped me out of problems. Strange enough, on my breadboard try out I had to "remove" this R to make it work. Anyway thanks man.

Suman

May 30, 2013 10:46 pm

Shrestha



Hi guys!  
Please help me to use mct2e

vips

May 11, 2013 09:02 am



i dont think it is working.... i have worst experience abt the ckt

Charles

April 29, 2013 3:33 pm



Hi abhishek,

In this example the pulse is being generated on the cathode (2). The pulse is created by sinking the cathode to ground through a microcontroller.

It has been a while but I think the output is coming from the collector.

The whole thing is confusing to look at because both sides are creating an oscillation by sinking current. On the right side, the PWM output happens because the path on pin 4 opens up and current flows to ground when the LED is lit on the left side.

abhishek

April 29, 2013 1:29 pm



hi

how am i supposed to connect a pulse to mct2e and from which i have to take the output .i mean to which pins i have to connect .

pins

1-anode

2-cathode

3-no internal connection

4-emitter

5-base

6-collector

so to which pin i have to give pulse nd from which i have to take the output

solderman  
39

March 27, 2013 06:03 am



Can an opto isolator be used with a pic 12F683 output (pin5 ! The voltage at the pin is  $> < 2.5v$ . I want it to switch ON a 2n3904 transistor.

Charles

March 9, 2013 1:41 pm



Adopting to finite voltages like .2v and 1.6v will depend on the datasheet of your specific optocoupler and other external components you use to manipulate those values.

Think of the optocoupler like a transistor and an LED. All LED's have different threshold voltages to turn them on and off completely while not damaging them.


Likewise, all transistors have certain threshold conditions depending on their types and models to activate or deactivate them.

In all cases, these conditions can be manipulated by using external components if the optocoupler doesn't fit the design exactly.

As usual there is no straightforward yes or no answer to your question. Best advice I have is to read the datasheet, do calculations more than once, then test.

sri

March 3, 2013 02:17 am

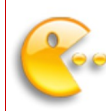

will optocoupler sense the difference between .2V n 1.6V .. should be off @ .2V n work by 1.6v

ching


February 26, 2013 11:23 pm



niceee

Emerson

September 27, 2012 10:10 am

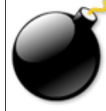

Thank you, boy!!! It helps a lot!

Legion

February 28, 2012 00:40 am



Have you found one that can be used to pass analog signals? I want to make a protection circuit for my signal generator.

Charles

February 13, 2012 10:24 am



Hi saadhana,

An opto isolator is just another name for an optocoupler.


These devices work very similar to a transistor in a circuit except they provide complete electrical isolation between the two sides of the circuit you implement them in.

Common use cases for them are providing signaling across different voltages, or in interface bus designs such as MIDI where engineers wish to protect the circuit

and external devices from potential outside damage.

**saadhana**


February 13, 2012 02:39 am

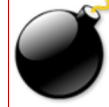

what is meant by opto isolator? how it works in circuit?  
can u give me any example?....

**Charles**


January 19, 2011 8:11 pm

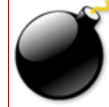

Arjoon,  
I'm not sure. It would depend on several factors concerning your design.

**Arjoon**


January 19, 2011 4:11 pm

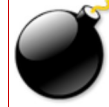

if i use an astable oscillator. what will be the maximum operating frequency

**dilan**

September 1, 2010 10:00 am

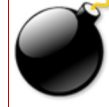

hey guy plz help me to use 4N32 opto  
i need it immediatly plzzz guyzzzzz

**Charles**


June 13, 2010 1:01 pm



Muslem,  
If you don't have enough amperage/voltage available to actually turn on the LED inside the optocoupler, you may have issues.  
  
The first 4N25 that I fooled with was broken. You should be able to tell my doing continuity tests between the different legs of the transistor.  
  
Is it also possible that your switching speed for your application is too high to notice much of a change?

**muslem**

June 13, 2010 02:07 am

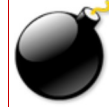

Hi,  
In the same optocoupler i give input pulse but I do n't get any output. wheter o or 1. whats the problm? Can any one response me ?  
Thanks to all

**Charles**


August 8, 2009 8:11 pm



Hi Joi. I don't remember exactly what the resistance value of the potentiometer was. I know the pot that I used has a range up to 70,000Ohms.

**Joi**


August 7, 2009 9:55 pm

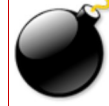

Hi! I'm doing exactly the same thing. My servo also has this jitter. Do you know approx. how big your bias resistor is in ohms? I'd like to decrease board size by just having a fixed resistor instead of a pot.. :) Thanks in advance, Joi

**Charles**


July 17, 2009 10:28 pm

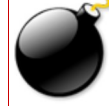

Thanks Albie. Your exactly right. I crossed out what I had and changed it to output.

**Albie**

July 17, 2009 06:38 am

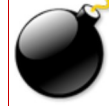

In the last line of paragraph 2, I think you might mean "output" instead of "input". The output would go low when it turns on causing the transistor to sink current.

**Post  
Message**

