

 

 
# The Ideal Diode


- Most Fundamental non-linear element
- Two terminal device



In Cutoff or Simply 'Off'

 


Is turned on or Simply 'On'

 

**Figure 3.1** The ideal diode: (a) diode circuit symbol; (b)  $i$ - $v$  characteristic; (c) equivalent circuit in the reverse direction; (d) equivalent circuit in the forward direction. Source: Page 140 Sedra and Smith 5<sup>th</sup> Edition

# The Ideal Diode


Example:

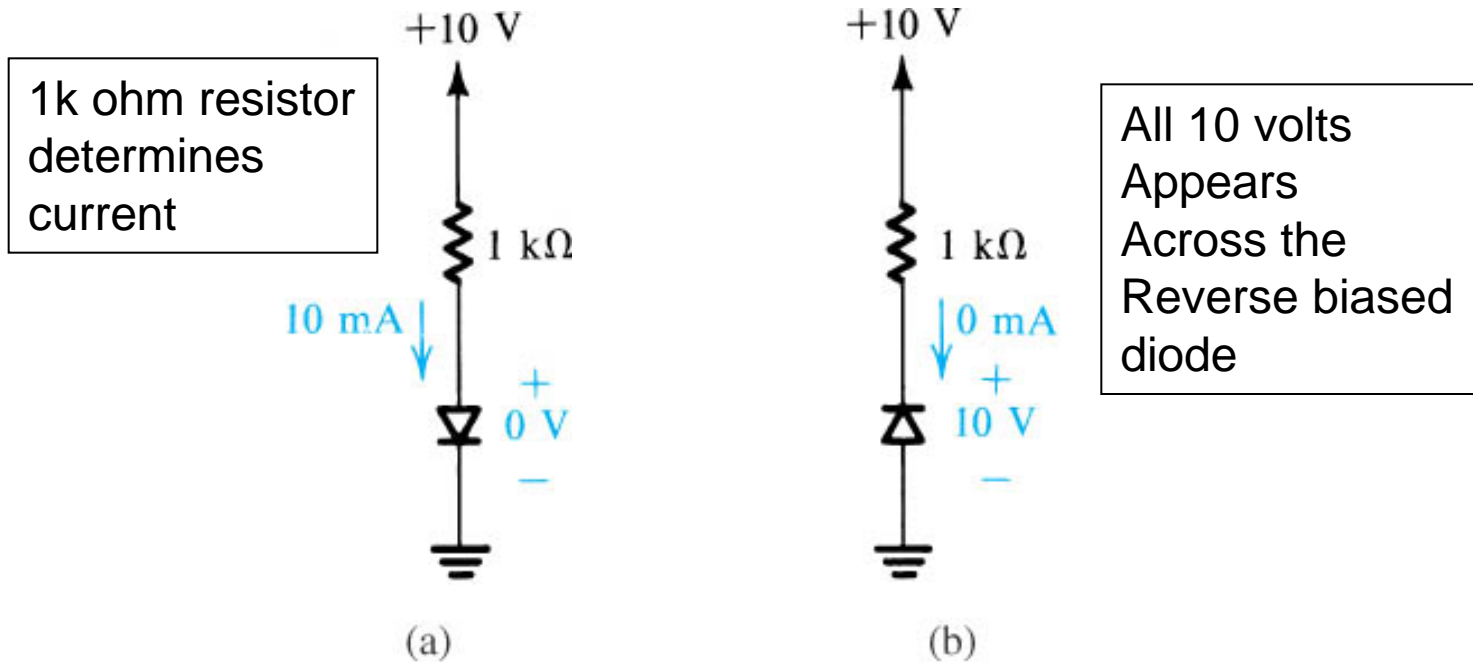

**Figure 3.2** The two modes of operation of ideal diodes and the use of an external circuit to limit the forward current (a) and the reverse voltage (b). Source: Page 141 Sedra and Smith 5th Edition
 
# The Ideal Diode


- Ideal diode current versus voltage (i-v) curve is highly nonlinear
- But, because it consists of two straight lines, albeit orthogonal (ie operating lines are 90 degrees to each other), it can be said to be **piece-wise linear**



- **Advantage:** If we have a circuit element which exhibits a piece-wise or near piece-wise linear operation and we choose to operate this circuit in the piece-wise linear location / region (eg small signal equivalent circuit models we will see later) then we can treat the circuit as a linear circuit in our analysis – provided we do not allow our design to swing across breakpoints where the circuit switches from one segment of linear operation to another!
- Sometimes a circuit may not be piece-wise linear, like a diode, but if small enough signals are used it can be close enough for analysis.

# Circuits with Ideal Diodes

## Diode Logic Gates

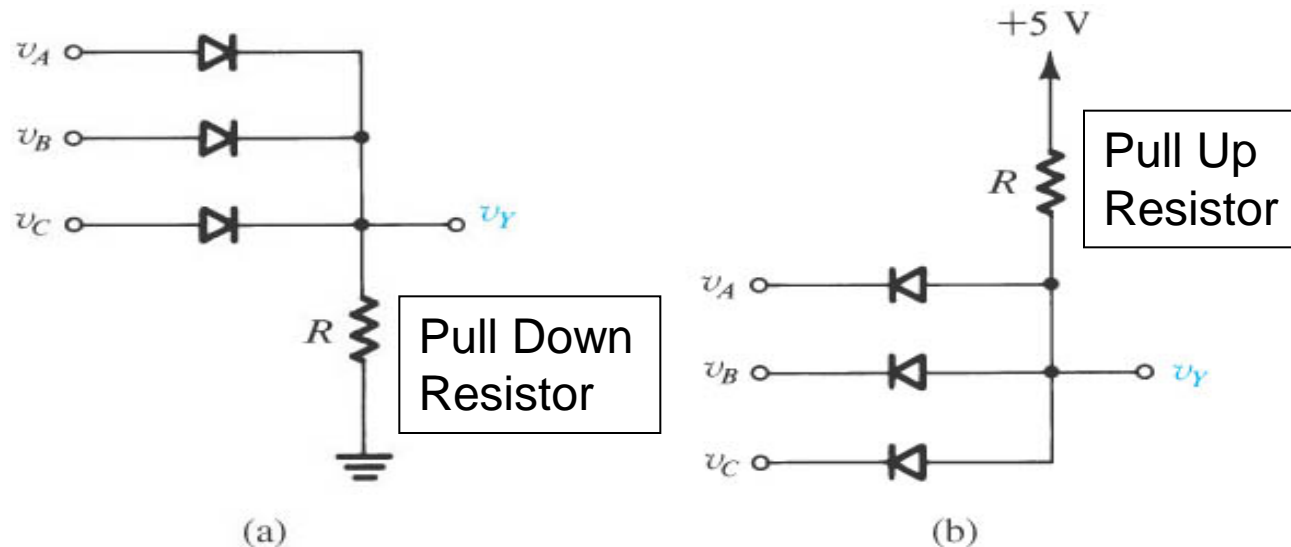


**Figure 3.5** Diode logic gates: (a) OR gate; (b) AND gate (in a positive-logic system). Source: Page 144 Sedra and Smith 5th Edition

 If 0V represents 0 and +5V represents 1 (positive logic) then:

- Circuit (a) will have 5V at  $v_Y$  if any of  $v_a, v_b, v_c$  are +5V with any diode or all diodes in the 'on' state; it will be 0V at  $v_Y$  (pulled down by resistor  $R$ ) if all inputs are 0V and thus the diodes are all 'off' the logic OR function.
- Circuit (b) will have 0V at  $v_Y$  if any of  $v_a, v_b, v_c$  are 0V with any diode then forward biased ('on' state) but if all of  $v_a, v_b, v_c$  are at +5V then the diodes will be 'off' and  $v_Y$  will be +5V (pulled up by  $R$ ) thus implementing a logic AND function

# Circuits with Ideal Diodes



Q? For the circuit shown find the current  $I$  and the Voltage  $V$ .  
(problem 3.9a from Sedra and Smith)

Ans: We need to determine if  $D_1$ ,  $D_2$  or both are conducting? So we should make plausible assumptions, proceed and then determine if these assumptions lead to a consistent solution.

So it seems plausible that both  $D_1$  and  $D_2$  are conducting.

If so then all 5V is dropped across the 5kohm resistor  $R_1$ ; resulting in current through  $R_1 = 5/5k = 1mA$ ;


Also if  $D_2$  is conducting  $V = 0$  volts and the current through  $R_2 = (0 - (-5))/10k = 0.5mA$

Which means that  $I = 1mA - 0.5mA = 0.5mA$

This seems to be a consistent solution

In fact if  $D_2$  isn't conducting then the voltage  $V_a$  must be less than -5V and  $D_1$  must be on (for a current flow) but once  $D_1$  is on then  $V_a$  must be 0 volts (as  $D_1$  is ideal and will have a 0 volt drop across it) so such a solution is not consistent;

# Circuits with Ideal Diodes

 

Now consider this circuit, once again  
 let's assume that  $D_1$  and  $D_2$  are 'on'.  
 If this is so then  $V_B = 0$  and  $V = 0$

The current in  $D_2$ ,

$$I_{D2} = \frac{10 - 0}{5} = 2\text{ mA}$$

Forming KCL (Kirchhoff's Current Law)  
 nodal equation at node B gives:

which results in an inconsistent  
 current for  $I$  of  $-1\text{ mA}$ !! So  $D_1$  and  $D_2$   
 cannot be both on!

# Circuits with Ideal Diodes

Now assume  $D_1$  is 'off' and  $D_2$  is 'on'


The current in  $D_2$  is then:

$$I_{D2} = \frac{10 - (-10)}{(10 + 5)} = 1.33mA$$

and the voltage at node B is:

$$V_B = -10 + (10 * 1.33) = +3.3V$$

 Which is consistent with  $D_1$  being off and  $D_2$  being on;  
hence  $V_B = 3.3V$  and  $I = 0$  for this circuit





# Circuits with Ideal Diodes

Q?: The figure shows a circuit for an ac voltmeter. It utilizes a moving coil meter that gives a full scale reading when the average current flowing through it is 1mA. The moving coil meter has a resistance of 50 ohms. Find the value of R that results in the meter indicating full scale reading when the input sine wave voltage  $v_I$  is 20 Volts peak to peak. Given that the average of a half sine wave (result of half wave rectification with ideal diode) is peak value divided by  $\pi$ .

Ans: Peak current = (10 Volts peak) / (R+50 $\Omega$ )

$$\text{Thus average current} = \frac{1}{\pi} \cdot \frac{10}{R + 50}$$

  
Equate this to 1mA (for full scale deflection) and re-arranging results in an R =3133 $\Omega$




 
# Real Diodes: Diode Markings


- The Cathode (K) is usually marked with a silver bar
- Example:



# Real Diodes

## Silicon Junction Diode

The current-voltage relationship of a typical silicon junction diode appears like this:

 


**Figure 3.7** The  $i-v$  characteristic of a silicon junction diode.

# Real Diodes

## Silicon Junction Diode

Three distinct regions are:

 - i) The **forward bias** region, determined by  $v > 0$
- ii) The **reverse bias** region, determined by  $v < 0$
- iii) The **breakdown** region, determined by  $v < -V_{ZK}$



Note: below 0.5V  
the current is negligibly small  
The voltage 0.5V is referred to as the  
**cut-in voltage**

**Figure 3.8** The diode  $i-v$  relationship with some scales expanded and others compressed in order to reveal details.

# Real Diodes: Silicon Junction Diode

## Forward Bias Region

When  $v > 0$  we have:

- i-v relationship closely approx. by  $\rightarrow$

$$i = I_s \left( e^{v/nV_T} - 1 \right)$$

- $I_s$  is usually called the **Saturation Current** (sometimes called the **Scale Current**)
- For small signal diodes (low power) it has a value in the order of  $10^{-15}$  Amps
- Rule of thumb: for every 5 degrees of temperature  $I_s$  doubles in value
- $V_T$  is called the thermal voltage
  - given by:
  - $k = \text{Boltzmann's constant} = \frac{kT}{q}$  joules / kelvin
  - $T = \text{the absolute temperature in kelvins} = 273 + \text{temp in celsius}$
  - $q = \text{the magnitude of charge of an electron} = 1.60 \times 10^{-19}$  coulomb

# Real Diodes: Silicon Junction Diode

## Forward Bias Region

$$i = I_S \left( e^{v/nV_T} - 1 \right)$$

- For  $V_T$ :
  - At room temperature (20 degrees C) the value of  $V_T$  is 25.2mV
  - At 25 degrees (often assumed for electronic equipment stored in a cabinet) it is 25.8mV
  - For simplicity we will use 25mV
- The constant  $n$  in equation:
  - Has a value between 1 and 2 (function of material used and physical structure of diode)
  - Normally assume  $n=1$  (unless stated otherwise)

# Real Diodes: Silicon Junction Diode

## Forward Bias Region

For the case where the current  $i \gg I_s$  the approximation that can be used is:

$$i \cong I_s e^{v/nV_T}$$

Alternatively we can express this in logarithmic (natural-base e) form:

$$v \cong nV_T \ln\left(\frac{i}{I_s}\right)$$

Exponential i-v relationship holds over many decades of current – can be as much as a span of 7 decades ie a factor of  $10^7 \implies$  This also applies to BJT's

# Real Diodes: Silicon Junction Diode

## Forward Bias Region

Using

$$i \cong I_S e^{v/nV_T}$$

And evaluating the current  $I_1$  which related to a diode voltage  $V_1$  we have:

$$I_1 = I_S e^{V_1/nV_T}$$

And evaluating the current  $I_2$  which related to a diode voltage  $V_2$  we have:

Dividing the second equation by the first gives:

$$\frac{I_2}{I_1} = e^{(V_2 - V_1)/nV_T}$$

# Real Diodes: Silicon Junction Diode

## Forward Bias Region

Taking natural logarithms of both sides gives:

$$\ln\left(\frac{I_2}{I_1}\right) = \ln\left(e^{(V_2-V_1)/nV_T}\right)$$
$$\ln\left(\frac{I_2}{I_1}\right) = (V_2 - V_1)/nV_T$$

which means that:

$$V_2 - V_1 = nV_T \ln\left(\frac{I_2}{I_1}\right)$$

Or we can get the results in terms of log10 by changing the base:

Since,

$$\log_a N = \frac{\log_b N}{\log_b a}$$
$$\therefore \ln\left(\frac{I_2}{I_1}\right) = \frac{\log_{10}\left(\frac{I_2}{I_1}\right)}{\log_{10} e} \quad \text{where} \quad \frac{1}{\log_{10}(e)} \cong 2.3$$

Which gives:

$$V_2 - V_1 = 2.3nV_T \log_{10}\left(\frac{I_2}{I_1}\right)$$



# Real Diodes: Silicon Junction Diode

## Forward Bias Region

$$V_2 - V_1 = 2.3nV_T \log_{10} \left( \frac{I_2}{I_1} \right)$$

Simply stated, for a decade of change in current the diode voltage drop changes by  $2.3nV_T$ :

- About 60mV for  $n=1$
- About 120mV for  $n=2$

This suggests that diode  $i$ - $v$  characteristics are best plotted on semi-log paper or scales--- using  $v$  as vertical & linear axis, and  $i$  as the horizontal and log scaled axis one will obtain a straight line with a slope of  $2.3nV_T$  per decade of current


Not knowing 'n' circuit designers use the rule of  $2.3nV_T$  being equal to 0.1 V ie a 0.1V/decade change

# Real Diodes: Silicon Junction Diode

## Forward Bias Region

- Note that diodes with different current ratings will experience a **0.7 V drop** (used as a **rule of thumb** for a fully conducting diode which will be typically in the range of 0.5-0.8V drop- and the basis of the model we will most often employ for diodes) at different currents (see assignment)
- Also,  $I_S$  and  $V_T$  are both temperature dependent which means forward i-v characteristic is also a function of temperature:

**Figure 3.9** Illustrating the temperature dependence of the diode forward characteristic. At a constant current, the voltage drop decreases by approximately 2 mV for every 1°C increase in temperature. (pg 151 Sedra&Smith)  
This characteristic has been exploited to produce electronic thermometers!

 

# Real Diodes: Silicon Junction Diode

## Reverse Bias Region

From  $i = I_S (e^{v/nV_T} - 1)$  (in theory), if  $v$  is negative and a few times larger than  $V_T$  then we can say that:

$$i \cong -I_S$$

That is the current in the reverse direction is constant and equal in magnitude to the saturation current (this constancy is the origin of its name!)

Real diodes exhibit currents that are still small but larger than  $I_S$  would indicate

- eg a small signal diode has  $I_S$  about  $10^{-14}$  to  $10^{-15}$  Amps but the reverse current could be of the order of  $1\text{nA}(10^{-9})$

There is also a tendency for the reverse current to increase in magnitude with the reverse voltage

The reverse current is less sensitive to temperature changes doubling (rule of thumb) every  $10^\circ\text{C}$  rise in temperature (see slide 17)

We normally don't need to consider this in an analysis as currents are small compared to a forward biased current

# Real Diodes: Silicon Junction Diode

## Break down Region

- Used in Zener diodes (diodes designed to be operated in the breakdown region)
- Once the reverse voltage exceeds a voltage called the breakdown voltage the diode will conduct in the reverse direction
- Provided power dissipation is limited by the surrounding circuit topology to a safe level (refer to devices data sheet) the diode can be operated in the breakdown region – normally we only do this to zener diodes in our designs
- One application of the breakdown region is that of a voltage regulator as its  $i$ - $v$  characteristic is almost vertical

# Diode Models

## Forward Bias


### The Exponential Model

- Most accurate model
- Severely non-linear so difficult to use
- A **graphical technique** is employed with a load line or an **iterative technique** is employed

# Diode Models Forward Bias

## Exponential Model

Consider the circuit:

 

We have:

$$I_D = I_S e^{V_D / n V_T}$$

And using KVL:

$$I_D = \frac{V_{DD} - V_D}{R}$$


We will assume that  $n$  and  $I_S$  are known

# Diode Models Forward Bias

## Exponential Model
 
### Graphical Analysis

- Intersection of load line and i-v gives values for  $I_D$  and  $V_D$
- Too much effort for other than simple circuit!



For v-axes let the current be 0 ( $i=0$ , open circuited diode) and then work out the voltage which would just be the supply voltage – gives  $v=0$  crossing

# Diode Models Forward Bias

## Exponential Model

### Iterative Analysis


Let  $R=1\text{ k}\Omega$  and  $V_{DD}=5\text{ V}$ . Assume  $V_D=0.7\text{ V}$ ,

and a voltage drop changes by

0.1V/decade then:

$$I_D = \frac{V_{DD} - V_D}{R}$$

$$= \frac{5 - 0.7}{1} = 4.3\text{mA}$$

 

Now use the diode equation to get a better estimate for  $V_D$ :

$$V_2 - V_1 = 2.3nV_T \log_{10} \left( \frac{I_2}{I_1} \right)$$

Using  $2.3nV_T = 0.1\text{ V}$  (ie a 0.1V/decade change)

solving with  $V_1=0.7; I_1=1\text{mA}$ ;

$$V_2 = V_1 + 0.1 * \log_{10} \left( \frac{I_2}{I_1} \right) \quad I_2=4.3\text{mA leads to } V_2=0.763\text{V}$$



# Diode Models Forward Bias

## Exponential Model

### Iterative Analysis

The result of the first iteration is then:

$$I_D = 4.3 \text{ mA and } V_D = 0.763 \text{ V}$$

Now use these values in a second iteration:

$$\begin{aligned} I_D &= \frac{V_{DD} - V_D}{R} \\ &= \frac{5 - 0.763}{1} = 4.237 \text{ mA} \end{aligned}$$


and:

$$\begin{aligned} V_2 &= V_1 + 0.1 * \log_{10} \left( \frac{I_2}{I_1} \right) \\ &= 0.763 + 0.1 * \log_{10} \left( \frac{4.237}{4.3} \right) \\ &= 0.762 \text{ V} \end{aligned}$$

The result of the second iteration is then:

$$I_D = 4.237 \text{ mA and } V_D = 0.762 \text{ V}$$

 Which is the solution since the change was very small from first iteration



# Diode Models Forward Bias

## Piecewise-Linear Model


- Approximates the curve by two straight lines, line A with 0 slope and line B with non zero slope
- Difference between actual and real is less than 50mV
- Could refine to restrict to current ranges and get more lines but closer match to real curve

Mathematically:

$$i_D = 0, \quad v_D \leq V_{D0}$$
$$i_D = (v_D - V_{D0})/r_D, \quad v_D \geq V_{D0}$$

Where  $V_{D0}$  is the intercept of line B on V-axes and  $r_D$  is the inverse slope of line B


**Figure 3.12** Approximating the diode forward characteristic with two straight lines: the piecewise-linear model. Pg 156 Sedra and Smith

 

# Diode Models Forward Bias

## Piecewise-Linear Model

The models equivalent circuit is:

 


**Figure 3.13** Piecewise-linear model of the diode forward characteristic and its equivalent circuit representation.  
Pg 156 Sedra and Smith

 Also known as battery-plus resistance model

# Diode Models Forward Bias

## Piecewise-Linear Model



Using the same example as for the exponential model with parameters (from graph) of  $V_{D0}=0.65$  V and  $r_D=20\Omega$  we will re-solve using the Piecewise linear model:


The circuit becomes:

Then for  $I_D$  we have:

$$\begin{aligned} I_D &= \frac{V_{DD} - V_{D0}}{R + r_D} \\ &= \frac{5 - 0.65}{1 + 0.02} \\ &= 4.26 \text{ mA} \end{aligned}$$

The Diode voltage is then:
 
$$\begin{aligned} V_D &= V_{D0} + I_D r_D \\ &= 0.65 + 4.26 \times 0.02 = 0.735 \text{ V} \end{aligned}$$




Compared to 4.237mA and 0.762V for exponential model

# Diode Models Forward Bias
 
## Constant Voltage Drop Model


- Simplest diode model
- Most often employed in quick calculations and at the initial phases of electronic design
- Uses a fixed forward bias diode drop of 0.7 V (usually) for silicon diodes
- The i-v curve for this model (compared to exponential) is:
- It is clearly a form of the piecewise linear model where line B has infinite slope! ( $r_D = 0\Omega$ ) And  $V_{D0} = 0.7\text{ V}$




# Diode Models Forward Bias

## Constant Voltage Drop Model

The equivalent circuit of this model is:

 

(a)

 

(b)

To solve our earlier problem here  $V_D = 0.7$  V and  $I_D$  is given by:

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.7}{1} = 4.3 \text{ mA}$$

Compared to 4.237mA and 0.762V for exponential model

# Diode Models Forward Bias

## Ideal Diode Model

- Already seen this model
- Used as a gross estimate of circuit performance
- For little extra effort the assumption of a fixed 0.7 V gives more realistic results
- Ideal diode model most often used to decide which diodes are 'on' and which 'off' in a circuit topology

# Break



# Diode Models Forward Bias

## Small Signal Diode Model

- Some circuit applications will require a diode to operate at a certain voltage and current and have a small signal superimposed on it
- In such circumstances we use one of the previous models (most likely the constant voltage model) to calculate the DC biasing point and then we need to calculate the effect of a small AC signal superimposed on the DC bias point
- To do this we can use the small signal diode model
- It is based on taking the slope of a tangent to the exponential curve at the calculated Q point (the DC bias point)

# Diode Models Forward Bias



Small signal  
Approximation:

$$i_D(t) \cong I_D \left( 1 + \frac{v_d}{nV_T} \right) \longrightarrow i_D(t) = I_D + i_d \longrightarrow i_d = \frac{I_D}{nV_T} v_d$$

Provided:  $\frac{v_d}{nV_T} \ll 1$

Where  $v_d$  and  $i_d$  are time dependent small signal variations as shown

  Note: This approx. is valid for signals whose amplitudes at 20 °C ( $V_T=25\text{mV}$ ) is 10mV if  $n=2$  and 5mV if  $n=1$



$$v_D(t) = V_D + v_d$$

# Diode Models Forward Bias

## Small Signal Diode Model

The relationship between small signal current,  $i_d$ , and small signal voltage,  $v_d$ , is:

$$\frac{i_d}{v_d} = \frac{I_D}{nV_T}$$

It has the dimensions of conductance, mhos ( )

It is called the **diode small-signal conductance**

The inverse of this parameter is the diode **small-signal resistance** or **incremental resistance**,  $r_d$

Note:  $r_d$  is inversely proportional to bias (DC) current  $I_D$

# Diode Models Forward Bias

## Small Signal Diode Model

Point to note:

Using the principle of superimposition, and provided the small signal Superimposed is small such that:

$$\frac{v_d}{nV_T} \ll 1$$

then we can calculate the DC bias point first then do the AC analysis by eliminating ALL DC sources by:

- Short circuiting DC voltage sources
- Open circuiting DC current sources


Then replace the diode with its small signal resistance

# Diode Models Forward Bias

## Small Signal Diode Model

 Example: Consider the circuit shown

The  $V^+$  terminal is providing a 21 V DC supply with a superimposed sinusoidal **ripple voltage** with frequency 50Hz and peak amplitude of  $\sqrt{2}$  volts. Calculate the DC voltage of the diode and the amplitude of the sine wave appearing across it. Justify the use of the small signal model. Assume the diode has a 0.7 Volt drop at 1mA current and the value of 'n' is 2.



# Diode Models Forward Bias

## Small Signal Diode Model


### Example

#### DC calculation:

Assume  $V_D \cong 0.7V$  and calculate the diode current (ie use constant voltage drop model):

$$I_D = \frac{V^+ - V_D}{R} = \frac{21 - 0.7}{20} = 1.015mA$$

 as this is very close to 1mA we can be reasonably certain that the voltage drop will be 0.7V



# Diode Models Forward Bias

## Small Signal Diode Model

### Example

Small Signal Model:

At the DC operating point we can calculate the diode incremental resistance,  $r_d$ :

$$r_d = \frac{nV_T}{I_D} = \frac{2 \times 25mV}{1.015mA} = 49.26\Omega$$

For this example  $n=2$ ; normally we will assume  $n=1$  unless told otherwise!

# Diode Models Forward Bias


## Small Signal Diode Model

### Example

The small signal equivalent circuit with suppressed DC sources is then →

Using the voltage divider rule the peak amplitude  $v_d$  can be found as:
 
$$\begin{aligned} v_d(\text{peak}) &= v_s \cdot \frac{r_d}{R + r_d} \\ &= \sqrt{2} \cdot \frac{0.04926}{20 + 0.04926} = 3.475 \text{ mV} \end{aligned}$$




Since this is quite small (since  $n=2$  we use  $<10\text{mV}$  ;see slide 41) it satisfies the small signal criteria and justifies our use of the model!


 
# Zener Diodes


- Diodes designed to operate in the breakdown region
- Have application in voltage regulators but now these have special purpose devices that do this (not as important as they once were)
- Can also be called breakdown diodes
- The circuit diagram of a zener is:



- Normal applications of zener diodes is current flows into the cathode, and the cathode is +ve with respect to the anode which means that  $I_Z$  and  $V_Z$  have +ve values in this diagram

# Zener Diodes

Cathode

 


# Zener Diodes

i-v characteristics of zener breakdown region:

Note that for  $V_{Z0}$  and  $V_{ZK}$   
In practice their values  
Are almost equal!

Point at which the line with slope  $1/r_z$   
intersects the voltage axes

 Good idea to avoid  
Operation around  
Knee as here the  
Slope varies widely  
and hence the  
**Incremental**  
(dynamic) resistance  
 $r_z$  ( this is also  
Specified in data sheets)  
will also vary widely



**Knee current:** for  
currents above this  
the zener current is  
nearly a straight line

**Zener test current,**  
specified in data sheet  
intersects with curve at  
Q, changes in  $i$  will cause  
slight changes in  $v$


# Zener Diodes Model

Using the values from the breakdown curve as labeled, the Zener Voltage ,  $V_Z$ , can be given as:

$$V_Z = V_{Z0} + r_z I_z$$

which applies for  $I_Z > I_{Zk}$  and  $V_Z > V_{Z0}$  (the breakdown region where curve conducts nearly linearly); with  $r_z$  given by the inverse of the slope in the breakdown region at the operating point , Q and we know that:

So the equivalent circuit model is:

 

$$\Delta V = r_z \Delta I$$



# Special purpose Diode

## Schottky Barrier Diode (SBD)

- Schottky Barrier Diode is formed by bringing metal into contact with a moderately doped n-type semiconductor material
- Also called hot carrier diodes
- Similar to Silicon Diode characteristic but
  - Current is conducted by electrons (major carriers) without a minority carrier charge storage effect at forward biased pn junction which means a faster on-off and off-on switching characteristic
  - Slightly higher currents flow when diode is reverse biased compared to silicon
  - Typically forward voltage drop of 0.3V to 0.5V are achieved compared to 0.6V to 0.8V of silicon
- Applications in design of GaAs circuits (very specialised) and in design of special purpose Bipolar transistor logic circuits called Schottky-TTL (transistor to transistor logic)

 
 
# Super Diode

Consider this op-amp circuit and its output voltage vs input voltage transfer characteristic:


  
# Super Diode

When the input voltage,  $v_i$ , is +ve then the output voltage  $v_A$  goes +ve and the diode will conduct



Which establishes a closed feedback path between the op-amps Output and its negative input, this results in a voltage follower type Situation with the virtual short occurring so the voltage at the Positive input will equal the voltage at the negative input ie

$$v_o = v_i \quad v_i \geq 0$$

For this op-amp to start operation the input voltage needs to exceed  $0.7/(\text{open loop gain of Op-Amp}, A) \rightarrow$  as the op-amp gain is typically very large, this voltage will be very small!

# Super Diode

Example if Open Loop  
Gain,  $A=100,000$  then  
this voltage is  $7\mu\text{V}$



What about  $v_i$  negative?

When negative the diode

will become reverse biased, ie it will open circuit. This will force the op-amp into open loop mode and the output  $v_a$  will swing to the negative voltage rail, as no current can pass through the op-amps -ve terminal or diode (in real devices insignificant currents) then no current flows through the load resistor  $R$  and the output  $v_o$  is also 0V's as shown ie:

$$v_o = 0 \quad v_i < 0$$

 
 
This circuit is suitable for low frequency and small voltages  
eg rectification of 100 mV sinusoidal/AC signal





# Super Diode

see pg1208 Sedra and Smith

  


## Disadvantages:


- When input voltage is negative and output voltage is zero all of the input voltage's magnitude appears across the two input terminals of the op-amp --- if this is greater than a few volts the op-amp will need **overvoltage protection** (most modern op-amps have this) or it could be damaged
- When the input voltage is negative the op-amp will be saturated and to return to the op-amps linear operation will take time (hence the low frequency requirement)

An improved circuit is possible!

# Super Diode with 2 Diodes!

 

(a)

 

(b)


**Figure 13.34** (a) An improved version of the precision half-wave rectifier: Diode  $D_2$  is included to keep the feedback loop closed around the op amp during the off times of the rectifier diode  $D_1$ , thus preventing the op amp from saturating. (b) The transfer characteristic for  $R_2 = R_1$ .  
pp.1208 Sedra and Smith

This circuit does not suffer from the problems of the original circuit – delay and need for over-voltage protection

## Operation:


- $D_2$ , for *positive input* voltage, closes the –ve feedback loop around the op-amp resulting in a virtual ground appearing across the inverting input and the op-amp output is clamped at one diode forward bias voltage drop below ground; this means that  $D_1$  is reverse biased and thus no current flows through  $R_2$  (since there is no current return path) so then  $v_O$  is zero!

# Super Diode with 2 Diodes!

 

(a)

 Called **Catching diode**: since it “catches” the op-amp voltage as it goes negative and clamps it to a diode drop below ground!




(b)


## Operation:

- $D_2$ , for **negative input** voltage, is reverse biased as the the -ve input will now tend to go negative, with the output voltage going positive BUT now  $D_1$  will be able to conduct (and will since its forward biased) via  $R_2$  which results in a closed negative feedback path around the op-amp ; forcing a virtual ground to appear at the -ve input – as no current passes into the op-amp (ideal) or very little (real) - then all the current passes through  $R_1$  and  $R_2$  and this current is equal

# Super Diode with 2 Diodes!

 

(a)

 

(b)


- The output voltage is then given by:

$$v_o = -\frac{R_2}{R_1} v_i \quad \text{for } v_i \leq 0$$


- If  $R_1 = R_2$  the output voltage will be:

$$v_o = -v_i \quad \text{for } v_i \leq 0$$

# Super Diode with 2 Diodes!

 

(a)

 

(b)

## Advantages:


- feedback loop remains closed at all times and thus the op-amp remains in its linear region avoiding the possibility of saturation and the associated time delay to get out of saturation.
- It also now can be used without worrying too much about over-voltage protection required for the original super-diode (we have a virtual ground in operation)

# Limiting and Clamping Circuits
 
## Limiting Circuits

Diodes can be used in a limiting circuit

A generic transfer function for a limiting circuit is:



$$v_o = K v_i$$


Circuits we will look at have  $K \leq 1$   
And are known as passive limiters

# Limiting and Clamping Circuits
 
## Limiting Circuits

The transfer function depicted in Fig 3.32 describes a **double limiter** – where both positive and negative peaks are limited

A **single limiter** only work on one side of the peaks (either negative or positive but not both)




$$v_o = K v_i$$

**Figure 3.32** General transfer characteristic for a limiter circuit, pp. 185 Sedra & Smith

# Limiting and Clamping Circuits

## Limiting Circuits

Fig 3.33 shows the effect on a sinusoidal waveform passed into a double limiter – the peaks have been clipped ( a non-linear function) and hence sometimes these circuits are called **clippers**

 


**Figure 3.33** Applying a sine wave to a limiter can result in clipping off its two peaks.

 

# Limiting and Clamping Circuits

## Limiting Circuits



Hard Limiter characteristic

Smoother transition  
between linear and saturated region

 


Figure 3.34 Soft limiting.S&Smith pg185

Soft Limiter characteristic

Limiters find applications in **signal processing applications** such as a situation where Voltages can damage electronic components if exceeded: an example is used in The schools DSP C3x boxes where a circuit using diodes ensures students can't Exceed the specified limits of 0 to 5V DC – a fuse is used to limit current.

# Limiting and Clamping Circuits


## Limiting Circuits

(Modeling diodes using the constant 0.7V diode model) some examples of limiting circuits are:

**Figure 3.35** A variety of basic limiting circuits.  
Pg. 186 S&Smith
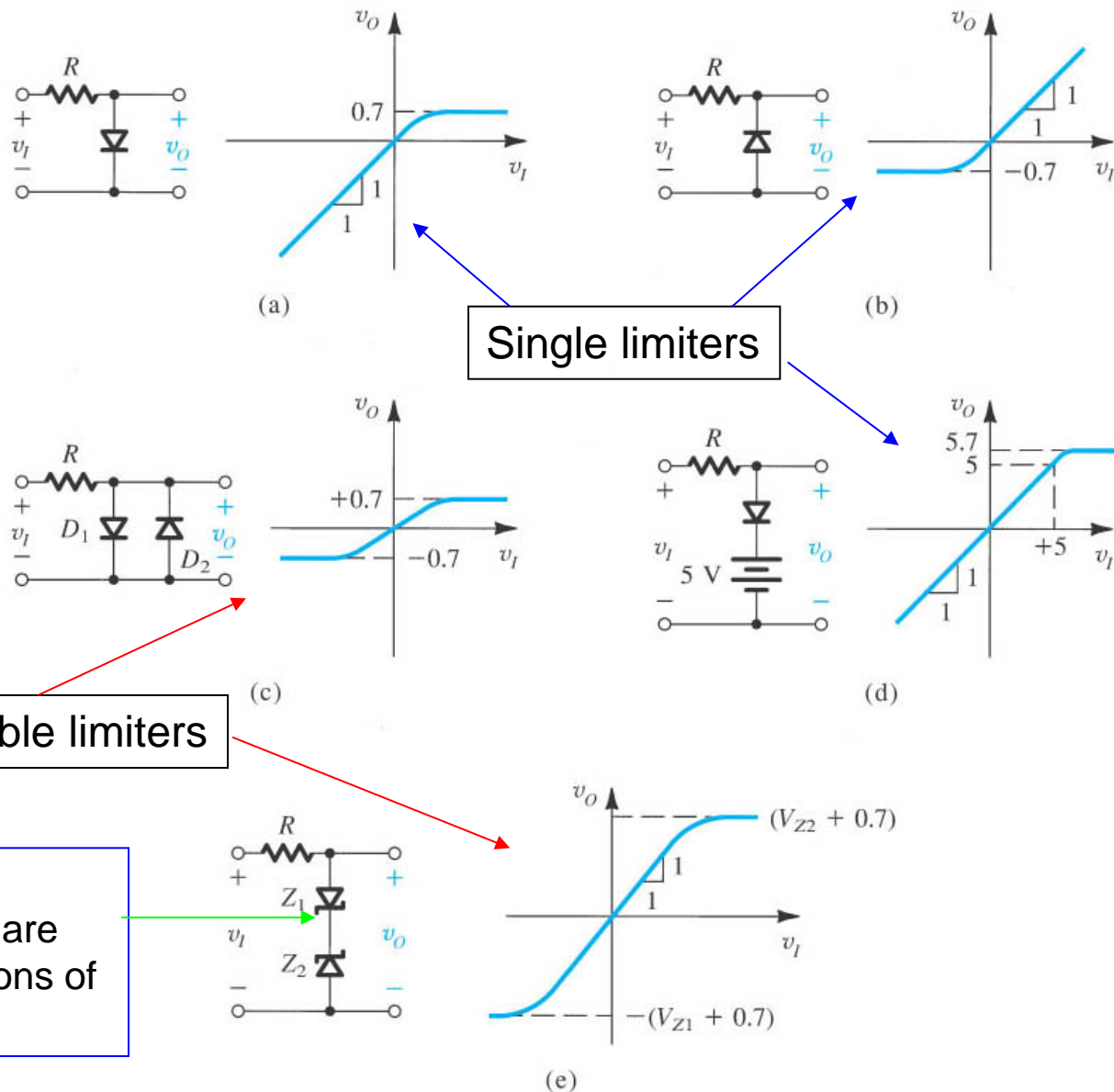
## Double limiters


Special pairs of zener diodes called **double-anode zener** diodes are Available commercially for applications of This type



# Limiting and Clamping Circuits
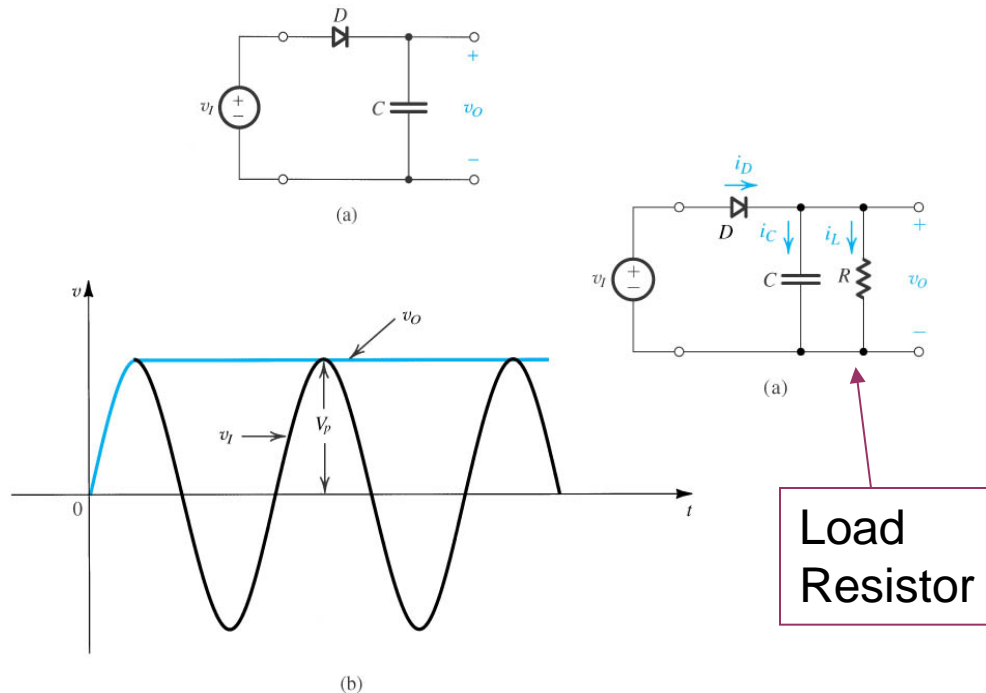
## The Clamped Capacitor or DC Restorer


A circuit (covered in detail in on pg 177-182) is the peak detector (or peak rectifier):



Load Resistor

Ripple voltage

$$V_r = \frac{V_p}{fCR}$$

 

**Figure 3.29** Voltage and current waveforms in the peak rectifier circuit with  $CR \ll T$ . The diode is assumed ideal.

# Limiting and Clamping Circuits

## The Clamped Capacitor or DC Restorer

Now if we take the peak detector circuit and look at the voltage across the diode instead of the capacitor we have a DC restorer:

 


Figure 3.36 The clamped capacitor or dc restorer with a square-wave input and no load. Pg. 188 S&Smith

Due to the polarity connection of the diode the capacitor in fig. (b) will charge to A voltage  $v_C$  with the polarity shown on the diagram (output pin positive)


This voltage will have the magnitude of the most negative peak of the input

Waveform – eventually the diode turns off and the capacitor retains the charge Indefinitely.

Example: in fig.(a) the most negative voltage of the square wave input is -6V, while The voltage range is 10V, then  $v_C$  will charge to 6V; the output voltage (using KVL) Is then the input voltage ( $v_i$ ) plus the capacitor voltage ( $v_C$ ) which gives the waveform At the output indicated by fig.(c) – the output has been shifted by  $v_C$  volts compared To the input waveform

# Limiting and Clamping Circuits

## The Clamped Capacitor or DC Restorer

 


**Figure 3.36** The clamped capacitor or dc restorer with a square-wave input and no load. Pg. 188 S&Smith

- The diode (with shown polarity) prevents the output voltage from going below  $0\text{ V}$  (ground) – done by conducting and charging up the capacitor – however the diode does not constrain the positive swing of  $v_O$  hence the circuit has the effect of *clamping the lowest peak* to  $0\text{ V}$  hence its alternate name the clamped capacitor!
- If we reverse the polarity then the highest peak will be clamped to  $0\text{ V}$
- If we pass a pulse or AC signal with a DC component through a capacitor coupling (or ac coupled system) then that signal will lose its DC component – we can use this circuit to restore a known DC component; a process known as *DC restoration* → hence the other name DC restorer

# Limiting and Clamping Circuits

## The Clamped Capacitor or DC Restorer

 

**Figure 3.36** The clamped capacitor or dc restorer with a square-wave input and no load. Pg. 188 S&Smith




### Application?

- DC component or average value of a pulse waveform is a measure of duty cycle (which is the proportion of each cycle occupied by the pulse)
- Duty cycle can be modulated (with information) in a process called Pulse Width Modulation (PWM) ie pulse width is changed to convey different signal (data) conditions eg speed control using H-bridge (special IC packages available –used in SoccerBot u/g thesis project 2004-6) for a small DC permanent magnet motor
- The DC Restorer followed by a Single Time Constant (RC) low pass filter could be used to find the average value of the pulse train (or superimposed pulses)

# Limiting and Clamping Circuits

If we now connect a load resistance,  $R$ , shunted across the diode the situation is different (alternatively, we could have used an op-amp voltage follower so its not loaded):

Diode conducts heavily and Capacitor charges

   

**Figure 3.37** The clamped capacitor with a load resistance  $R$ .

Pg 189 S&Smith



The capacitor can now be discharged through  $R$ , through  $t_0$  to  $t_1$  the capacitor discharges exponentially with time constant  $CR$  but during  $t_1$  to  $t_2$  the capacitor recovers its lost charge as the input voltage rises by  $V_a$  volts (diode conducts)

Just before  $t_2$  the output voltage is typically A few tenths of a volt negative say  $-0.5$  V

We can use the charge equilibrium to Calculate the average diode current And the detail of the output voltage
  
# The Voltage Doubler

If we have a clamped capacitor (DC restorer) stage followed (cascaded) by a peak detector (peak rectifier) stage we can provide a DC output voltage that is twice the input voltages peak value:





# The Diode Ring Modulator

For the Lab in weeks 8-13 as alternative!

- We can use diodes to do rectification (half-wave and full wave) and also to produce a Balanced modulator
- We will now briefly look at the Balanced modulator called a diode ring modulator (can get CA3039 IC for this purpose)


# The Diode Ring Modulator

For the Lab in weeks 8-13 as alternative!

- The diode ring circuit for a Balanced Modulator capable of providing Double Side Band Suppressed Carrier (or signal multiplication) is:

When message Signal is zero, Output Is zero (balanced) ie A and A' have the same voltage value (here 0)

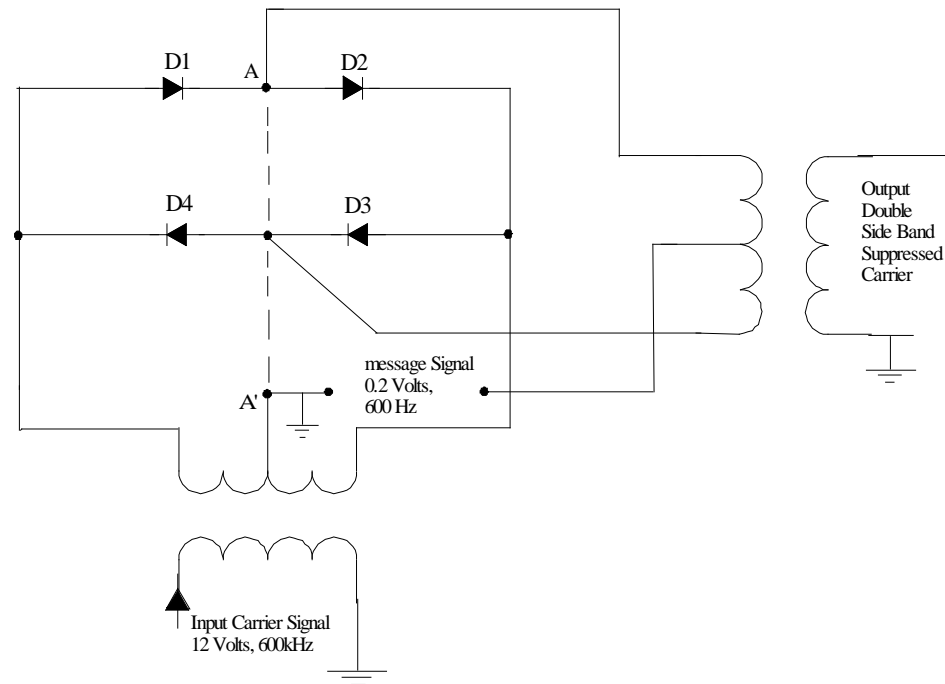When message is non zero then provided Diode forward biases are not Exceeded by amplitude of message signal the points A and A' are unbalanced and DSB-SC results With D1 and D2 conducting on one cycle and D4 and D3 on opposite Cycle – being modulated in unbalance by the message signal!



Mathematically:

$$A_c \cos(\omega_c t) \times A_m \cos(\omega_m t) = \frac{A_c A_m}{2} \cos((\omega_c - \omega_m)t) + \frac{A_c A_m}{2} \cos((\omega_c + \omega_m)t)$$

# EWB Simulation — Available on WebCT

