 



# The Operational Amplifier



$$V_S^- < V_{out} < V_S^+$$

Example:  $+V_S$  is +15 volts,  
 $-V_S$  is -15 volts  
Then  $V_{out}$  is somewhere  
Between the power  
Supply extremes!


# The Operational Amplifier

 

For an IDEAL operational amplifier we have  $A_{V(OL)} = \infty$

For a practical operational amplifier we have finite but large (typically 100000) value for the open loop gain,  $A_{V(OL)}$

# The Operational Amplifier

 


We have a differential input

Voltage,  $v_{in}$ , given by:  $v_{in} = v^+ - v^-$

We can then have the relationship between the output and differential input,  $v_{in}$ , as:

$$v_{out} = A_{V(OL)}(v_{in}) = A_{V(OL)}(v^+ - v^-) \quad 3$$

# The Operational Amplifier

 


Ideal operational amplifier  
Has infinite input resistance:

$$R_{in} = \infty$$

Non-Ideal operational amplifiers  
Have very large input resistance  
In the order of  $10^6 \Omega$ 's

# The Operational Amplifier

 

Since Ideal operational amplifier  
Have infinite input resistance:


$$R_{in} = \infty$$

Then the current into an ideal  
Op-amps terminals (+ve or -ve)

Is zero!  $i_{in}^{+} = i_{in}^{-} = 0$

Since Non-Ideal operational amplifiers  
Have very large input resistances of  
the order of  $10^6 \Omega$ 's so the current  
Into the Op-amps terminals is  
Negligibly small!

# The Operational Amplifier

 

Ideal operational amplifier


Have zero output resistance:

$$R_{out} = 0$$

Non-Ideal operational amplifiers  
Have very low Output Resistances  
*of the order of a few hundred ohms  
Or less!*

# The Operational Amplifier

Noninverting input

 

Inverting input

## SUMMARY

An IDEAL op-amp has:

Infinite Input Resistance

Zero Output Resistance

Infinite Open Loop Gain

Infinite Bandwidth

This is not true of non-ideal op-amps  
See ECTE212!

# The Operational Amplifier

## The Virtual Short Circuit

Consider an IDEAL  
Op-amp:

In this case  $R_{out}=0$

Then we have:

$$v_{out} = A_{V(OL)} v_{in}$$


If  $A_{V(OL)} \gg v_{out}$  And for  
IDEAL it is because  $A_{V(OL)}$  is infinite!

Then we can write:

$$v_{in} = \frac{v_{out}}{A_{V(OL)}} = v^+ - v^- \approx 0$$

or  $v^+ \approx v^-$  Which also means that

$$i_{in} = \frac{v^+ - v^-}{R_{in} \big|_{R_{in}=\infty}} \approx \frac{0}{\infty} = 0$$

 



# The Operational Amplifier

## The Virtual Short Circuit

Thus we have a Virtual short Circuit such That:


$$v_{in} = \frac{v_{out}}{A_{V(OL)}} = v^+ - v^- \approx 0$$

and

$$i_{in} = \frac{v^+ - v^-}{R_{in} \big|_{R_{in}=\infty}} \approx \frac{0}{\infty} = 0$$

and

$$v^+ \approx v^-$$

 

# The Operational Amplifier

## The Virtual Ground


If we set:  $v^+ = 0$

Then we have a  
Virtual ground  
Since for an ideal  
Op-amp:

$$v^- \approx v^+ = 0$$

Implies that:

$$v^- = 0$$

 


# The Operational Amplifier

Consider the relationship between the output and differential input,  $v_{in}$ , :

$$v_{out} = A_{V(OL)}(v_{in}) = A_{V(OL)}(v^{+} - v^{-})$$


If the difference between the +ve and -ve terminals is not close to zero, the infinite (or large) gain will drive the output to either A very large +ve or very large -ve value. Real op-amps will Saturate at the +ve supply Rail or -ve supply rail

 This allows the development of a Zero crossing circuit...




# The Operational Amplifier

## Zero-crossing comparator

 


# The Operational Amplifier

## Inverting comparator with offset

 

# The Operational Amplifier

 


Operational amplifiers are almost always used with negative feedback, in which part of the output signal is returned to the input in opposition to the source signal.
 
# The Operational Amplifier

In a negative feedback system, the ideal op-amp output voltage attains the value needed to force the differential input voltage and input current to zero.

- Part of the output is returned to the input
- The feedback signal opposes the input source



## Comment

When the fed back signal opposes the Input we call this negative feedback

Note we will find that by providing Negative feedback from the output to the input That the infinite gain is changed to some Finite gain – this is one of the typical Consequences of negative feedback



# The Operational Amplifier

## Analysis of Ideal Op-Amp

- Verify that negative feedback is present
- Assume that the differential input voltage and the input current of the op-amp are zero
- Apply standard circuit analysis principles

# The Operational Amplifier

## The Inverting Amplifier


Consider the situation where we connect the +ve terminal To ground and the -ve terminal is connected via A feedback ( $R_F$ ) resistor to the output and then the input is Connected to another resistor ( $R_S$ ) to the –ve terminal:

The currents are shown, where  $i_F$  is the Current from the output to the –ve terminal Through the feedback resistor  $R_F$  and  $i_S$  is the current from the input voltage source  $v_S$  into the the input resistor  $R_S$

$i_{in}$  is the current into the –ve terminal Of the op-amp

Now if we assume that the op-amp Is ideal then the current into the –ve Terminal is zero , that is:

$$i_{in} = 0 \quad \text{IDEAL OP-AMP}$$

 

# The Operational Amplifier


## The Inverting Amplifier

Given that  $i_{in}$  is zero we can apply KCL at the  $-ve$  terminal:

$$i_S + i_F - i_{in} = 0 \implies i_S + i_F = 0$$

Now we know that by grounding the  $+ve$  input  
Due to the infinite gain of the Ideal Op-Amp  
That the  $-ve$  terminal will also have the same  
Voltage (virtual short circuit property), so  
This means the  $-ve$  terminal has a voltage of  
Zero (0) volts! Which means that:
 
$$i_S = \frac{v_S - v^-}{R_S} = \frac{v_S - 0}{R_S} = \frac{v_S}{R_S}$$



# The Operational Amplifier

## The Inverting Amplifier

We can also calculate  $i_F$  using:


$$i_F = \frac{v_{out} - v^-}{R_F} = \frac{v_{out} - 0}{R_F} = \frac{v_{out}}{R_F}$$

Now we apply our equation for KCL at  
The -ve node to get:

$$i_S + i_F = 0 = \frac{v_S}{R_S} + \frac{v_{out}}{R_F}$$

Which after rearranging gives:
 
$$\frac{v_{out}}{v_S} = -\frac{R_F}{R_S} = \text{Gain} = A_v$$




# The Operational Amplifier

## The Inverting Amplifier

The input resistance looking  
In from the terminal (a) to  
Ground for the inverting  
amplifier is in fact the  
Value of the resistor  $R_S$ :


$$R_{in} = R_S \equiv \frac{v_S}{i_S}$$

 

# The Inverting Amplifier
 
## Example

If the input voltage,  $v_S$ , is 2 volts DC and the supply rails are +15 volts and -15 volts respectively (not Shown) what is the output Voltage  $v_{out}$  equal to when  $R_S=10\text{ k}\Omega$  and  $R_F=20\text{ k}\Omega$ ?



Answer: 
$$\frac{v_{out}}{v_S} = -\frac{R_F}{R_S} = \text{Gain} = A_v = -\frac{20000\ \Omega}{10000\ \Omega} = -2$$


$$\therefore v_{out} = -2v_S = -2 \times 2 = -4\ \text{volts}$$

Notice that this voltage is still between the voltage supply rails of the op-amp  
And is inverted (opposite polarity) to the input voltage

# The Inverting Amplifier
 
## Example

If the input voltage,  $v_S$ , is -3.333 volts DC and the supply rails are +15 volts and -15 volts respectively (not Shown) what is the output Voltage  $v_{out}$  equal to when  $R_S=1\text{ k}\Omega$  and  $R_F=3\text{ k}\Omega$ ?




Answer: 
$$\frac{v_{out}}{v_S} = -\frac{R_F}{R_S} = \text{Gain} = A_v = -\frac{3000\ \Omega}{1000\ \Omega} = -3$$

$$\therefore v_{out} = -3v_S = -3 \times \left( \frac{-10}{3} \right) = +10\ \text{volts}$$
 
# Example

If the input voltage,  $v_S$ , is  
 $(3\sqrt{2})\sin(2000 \times \pi \times t)$  volts  
and the supply rails are +15 volts  
and -15 volts DC respectively (not  
shown) what is the output Voltage  $v_{out}$   
equal to when  $R_S=10\text{ k}\Omega$  and  
 $R_F=15\text{ k}\Omega$ ?






Answer: 
$$\frac{v_{out}}{v_S} = -\frac{R_F}{R_S} = \text{Gain} = A_v = -\frac{15000\ \Omega}{10000\ \Omega} = -1.5$$

$$\begin{aligned}\therefore v_{out} &= -\frac{3}{2}v_S = -\frac{3}{2} \times (3\sqrt{2}\sin(2000 \times \pi \times t)) \\ &= -\frac{9}{\sqrt{2}}\sin(2000 \times \pi \times t) \text{ volts}\end{aligned}$$




# Example

  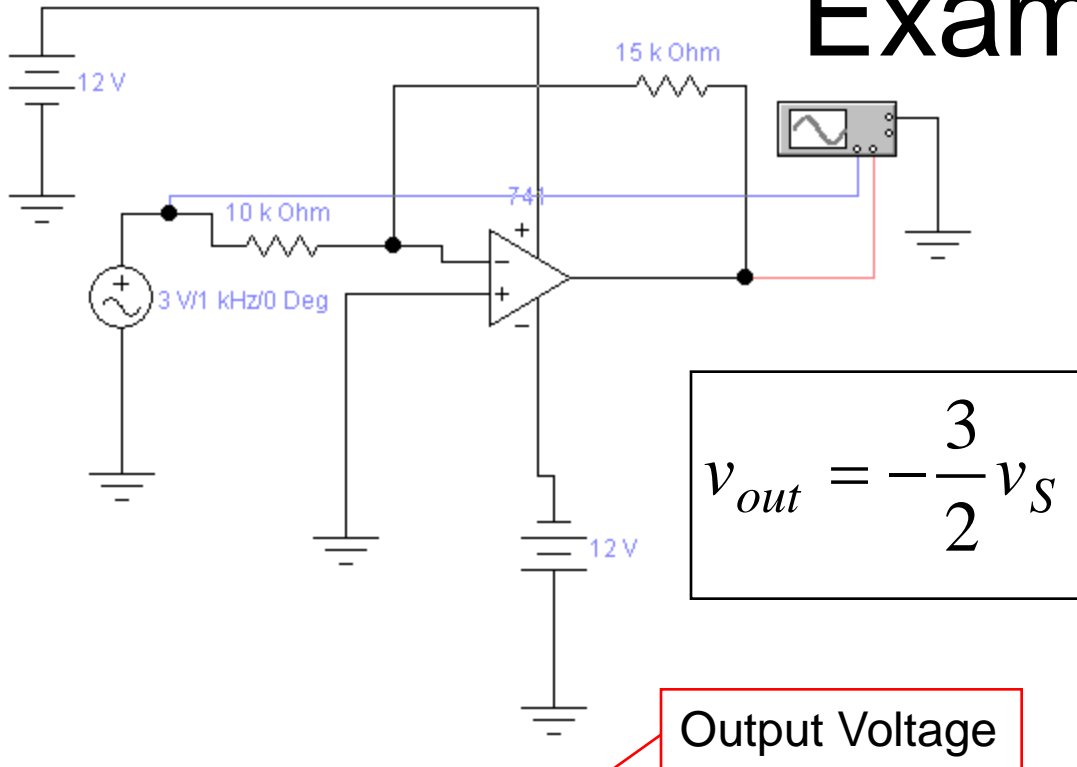

We say that the inverter results in the Output sinusoid being 100% out of Phase with the input sinusoid (that is the inversion of the input signal)

# The Operational Amplifier

## The Inverting Amplifier

 


We can use the same technique to analyse this circuit (which is still an inverting amplifier!)

# The Operational Amplifier

## The Inverting Amplifier

Consider

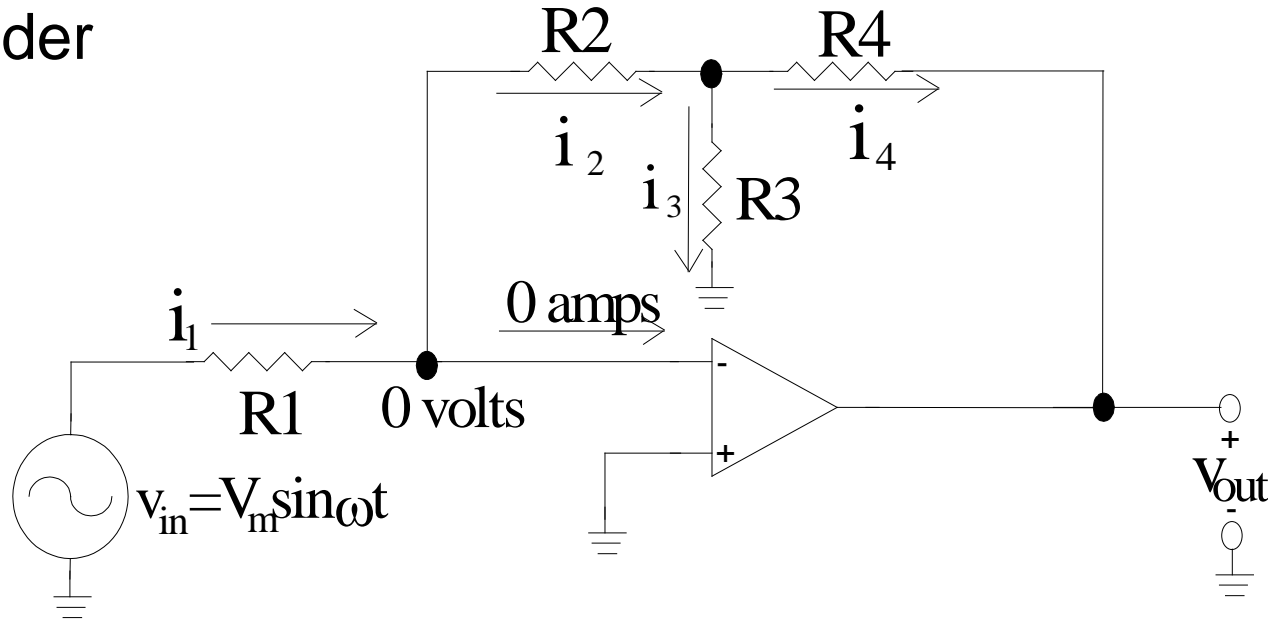


As before we apply KCL at the -ve terminal to get:

$$i_1 - 0 - i_2 = 0 \quad \text{Or} \quad i_1 = i_2$$

We can calculate  $i_1$  using Ohms law: 
$$i_1 = \frac{v_{in} - 0}{R1} = \frac{v_{in}}{R1}$$

# The Operational Amplifier

## The Inverting Amplifier

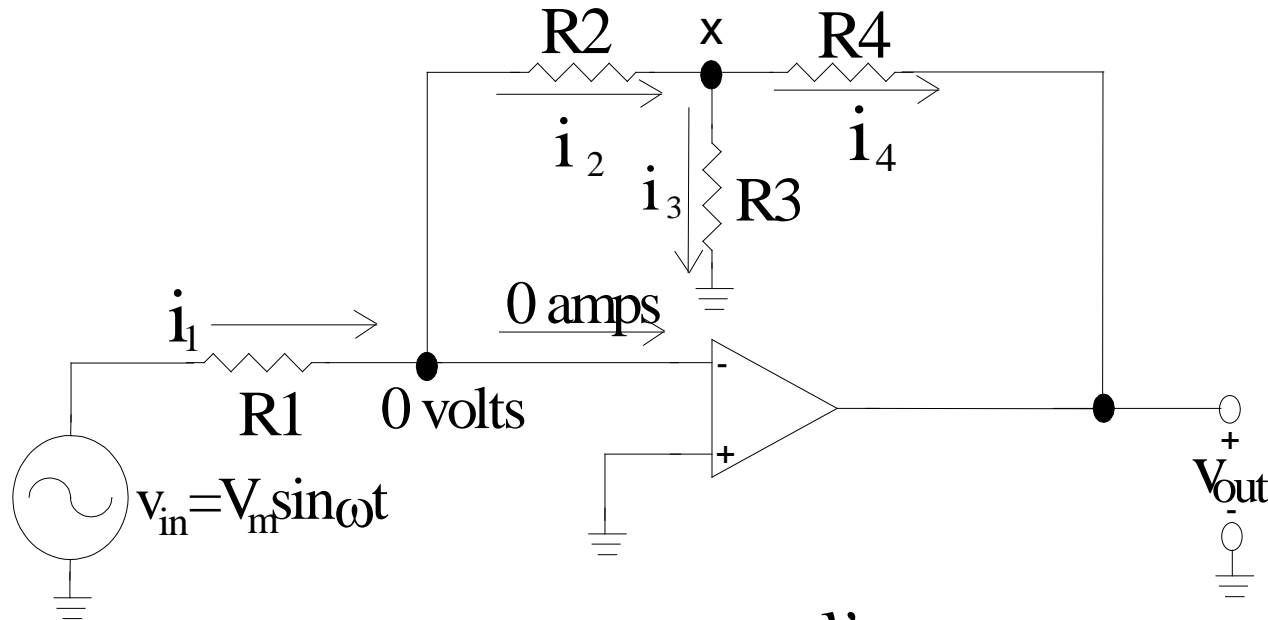

Thus we can see that  $i_1 = i_2 = \frac{v_{in}}{R1}$


We can now determine the voltage

At node 'x' above:

$$v_x = 0 - i_2 R2 = -i_1 R2 = -\frac{v_{in}}{R1} \cdot R2 = -\frac{R2}{R1} \cdot v_{in}$$

# The Operational Amplifier

## The Inverting Amplifier

 


Now we can find the current through  $R3$ ,  $i_3$ :

$$i_3 = \frac{v_x - 0}{R3} = \frac{v_x}{R3} = \left( \frac{-((R2/R1) \cdot v_{in})}{R3} \right) = - \left( \frac{R2}{R1 \times R3} \right) \cdot v_{in}$$

# The Operational Amplifier

## The Inverting Amplifier

 


To find  $i_4$  we use KCL at 'x':  $i_2 - i_3 - i_4 = 0$   
 $\therefore i_4 = i_2 - i_3$

Thus: 
$$i_4 = \left( \frac{v_{in}}{R1} \right) - \left( \left( \frac{-R2}{R1 \times R3} \right) \cdot v_{in} \right) = \frac{v_{in}}{R1} + \frac{R2 \cdot v_{in}}{R1 \cdot R3}$$

# The Operational Amplifier

## The Inverting Amplifier

 


Now we can include  $v_{out}$  in our expressions:

$$\begin{aligned}
 v_{out} &= v_x - i_4 \cdot R4 \\
 &= -\frac{R2}{R1} \cdot v_{in} - \left( \frac{v_{in}}{R1} + \frac{R2 \cdot v_{in}}{R1 \cdot R3} \right) \cdot R4
 \end{aligned}$$

# The Operational Amplifier

## The Inverting Amplifier

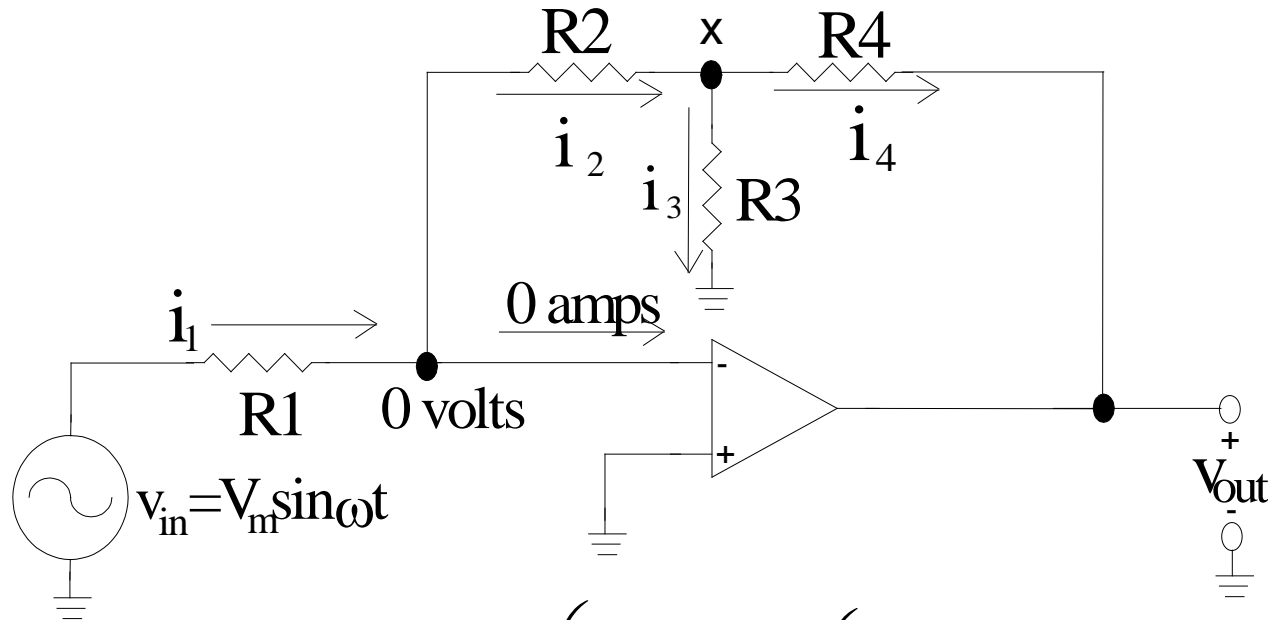


Rearranging: 
$$v_{out} = v_{in} \cdot \left( -\frac{R2}{R1} - \left( \frac{R4}{R1} + \frac{R2 \cdot R4}{R1 \cdot R3} \right) \right)$$

$$\therefore \frac{v_{out}}{v_{in}} = - \left( \frac{R2}{R1} + \frac{R4}{R1} \left( 1 + \frac{R2}{R3} \right) \right) = A_v$$



# The Operational Amplifier

## The Inverting Amplifier

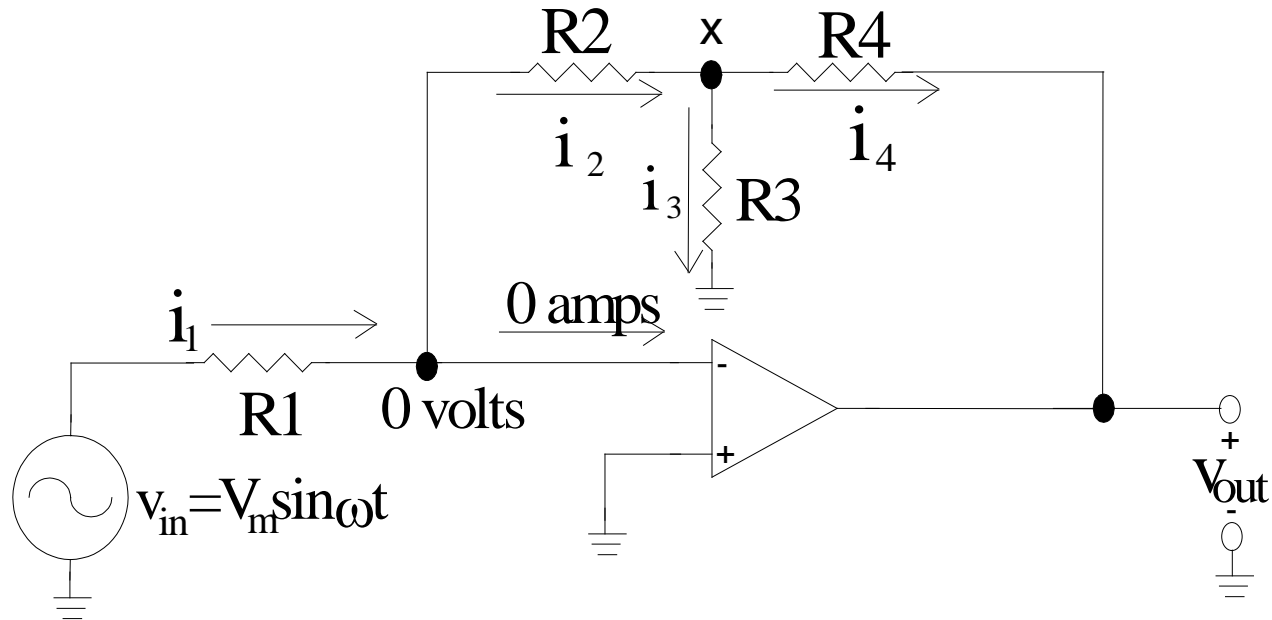


Which can also be expressed as:

$$\frac{v_{out}}{v_{in}} = -\frac{R2}{R1} \left( 1 + \frac{R4}{R2} + \frac{R4}{R3} \right)$$

# The Operational Amplifier


## The Inverting Amplifier

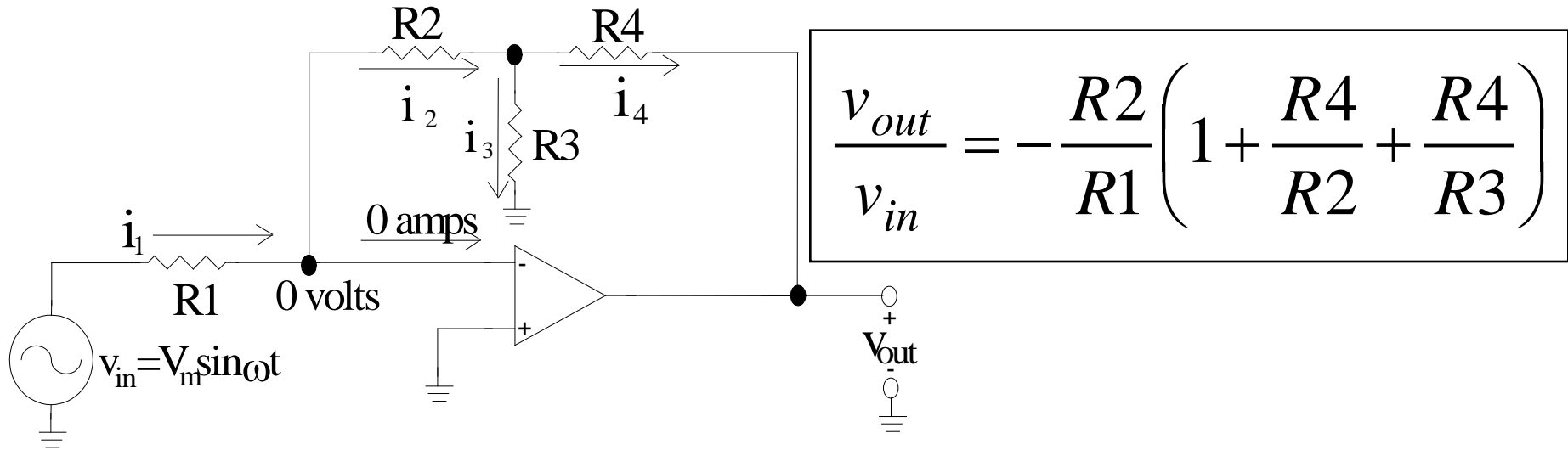

This circuit has the advantage that it can have a large Input resistance and large gain, Consider this next example...

# The Operational Amplifier


## The Inverting Amplifier

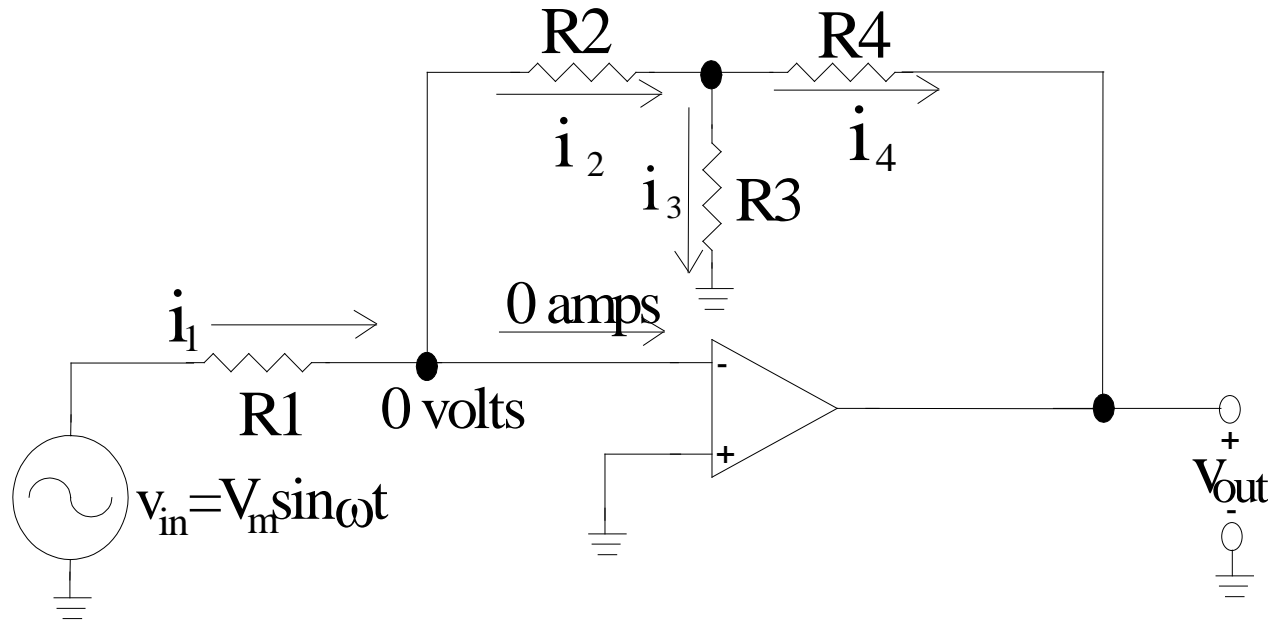

It is specified that we need an amplifier with an Input resistance of  $1 \text{ M}\Omega$  and a gain of approximately  $-100 \text{ Volt / Volt}$  to within 10%. The maximum value of resistance values available is  $1 \text{ M}\Omega$ . Choose values for  $R_1$ ,  $R_2$ ,  $R_3$  &  $R_4$  in the op-amp circuit above to achieve this specification.

# The Operational Amplifier

## The Inverting Amplifier

 


Given that the input resistance is  $1\text{M}\Omega$  we then select  $R1$  to be  $1\text{M}\Omega$  ie:  $R1 = 1\text{M}\Omega$

Since: 
$$\frac{v_{out}}{v_{in}} = -\frac{R2}{R1} \left( 1 + \frac{R4}{R2} + \frac{R4}{R3} \right)$$

Then let  $R2=R1=1\text{M}\Omega$   
ie Ratio  $R2/R1 = 1$

# The Operational Amplifier

## The Inverting Amplifier

 


Now this means that  $R4/R2$  will contribute little to the gain since  $R2$  is  $1\text{M}\Omega$  and this is the largest possible resistor value

We must get our gain from the ratio of  $R4/R3$ .

# The Operational Amplifier


## The Inverting Amplifier

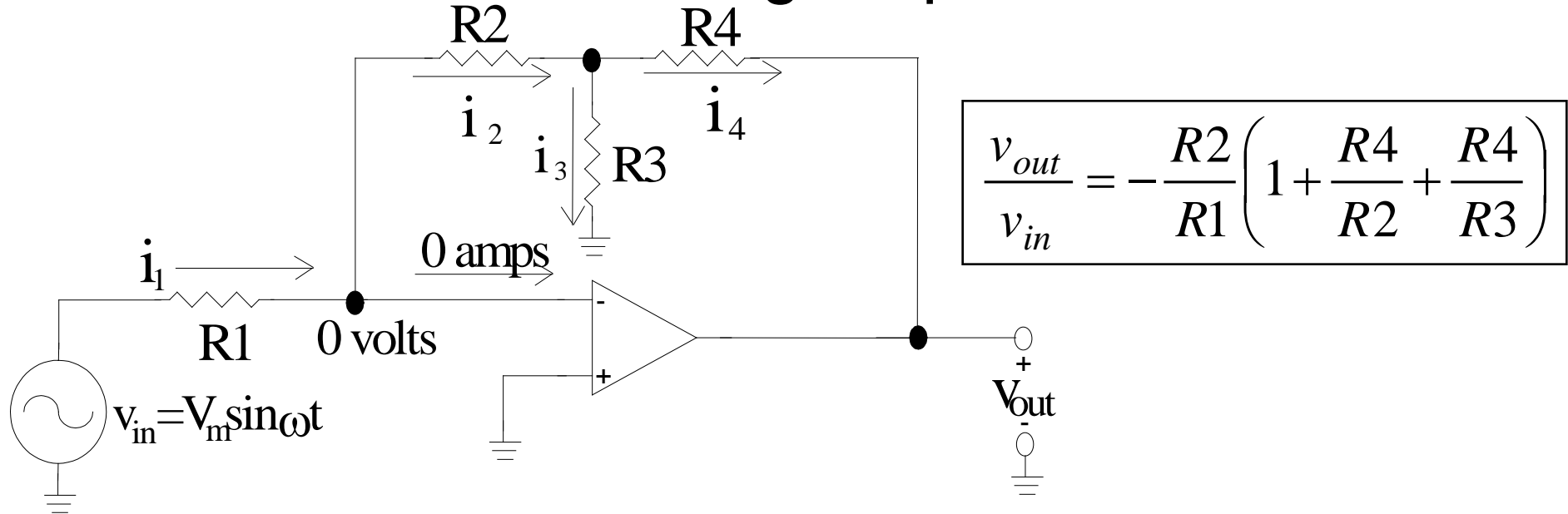

If we choose  $R4$  to be  $1\text{M}\Omega$  and choose  $R3$  to be  $10\text{ k}\Omega$  , then:

$$\frac{v_{out}}{v_{in}} = -\frac{R2}{R1} \left( 1 + \frac{R4}{R2} + \frac{R4}{R3} \right) = -\frac{1}{1} \left( 1 + \frac{1}{1} + \frac{1}{0.01} \right) = -1(1 + 1 + 100) = -102$$

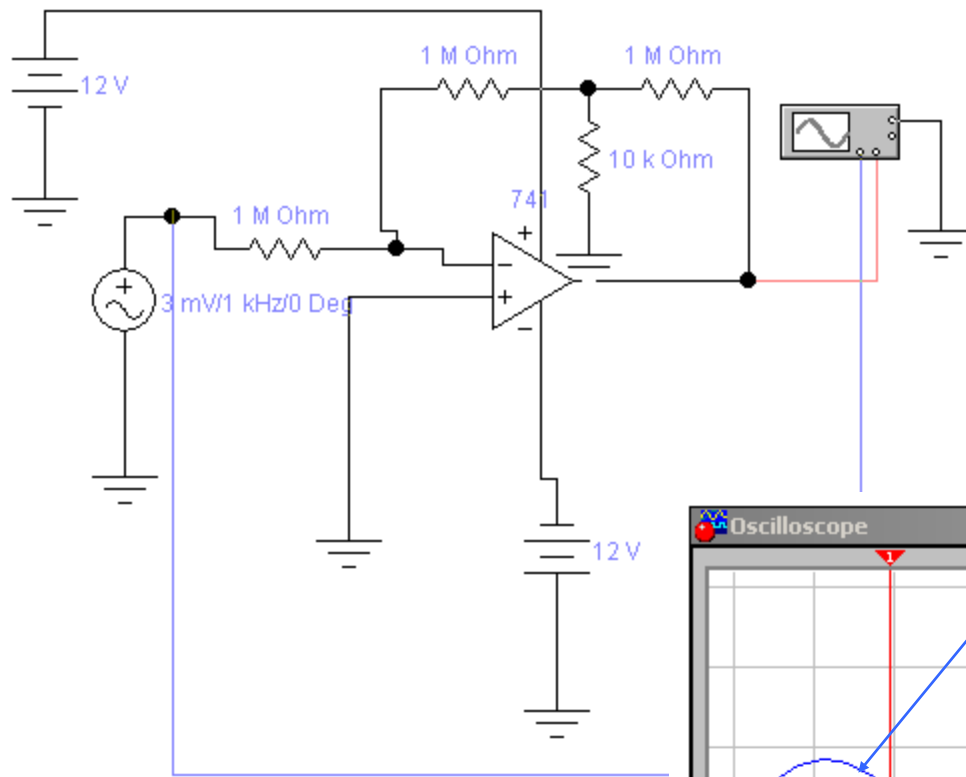
This satisfies the required gain to within 10%



Input, channel A

Output, channel B

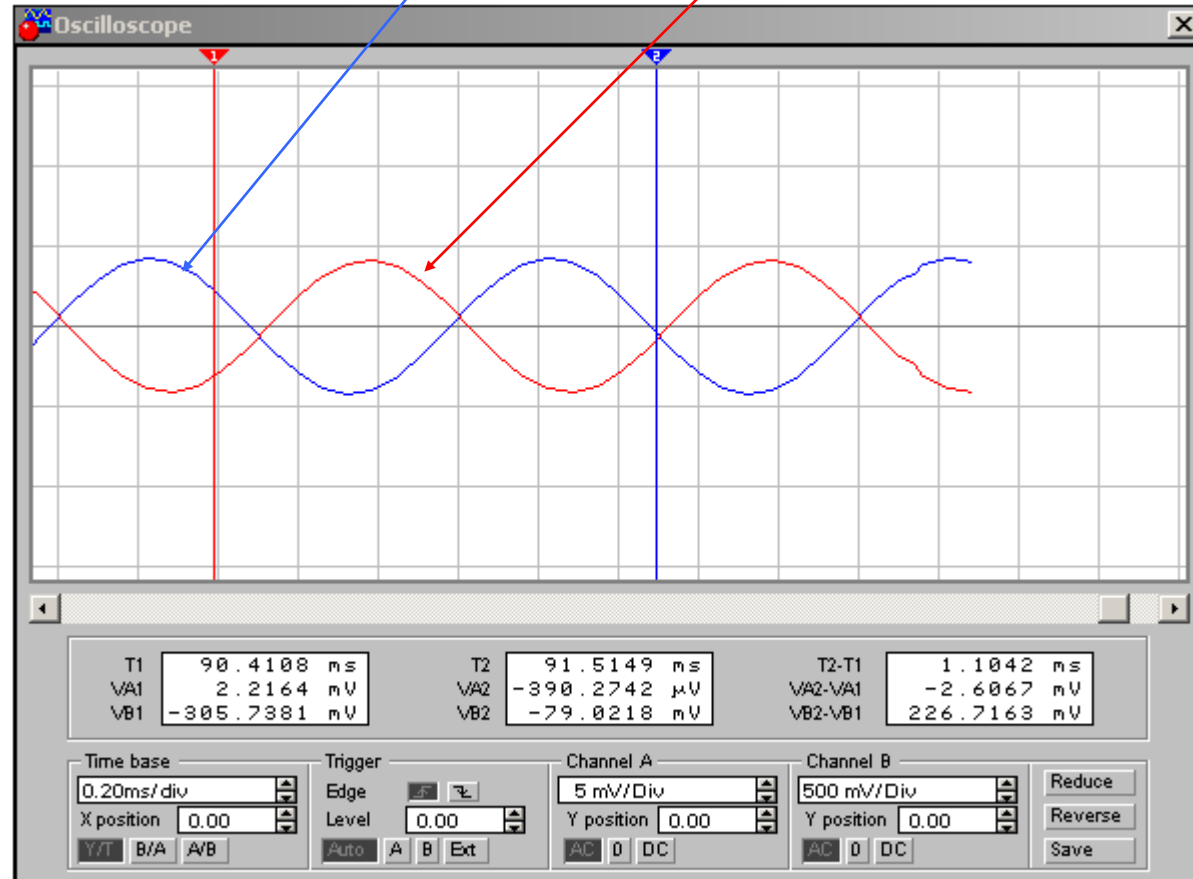Output is on 500mV/div  
Scale whereas  
Input is on 5mV/div  
Scale so amplification  
Is by a factor -100 V/V  
As we can still see  
The sinusoids  
Are 180 degrees out of phase



# The Operational Amplifier

## The Summing Amplifier

Consider this circuit where we  
Have multiple input signals  
With multiple input resistors

Each voltage source 'sees'  
An input resistance equal to  
The value of the input resistor  
For that 'leg'

That is  $v_{s1}$  sees an input resistance  $R_{s1}$


and  $v_{s2}$  sees an input resistance  $R_{s2}$

We want to find an expression for the output  
Voltage in terms of the individual input voltages!

To do this we will apply KCL at the -ve terminal of the op-amp, ie:

$$i_1 + i_2 + \dots + i_N - 0 + i_F = 0$$

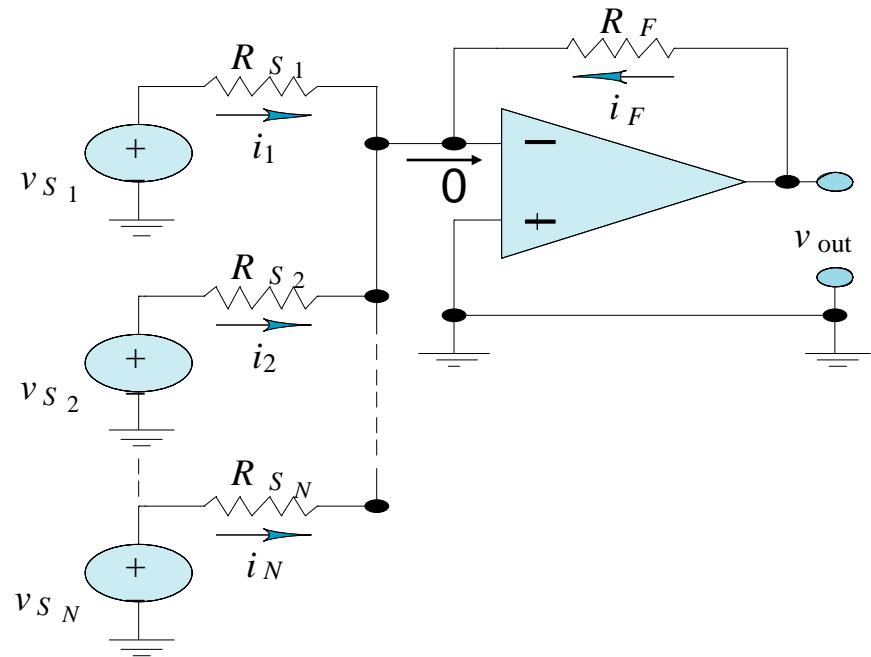Since Ideal, zero current into -ve terminal





# The Operational Amplifier

## The Summing Amplifier

Now the virtual ground forces the –ve Terminal to a 0 V potential.

We use Ohms Law to find the Input currents:


$$i_1 = \frac{v_{S1} - 0}{R_{S1}} = \frac{v_{S1}}{R_{S1}}$$

$$i_2 = \frac{v_{S2} - 0}{R_{S2}} = \frac{v_{S2}}{R_{S2}}$$

⋮

$$i_N = \frac{v_{SN} - 0}{R_{SN}} = \frac{v_{SN}}{R_{SN}}$$
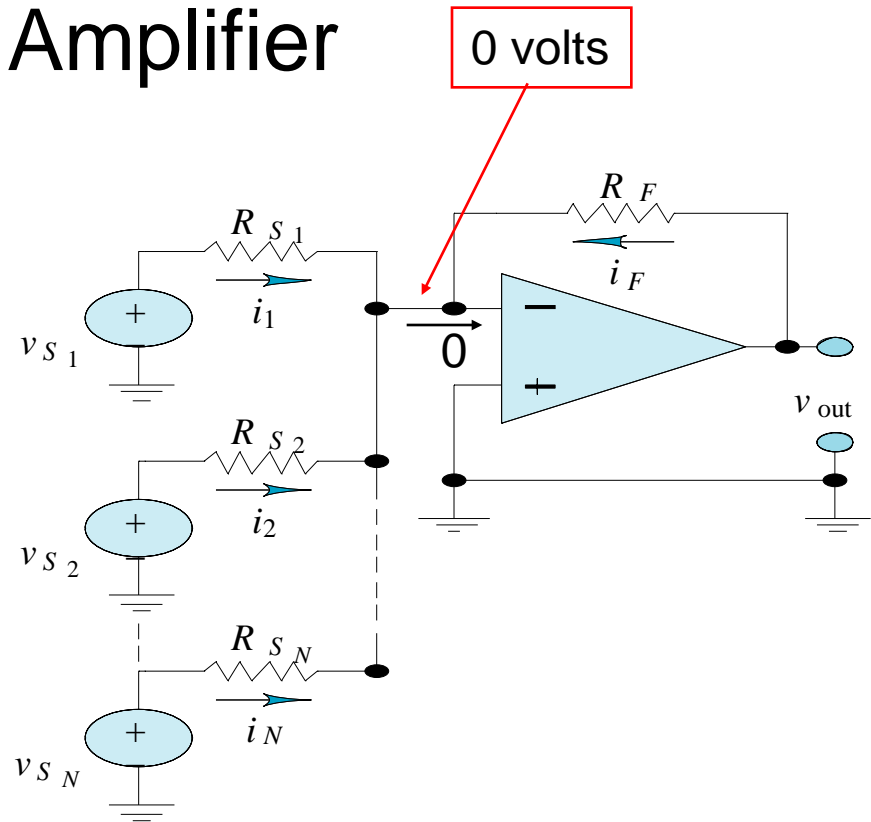
$$\boxed{\text{KCL}} \Rightarrow \frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} + \dots + \frac{v_{SN}}{R_{SN}} + i_F = 0$$



# The Operational Amplifier

## The Summing Amplifier

We can use the same principle  
To calculate the current in  $R_F$ :

$$i_F = \frac{v_{out} - 0}{R_F} = \frac{v_{out}}{R_F}$$

So subbing into KCL equation:

$$\frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} + \dots + \frac{v_{SN}}{R_{SN}} + \frac{v_{out}}{R_F} = 0$$

Rearranging:


$$v_{out} = -R_F \cdot \left( \frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} + \dots + \frac{v_{SN}}{R_{SN}} \right)$$

If we allow all the input resistors to be the same ie:  $R_{S1} = R_{S2} = \dots = R_{SN} = R_S$

Then:

$$v_{out} = -\frac{R_F}{R_S} (v_{S1} + v_{S2} + \dots + v_{SN})$$

That is the SUM!

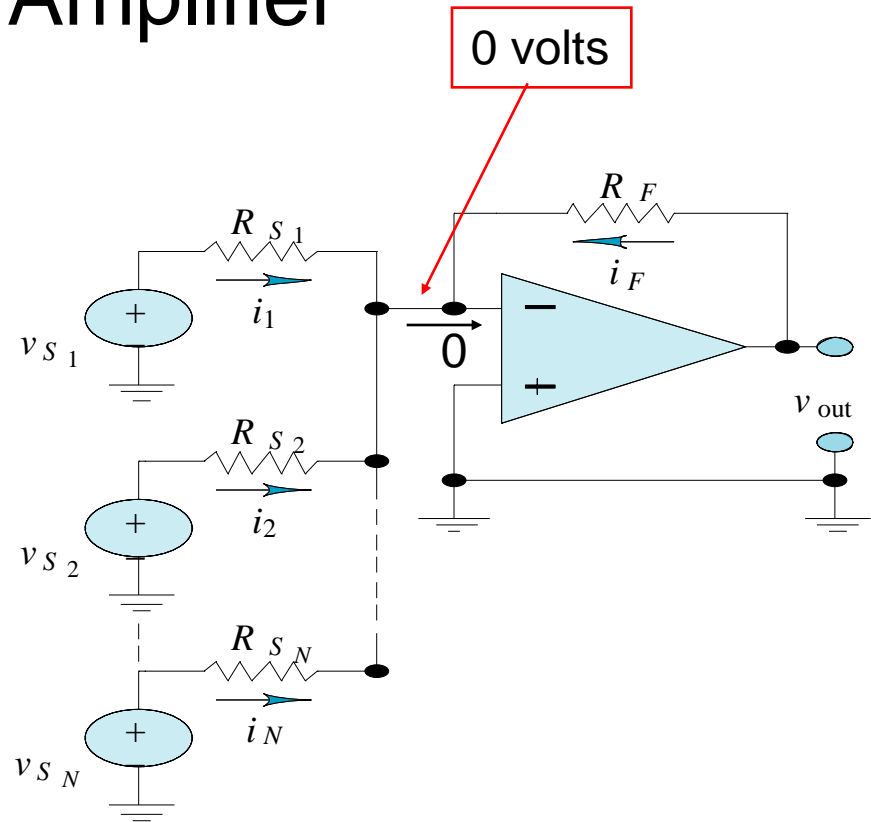

# The Operational Amplifier

## The Summing Amplifier: Example


If  $v_{s1} = +0.6$  volts and  $v_{s2} = -1.4$  volts,  
With  $R_{S1} = 400\text{k}\Omega$  and  $R_{S2} = 100\text{k}\Omega$ ,  
And  $R_F = 200\text{k}\Omega$ , determine the output  
Voltage.

Answer:

$$v_{out} = -R_F \cdot \left( \frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} \right)$$

Subbing values:
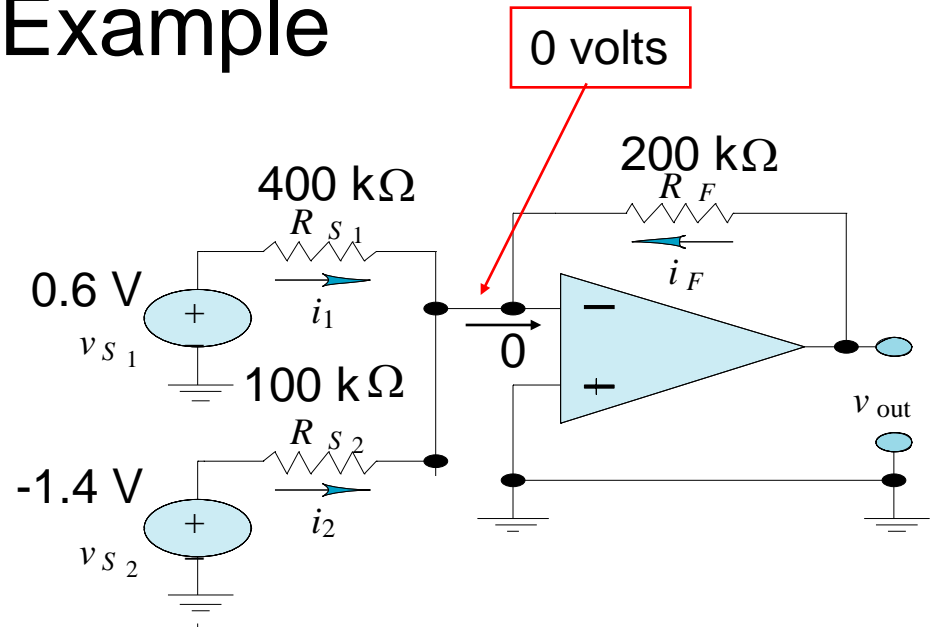
$$\begin{aligned} v_{out} &= -(200 \text{ k}\Omega) \cdot \left( \frac{0.6 \text{ volts}}{400 \text{ k}\Omega} + \frac{-1.4 \text{ volts}}{100 \text{ k}\Omega} \right) \\ &= -\left( \frac{200}{100} \right) \cdot \left( \frac{6}{40} - \frac{7 \times 8}{5 \times 8} \right) = -2 \cdot \left( -\frac{50}{40} \right) = +2.5 \text{ volts} \end{aligned}$$



# The Operational Amplifier

## The Non-Inverting Amplifier

We can also put the op-amp in an non-inverting configuration which has Infinite input resistance looking into the +ve terminal and the input will be Inphase with the output

We want to find an expression for  $v_{out}$ :

Since zero current flows into the -ve terminal

We can write:


$$i_S = i_F$$

And the virtual short circuit

Means that:  $v_S = v^+ = v^-$

So we can use Ohms Law:

$$i_S = \frac{v_S}{R_S}$$

 

# The Operational Amplifier

## The Non-Inverting Amplifier

Thus we can write using KVL:  $v_{out} - i_F R_F - i_S R_S = 0$

Subbing for  $i_S$  and rearranging:


$$v_{out} = i_S (R_F + R_S) \quad \text{Since} \quad i_S = i_F$$

Which means that:

$$i_S = \frac{v_{out}}{(R_F + R_S)} = \frac{v_S}{R_S}$$

Thus:
 
$$\begin{aligned} v_{out} &= \frac{v_S}{R_S} (R_F + R_S) \\ &= \left( 1 + \frac{R_F}{R_S} \right) \cdot v_S \end{aligned}$$




# The Operational Amplifier Example

If the input voltage,  $v_S$ , is 2 volts DC and the supply rails are +15 volts and -15 volts respectively (not Shown) what is the output Voltage  $v_{out}$  equal to when  $R_S=10\text{ k}\Omega$  and  $R_F=20\text{ k}\Omega$ ?

Answer:
 
$$\begin{aligned} v_{out} &= \left( 1 + \frac{R_F}{R_S} \right) \cdot v_S \\ &= \left( 1 + \frac{20}{10} \right) \cdot (2) \\ &= (3) \cdot (2) \\ &= +6 \text{ volts} \end{aligned}$$




# The Operational Amplifier Example

If the input voltage,  $v_S$ , is  $(3\sqrt{2})\sin(2000 \times \pi \times t)$  volts and the supply rails are +15 volts and -15 volts DC respectively (not shown) what is the output Voltage  $v_{out}$  equal to when  $R_S=10 \text{ k}\Omega$  and  $R_F=15 \text{ k}\Omega$ ?

Answer:

$$v_{out} = \left(1 + \frac{R_F}{R_S}\right) \cdot v_S$$

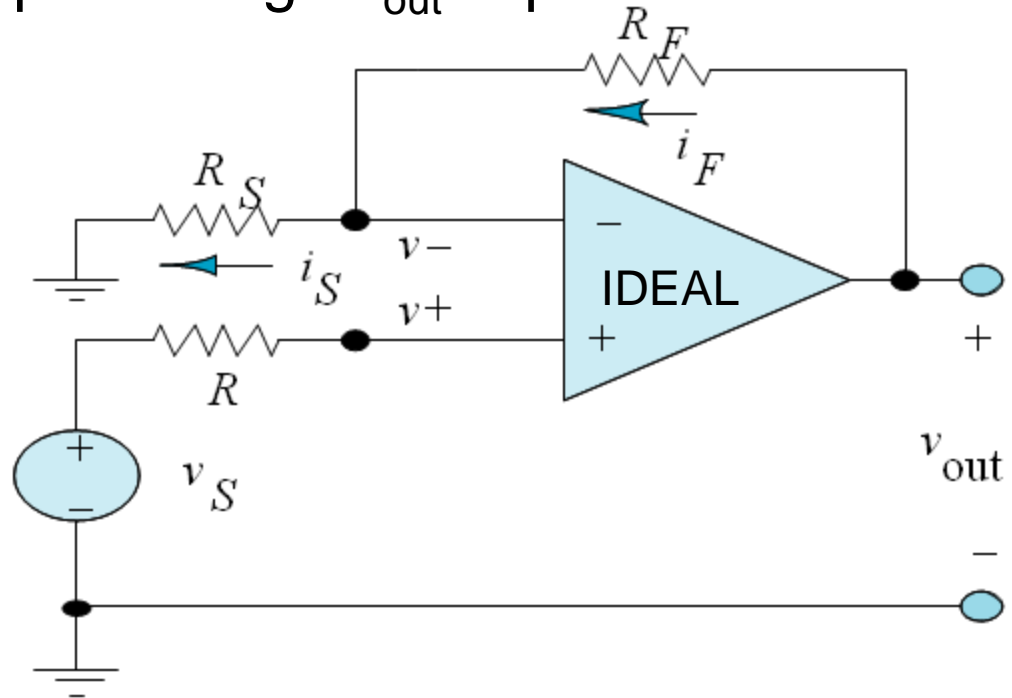
$$= \left(1 + \frac{15}{10}\right) \cdot (3\sqrt{2} \sin(2000 \times \pi \times t))$$


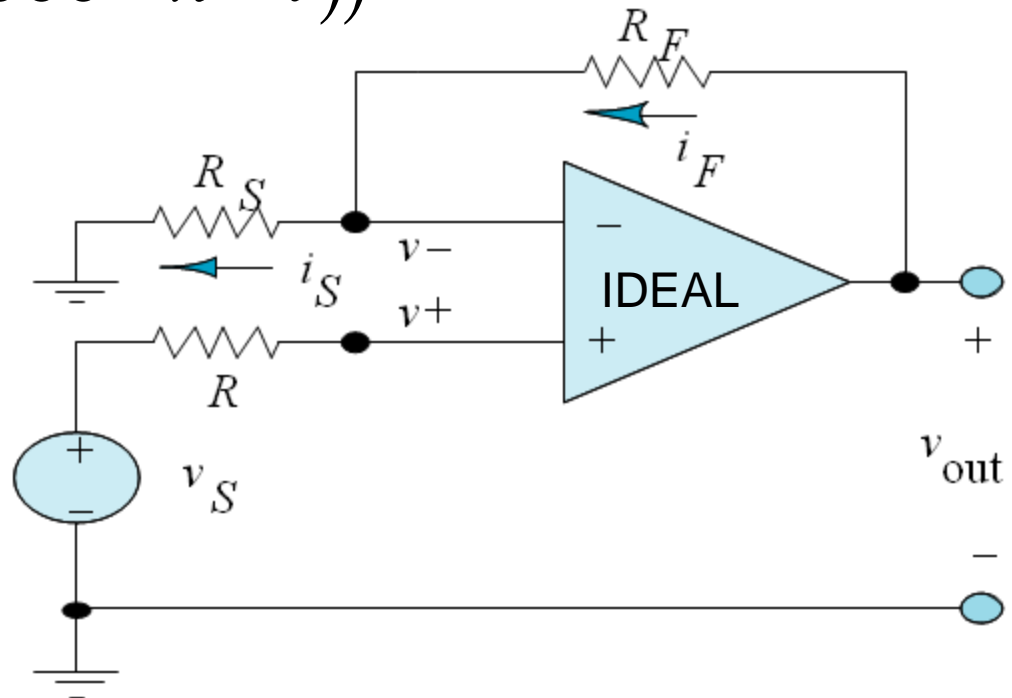
# The Operational Amplifier Example


$$v_{out} = \left(\frac{5}{2}\right) \cdot \left(3\sqrt{2} \sin(2000 \times \pi \times t)\right)$$

$$= \left(\frac{15}{\sqrt{2}}\right) \cdot \left(\sin(2000 \times \pi \times t)\right)$$






# Non-Inverting Op-Amp

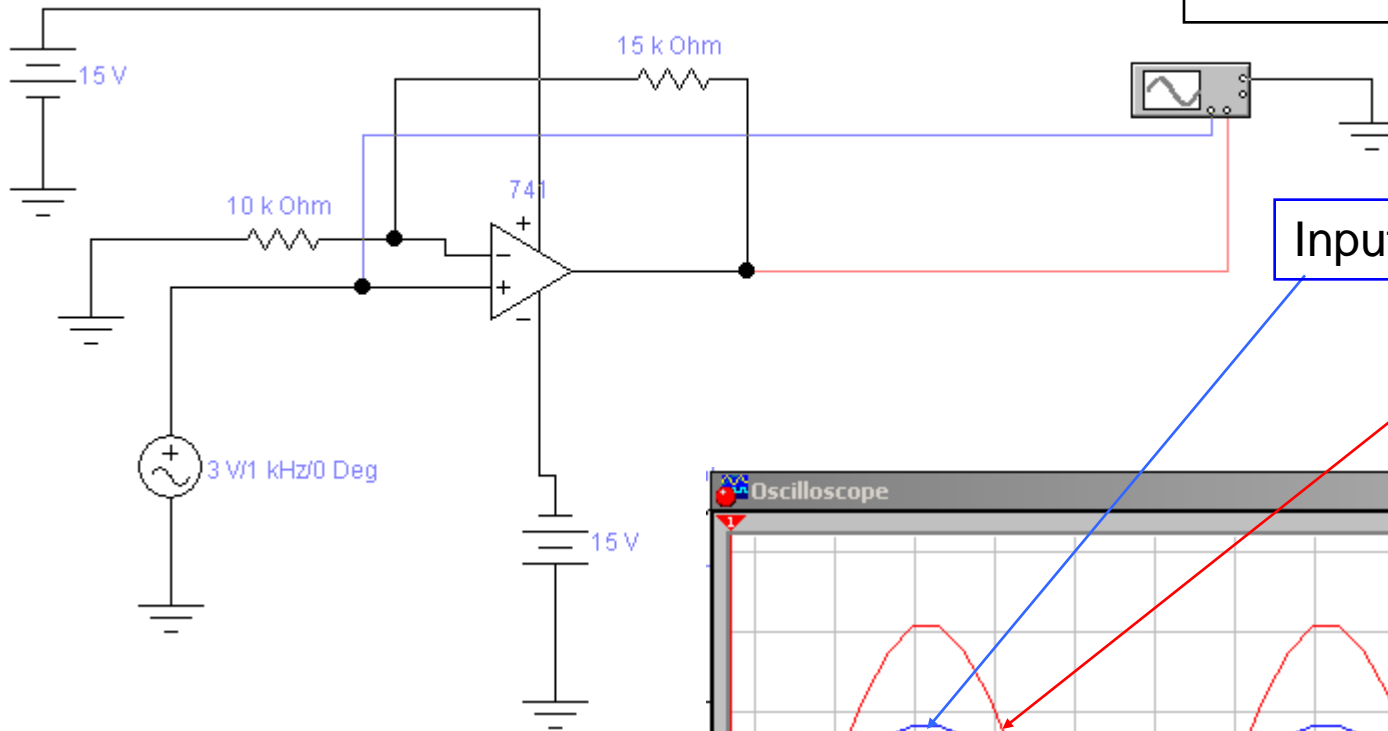

Input, channel A

Output, channel B

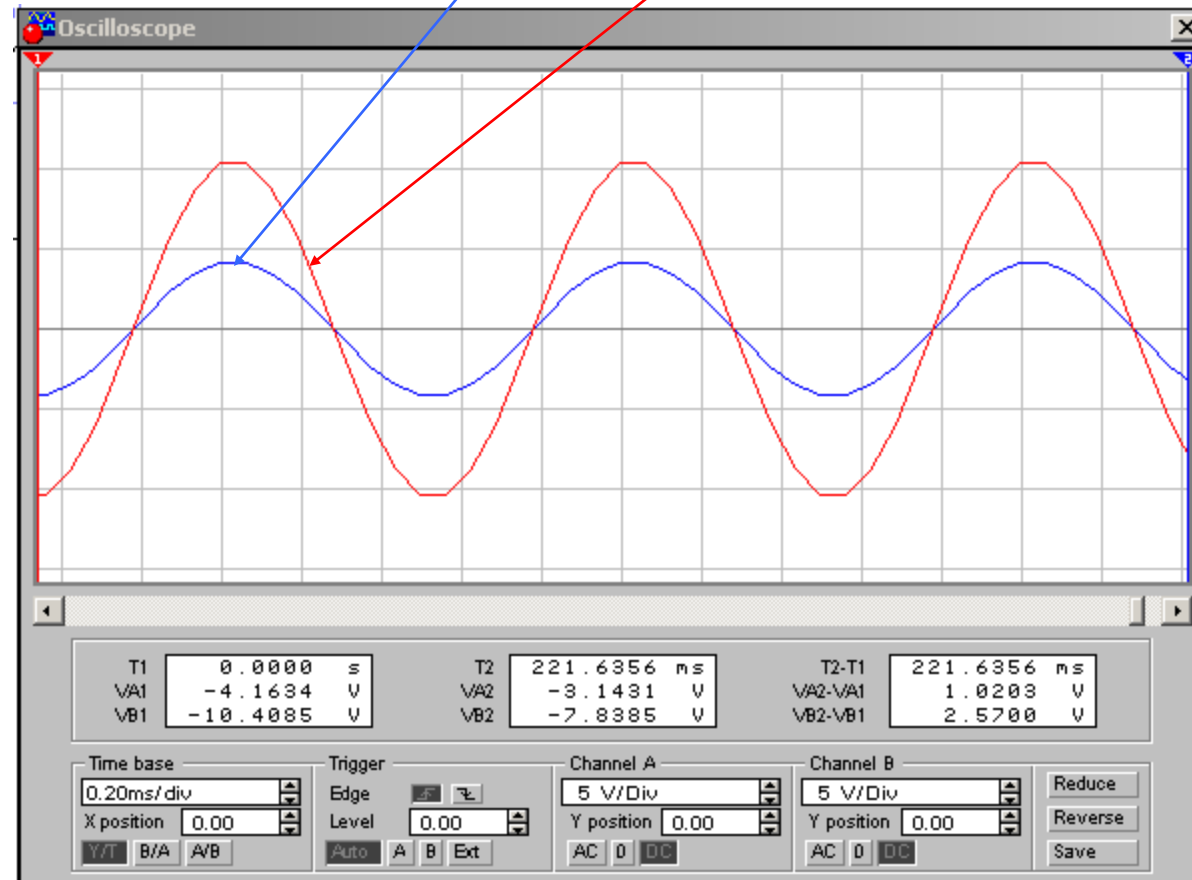Clearly, input and Output are in-phase  
And the output is 2.5 times the input



# The Operational Amplifier

## The Voltage Follower or Buffer

Another configuration close to the non-inverting configuration is the Voltage follower:


Since the op-amp is ideal  
There is zero current into  
The +ve terminal and no  
Need for R, which can be  
Modeled as the internal  
Resistance of the source,  $v_s$

The virtual short  
Circuit between the  
+ve and -ve terminals  
Means that:

$$v_{out} = v_s$$

And we have a high resistance  
Input with low resistance output  
With the same voltage at the output  
as the source

- Hence the term voltage follower!

 

# Level Shifter

This provides a method to  
Shift the DC level of a circuit  
Needed , for example, to remove DC!

We want to find  $v_{out}$ :

First suppress  $v_S$ :


$$v_S = 0 \longrightarrow v_{out} = \left(1 + \frac{R_F}{R_S}\right) V_{ref}$$

Then suppress  $V_{ref}$ :

$$V_{ref} = 0 \longrightarrow v_{out} = -\frac{R_F}{R_S} v_S$$

Now using Superposition we add them together to get:
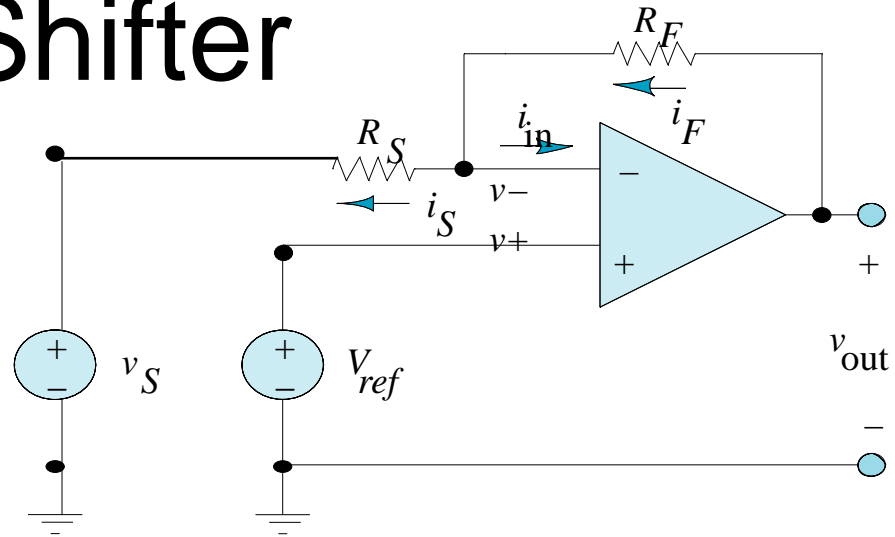
$$v_{out} = -\frac{R_F}{R_S} v_S + \left(1 + \frac{R_F}{R_S}\right) V_{ref}$$




# Example

Given:  $v_S = 1.8 + 0.1\cos(\omega t)$ ;  $R_F = 220k \ \Omega$ ;  $R_S = 10k \ \Omega$ ;

Find:  $V_{ref}$  to remove the DC bias

Solution:
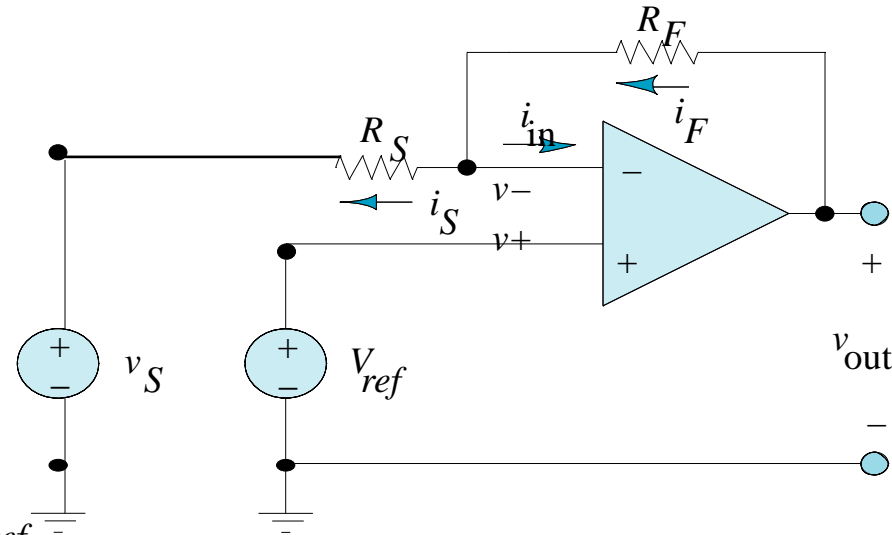
$$\begin{aligned} v_{out} &= -\frac{R_F}{R_S} [1.8 + 0.1\cos(\omega t)] + \left(1 + \frac{R_F}{R_S}\right) V_{ref} \\ &= -\frac{R_F}{R_S} 0.1\cos(\omega t) - \frac{R_F}{R_S} (1.8) + \left(1 + \frac{R_F}{R_S}\right) V_{ref} \end{aligned}$$



Removing the sinusoid and setting the DC component to equal zero:


$$-\frac{R_F}{R_S} (1.8) + \left(1 + \frac{R_F}{R_S}\right) V_{ref} = 0 \quad \Rightarrow \quad V_{ref} = 1.72 \text{ V}$$

# Example

$$v_s = 100 \sin 100t$$


Determine the voltage  $v_{int}$  and  $v_{out}$

Determine the current  $i_s$  and  $i_F$

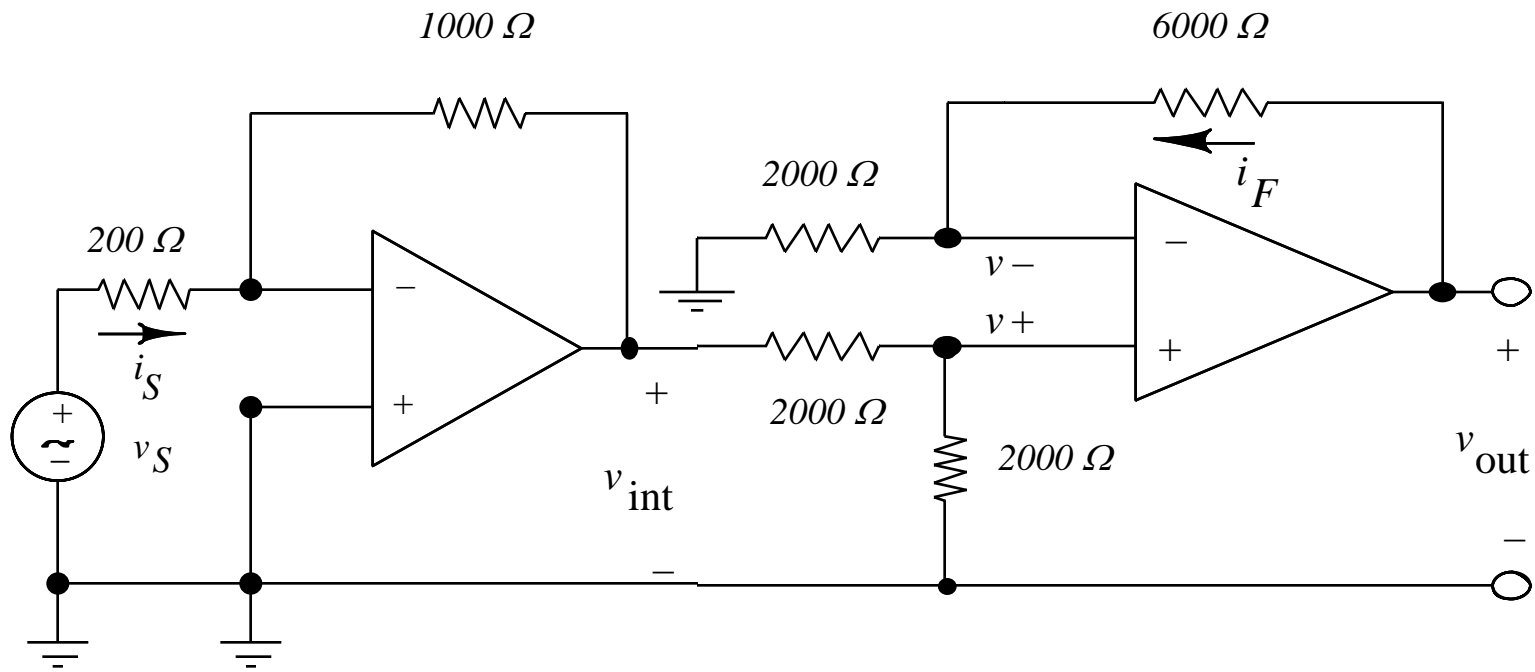
 
# Solution

- Since this is a cascaded amplifier circuit, treat each stage as individual (just as we did with the Voltage follower used as a BUFFER)
- The first stage is an inverting amplifier:



$$\begin{aligned}\text{Thus: } v_{int} &= -\frac{R_F}{R_S} v_S = -\frac{1000}{200} v_S \\ &= -5v_S = -5 \times 100 \sin(100t) \\ &= -500 \sin(100t)\end{aligned}$$

The current  $i_S$  is then:

$$i_S = \frac{v_S}{R_S} = \frac{100 \sin(100t)}{200} = 0.5 \sin(100t)$$


Due to the virtual ground

# Solution

The next stage is a resistor network, basically dividing the output of the Inverting amplifier by 2 and presenting it to the non-inverting amplifier:

Here we have:

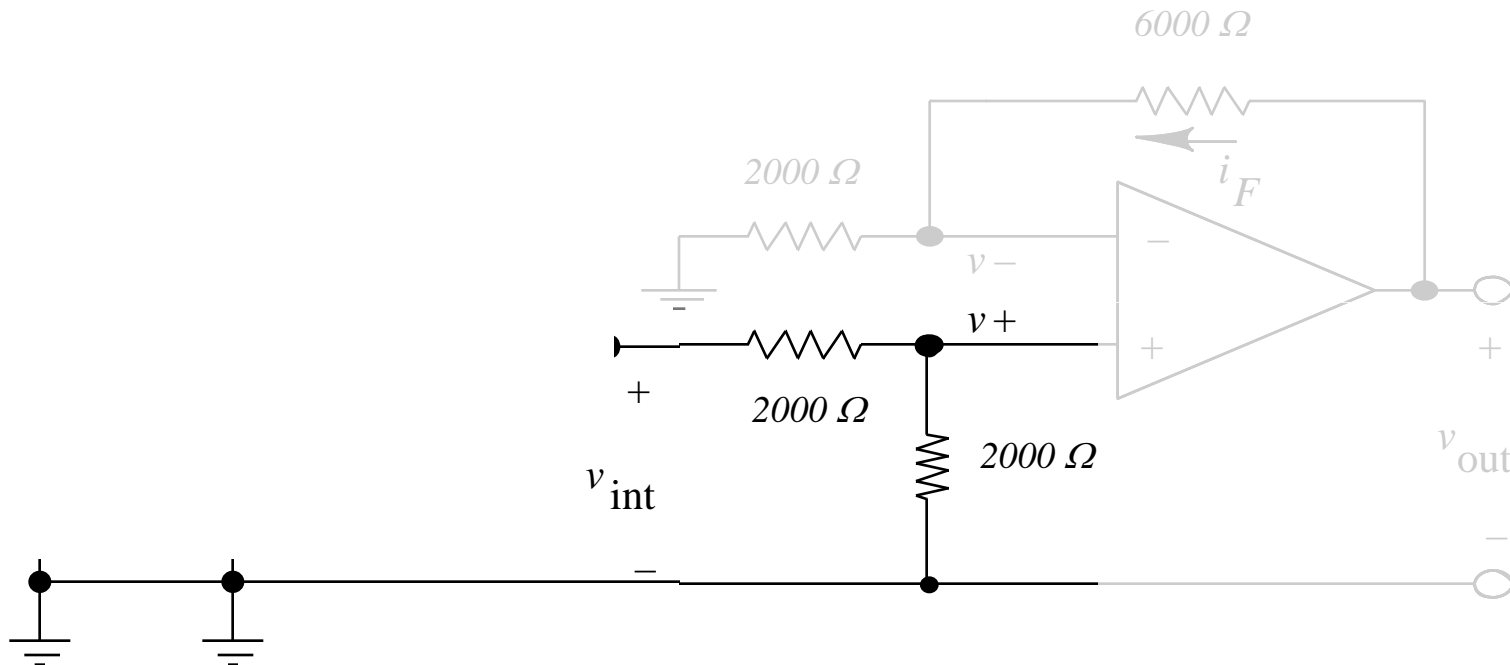
$$v^+ = \left( \frac{2000}{4000} \right) v_{\text{int}} = 0.5 \times v_{\text{int}} = -250 \sin(100t)$$


 
# Solution

The next stage is the non-inverting amplifier where:

$$\begin{aligned} v_{out} &= \left(1 + \frac{R_F}{R_S}\right) v^+ = \left(1 + \frac{6000}{2000}\right) v^+ = 4v^+ \\ &= -1000 \sin(100t) \end{aligned}$$






# Solution

And we can then calculate  $i_F$  as:

$$i_F = \frac{v_{out} - v^-}{R_F} = \frac{v_{out} - v^+}{R_F} = \frac{-1000 \sin(100t) - (-250 \sin(100t))}{6000} = \frac{-750 \sin(100t)}{6000}$$

$$= -0.125 \sin(100t)$$

 


# Differential Amplifier

This is a difference amplifier, it will amplify the difference between two voltage signals

We want to get an expression for  $v_{\text{out}}$ :

To do this we will use superposition

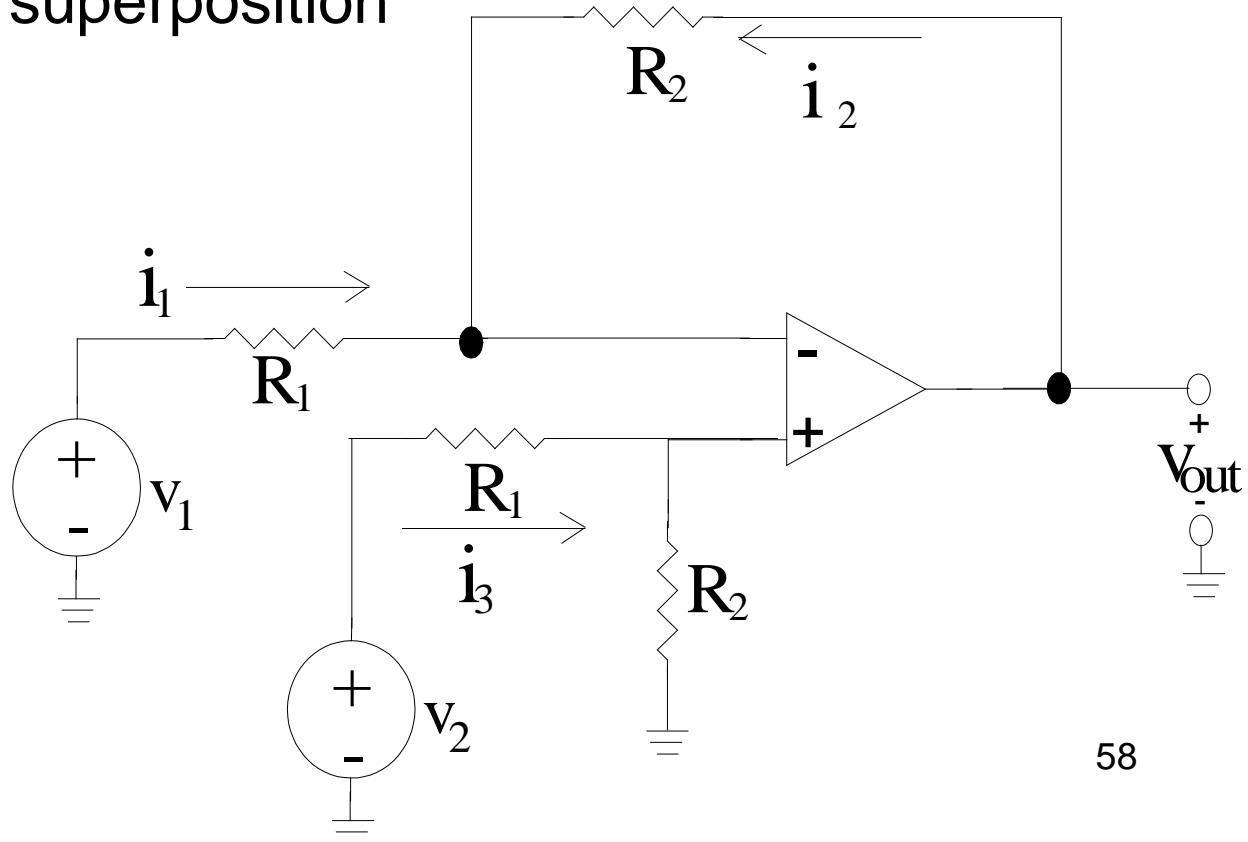


# Differential Amplifier

First we suppress  $v_2$  and calculate the output voltage  $v_{o1}$ :

This circuit is simply an inverting amplifier as no  
Current flows in the bottom two resistors so we  
Have a virtual ground, ie:

$$v_{o1} = -\frac{R_2}{R_1} v_1$$

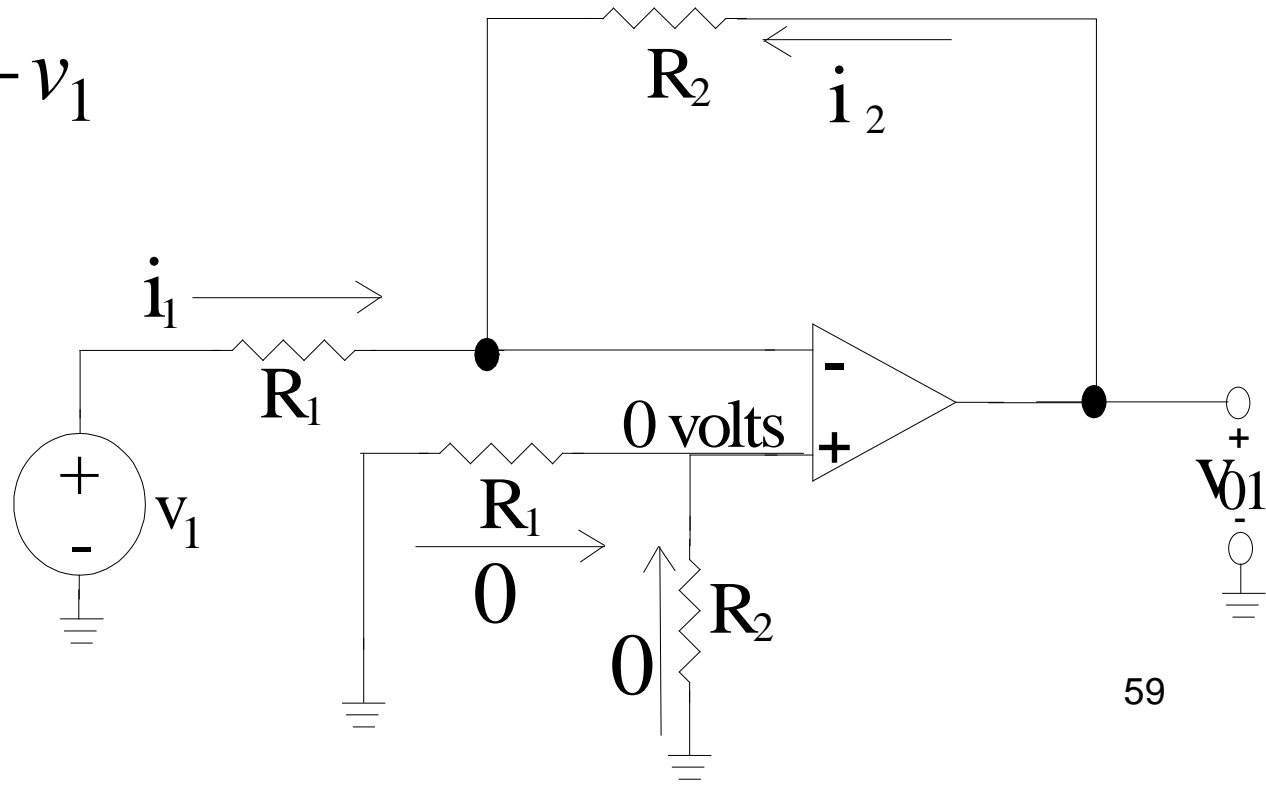


# Differential Amplifier

Now we suppress  $v_1$  and calculate the output voltage  $v_{o2}$ :

This circuit is simply an non-inverting amplifier with a Voltage divider on the input signal:

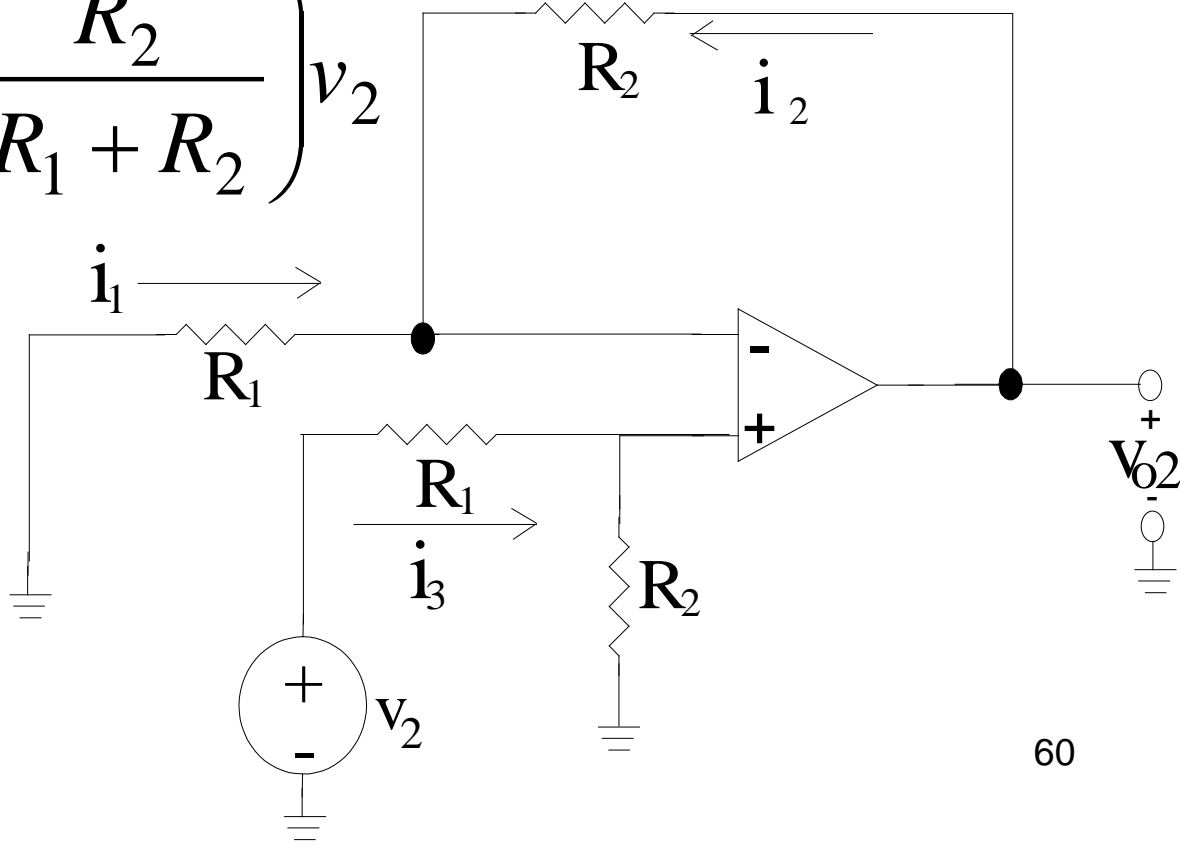
$$v_{o2} = \left(1 + \frac{R_2}{R_1}\right) \cdot \left(\frac{R_2}{R_1 + R_2}\right) v_2$$


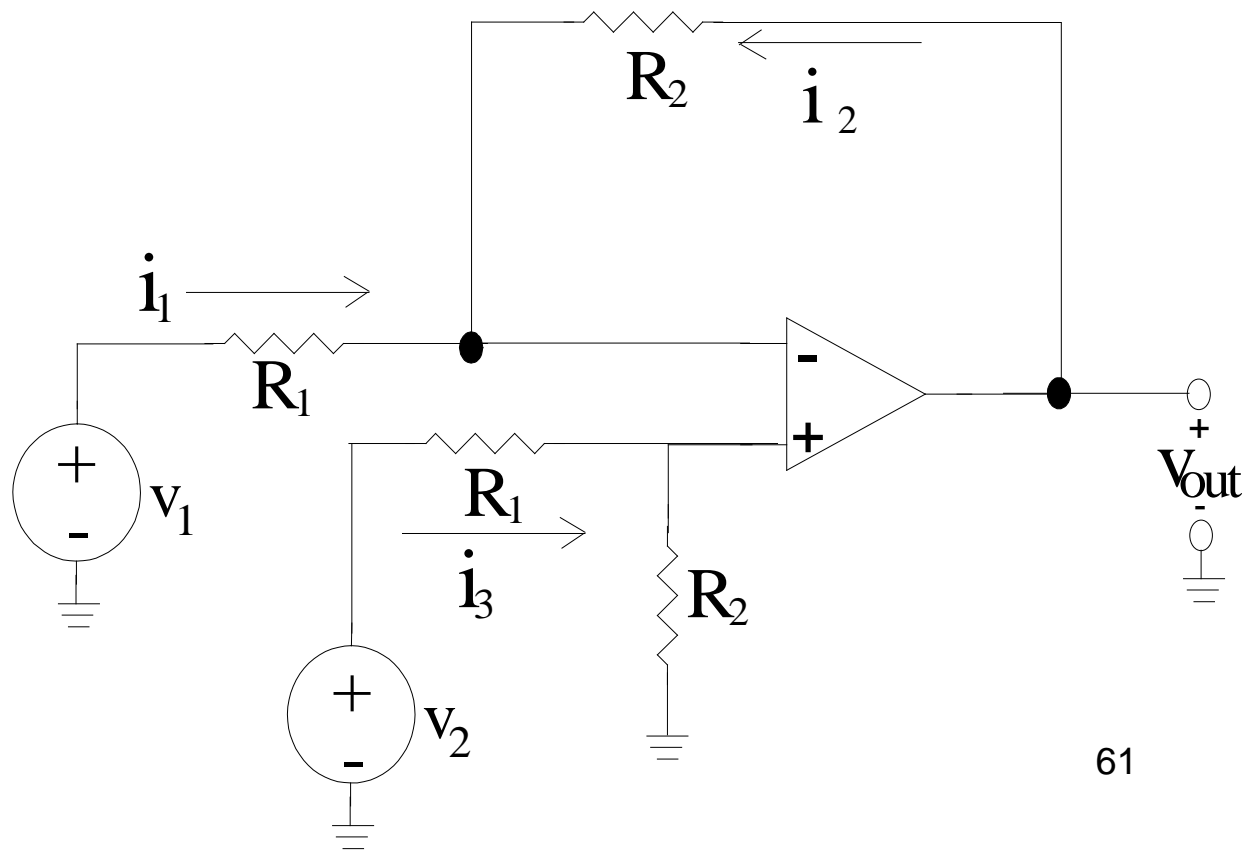
# Differential Amplifier

Adding  $v_{01}$  and  $v_{02}$  to get  $v_{out}$ :

$$v_{out} = v_{01} + v_{02} = -\frac{R_2}{R_1} v_1 + \left(1 + \frac{R_2}{R_1}\right) \cdot \left(\frac{R_2}{R_1 + R_2}\right) v_2$$




# Differential Amplifier

Rearranging gives:

$$\begin{aligned} v_{out} &= -\frac{R_2}{R_1} v_1 + \left( \frac{R_1 + R_2}{R_1} \right) \cdot \left( \frac{R_2}{R_1 + R_2} \right) v_2 \\ &= -\frac{R_2}{R_1} v_1 + \frac{R_2}{R_1} v_2 \end{aligned}$$

$$\therefore v_{out} = \frac{R_2}{R_1} (v_2 - v_1)$$

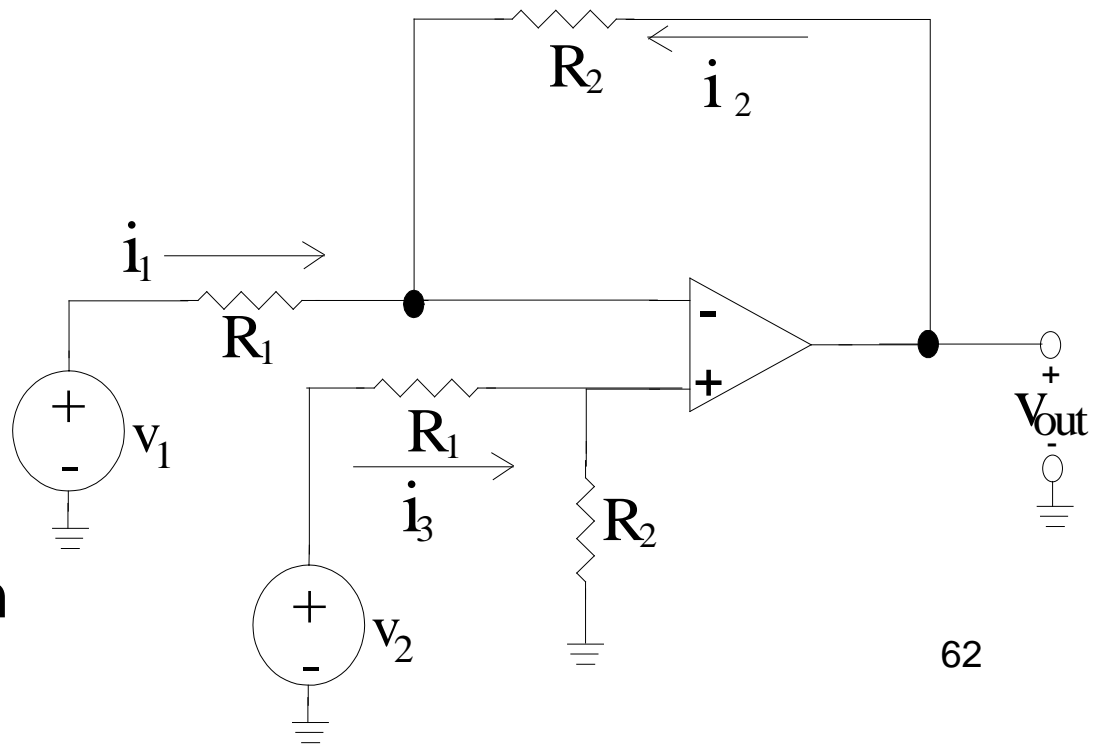
Which amplifies the  
Difference voltage between  
 $v_2$  and  $v_1$ !



# Differential Amplifier
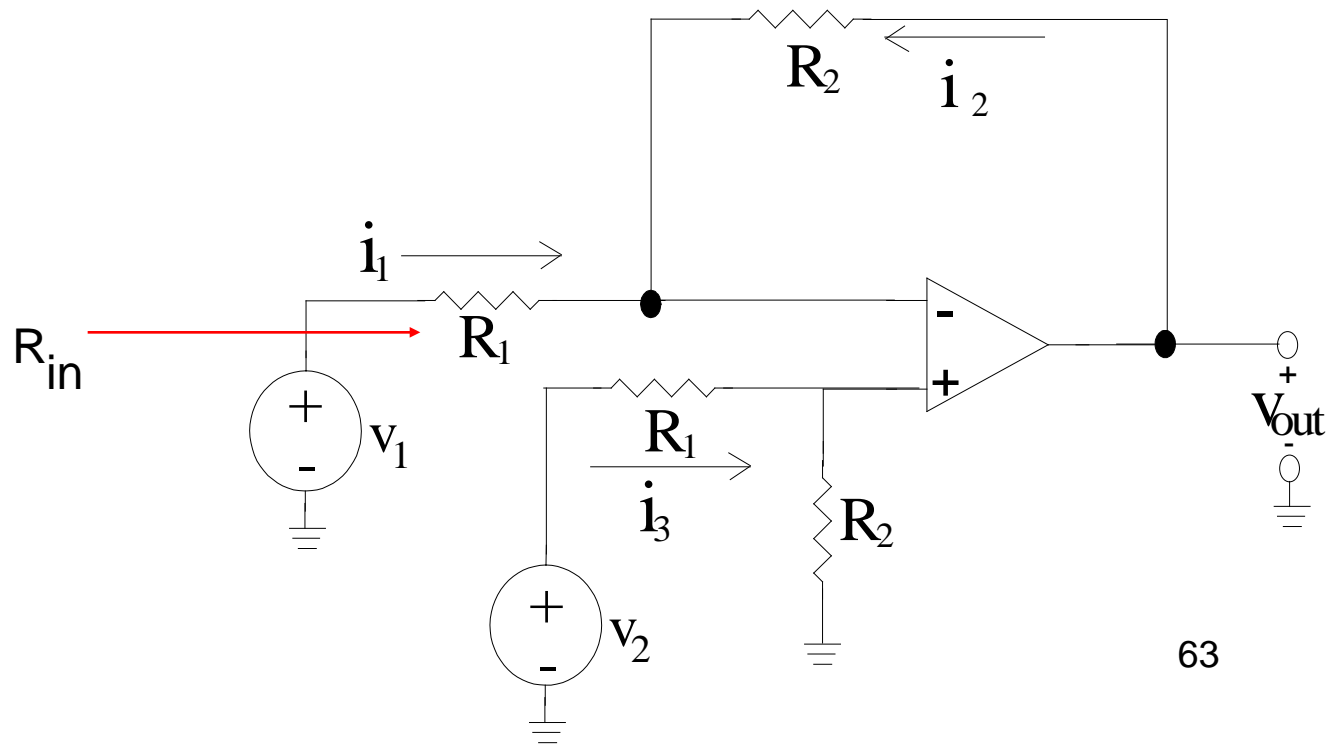
## Input Differential Resistance

If we want to calculate the input resistance seen from a Differential signal connected between the difference Inputs  $v_1$  and  $v_2$ , then we can draw an equivalent circuit And calculate the input differential resistance




# Differential Amplifier

## Input Differential Resistance

Using KVL on the input loop and noting that the Virtual short circuit causes the +ve and -ve Terminals to have the same voltage  $v'$ :

$$\begin{aligned}v_2 - v_1 &= iR_1 + 0 + iR_1 \\ &= 2iR_1\end{aligned}$$
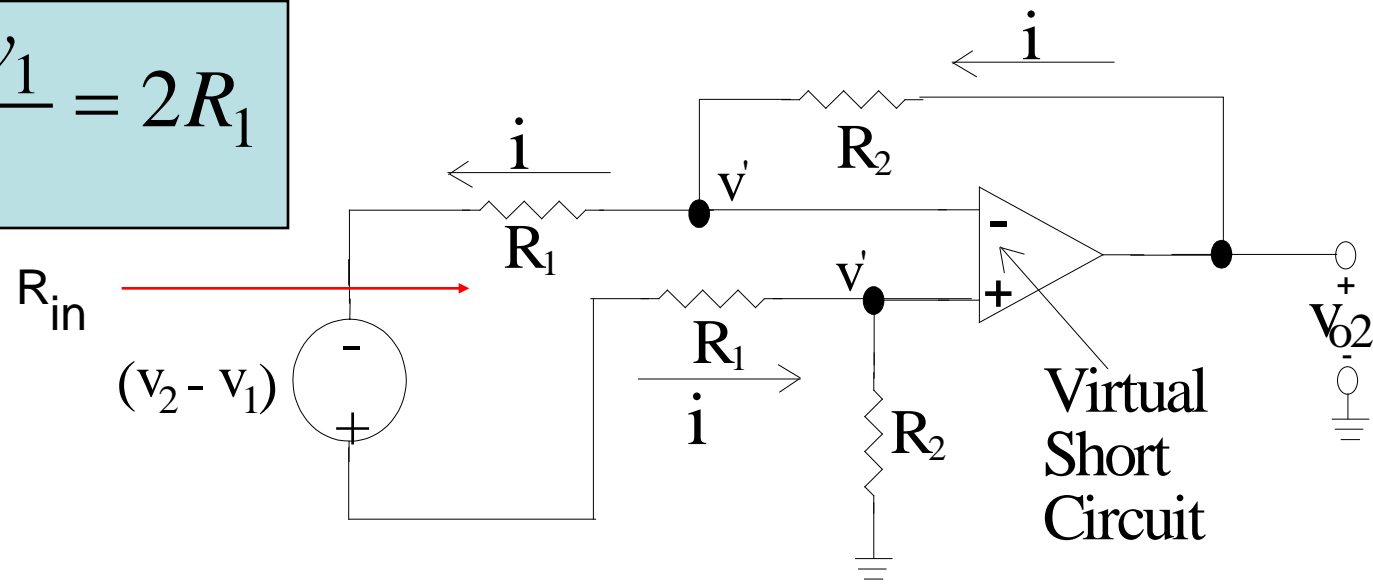
$$\therefore R_{in} \equiv \frac{v_2 - v_1}{i} = 2R_1$$





 
# Instrumentation Amplifier

A alternate differential Amplifier is called an Instrumentation amplifier  
And its advantage is  
That it has infinite  
Differential input resistance

Thus it does not 'load' the  
Signal sources its connected  
Too (draws no current)



# Instrumentation Amplifier

An analysis of the circuit


Would reveal that:

$$v_{out} = \frac{R_F}{R} (v'_a - v'_b) \quad \text{Since output Stage is simply The Difference Amplifier we just Analysed!}$$

also 
$$v'_a = \left(1 + \frac{R_2}{R_1/2}\right) v_a$$

and 
$$v'_b = \left(1 + \frac{R_2}{R_1/2}\right) v_b$$

 
$$\therefore v_{out} = \frac{R_F}{R} \left(1 + \frac{R_2}{R_1/2}\right) (v_a - v_b) = \frac{R_F}{R} \left(1 + \frac{2R_2}{R_1}\right) (v_a - v_b)$$



# Digital to Analog Converters

- Our next topic will be digital circuits
- It should be of interest how we convert a digital signal to analog and vice-a-versa
- First we will consider some simple Digital to analog structures!
- We use D/A or DAC as abbreviations for these devices
- They are available in specialised 'chips' and also can be built in to DSP boards as well (eg Systems on a Chip (SOC))!

# Digital to Analog Converters

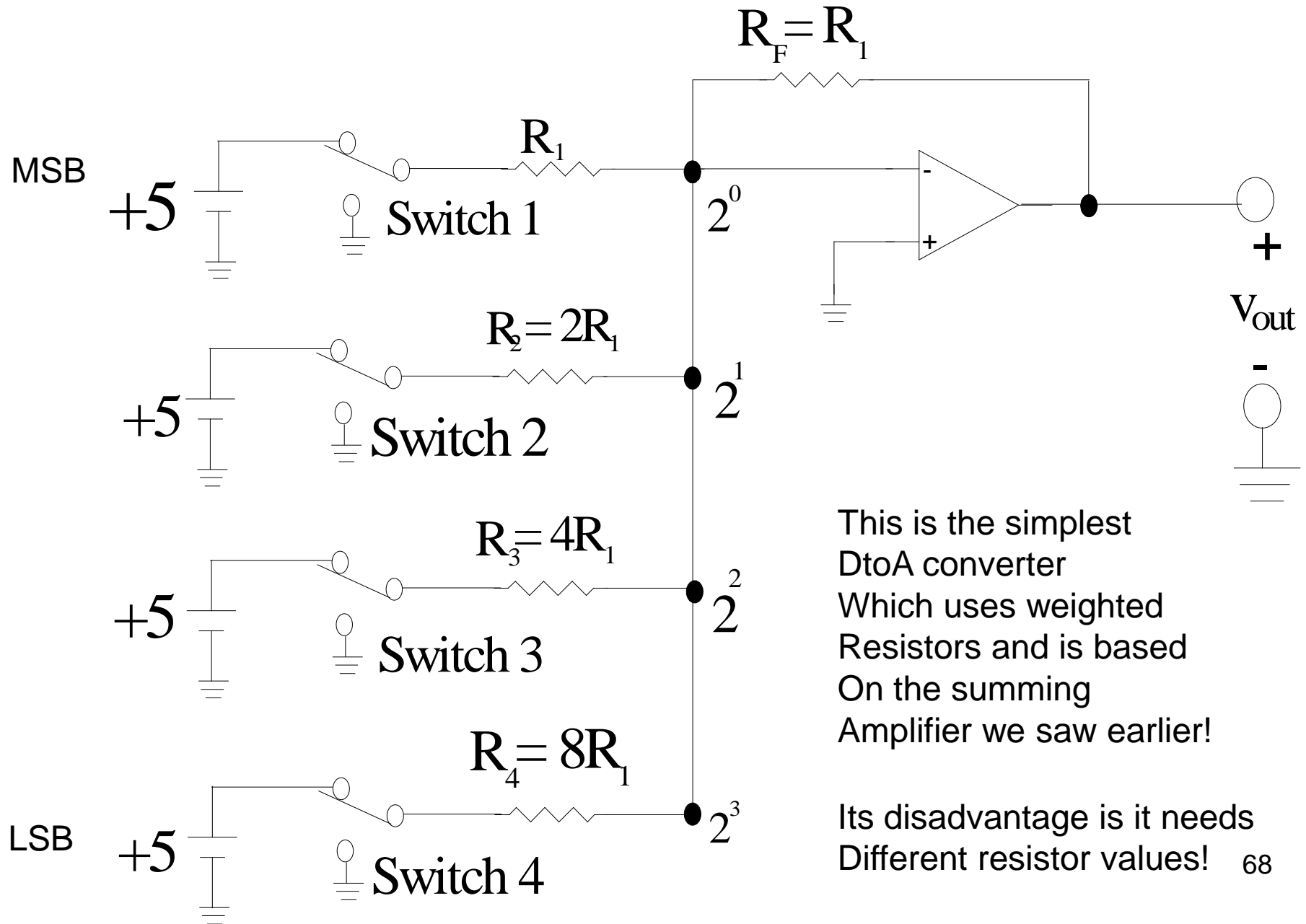

# Digital to Analog Converters


Here the switches are digital providing either 0V for '0' and +5V for '1'

The output voltage is given by:

$$v_{out} = -R_F \cdot \left( \frac{v_{S0}}{R_{S0}} + \frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} + \frac{v_{S3}}{R_{S3}} \right)$$


Where  $v_{S0}$  is the first digital input,  $v_{S1}$  is 2<sup>nd</sup> etc...
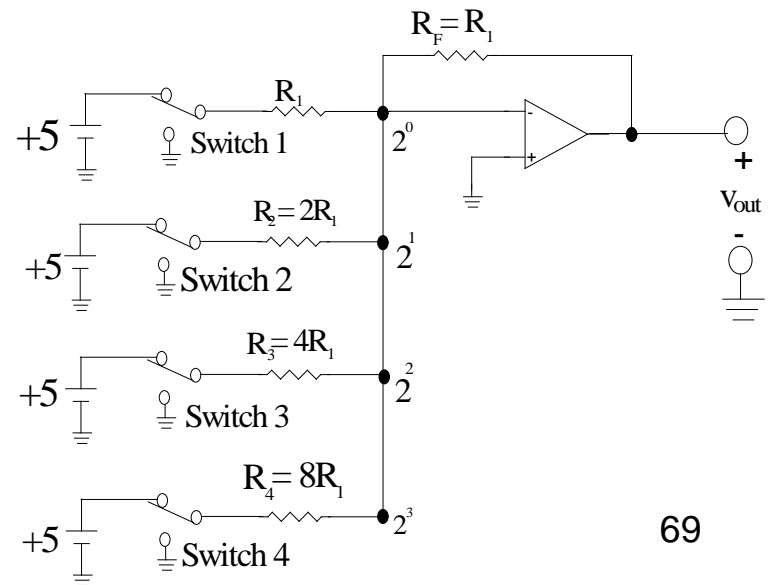
$$\begin{aligned} \therefore v_{out} &= -R_1 \cdot \left( \frac{v_{S0}}{R_1} + \frac{v_{S1}}{2R_1} + \frac{v_{S2}}{4R_1} + \frac{v_{S3}}{8R_1} \right) \\ &= - \left( v_{S0} + \frac{v_{S1}}{2} + \frac{v_{S2}}{4} + \frac{v_{S3}}{8} \right) \end{aligned}$$



# Digital to Analog Converters

## Example

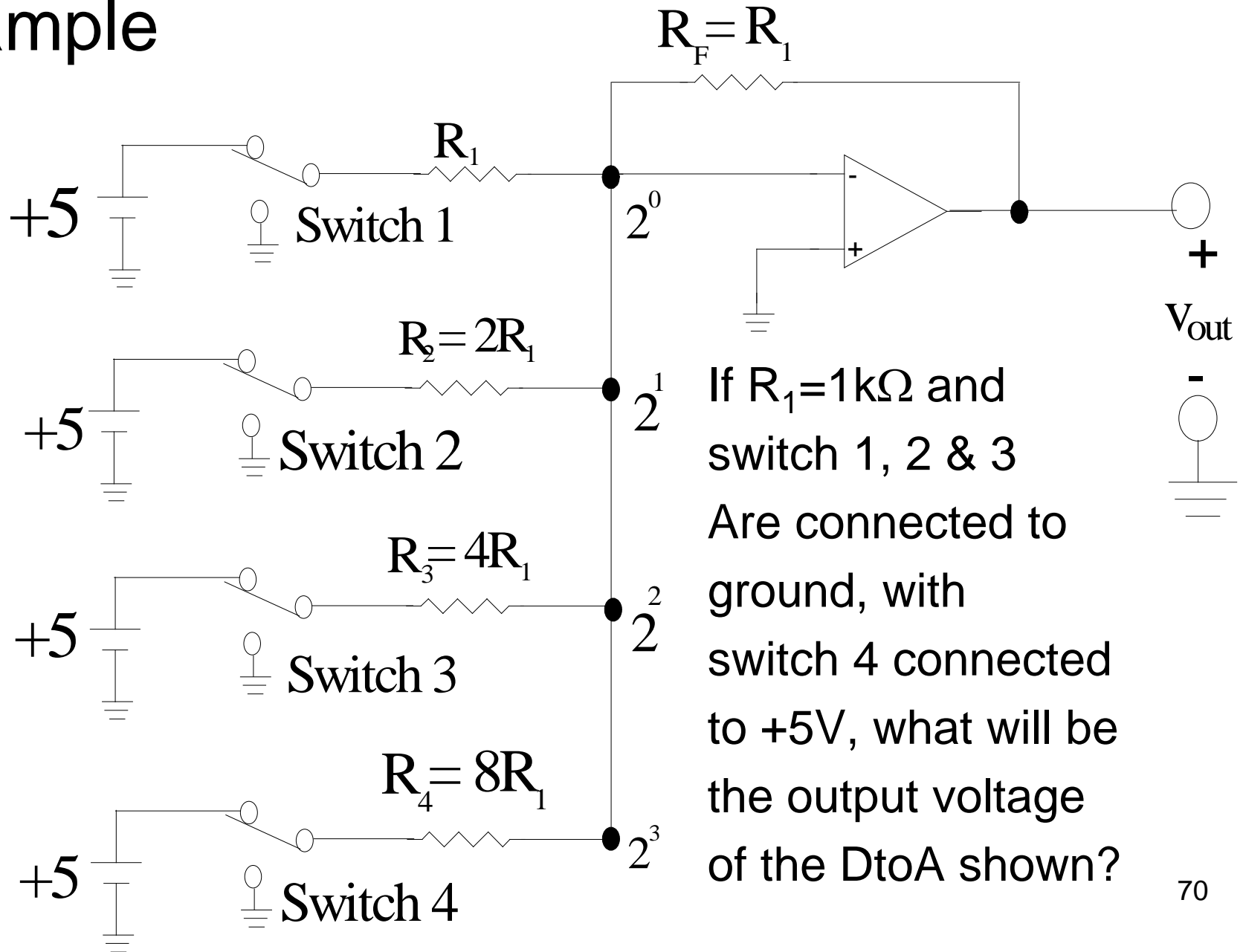

# Digital to Analog Converters

## Example


$$\begin{aligned}v_{out} &= -\left(v_{S0} + \frac{v_{S1}}{2} + \frac{v_{S2}}{4} + \frac{v_{S3}}{8}\right) \\&= -\left(0 + \frac{0}{2} + \frac{0}{4} + \frac{5}{8}\right) \\&= -0.625 \text{ volts}\end{aligned}$$

This would correspond to the binary number '0001'  
And also shows the resolution of the Converter  
(it changes in steps of 0.625 volts!)

# Digital to Analog Converters
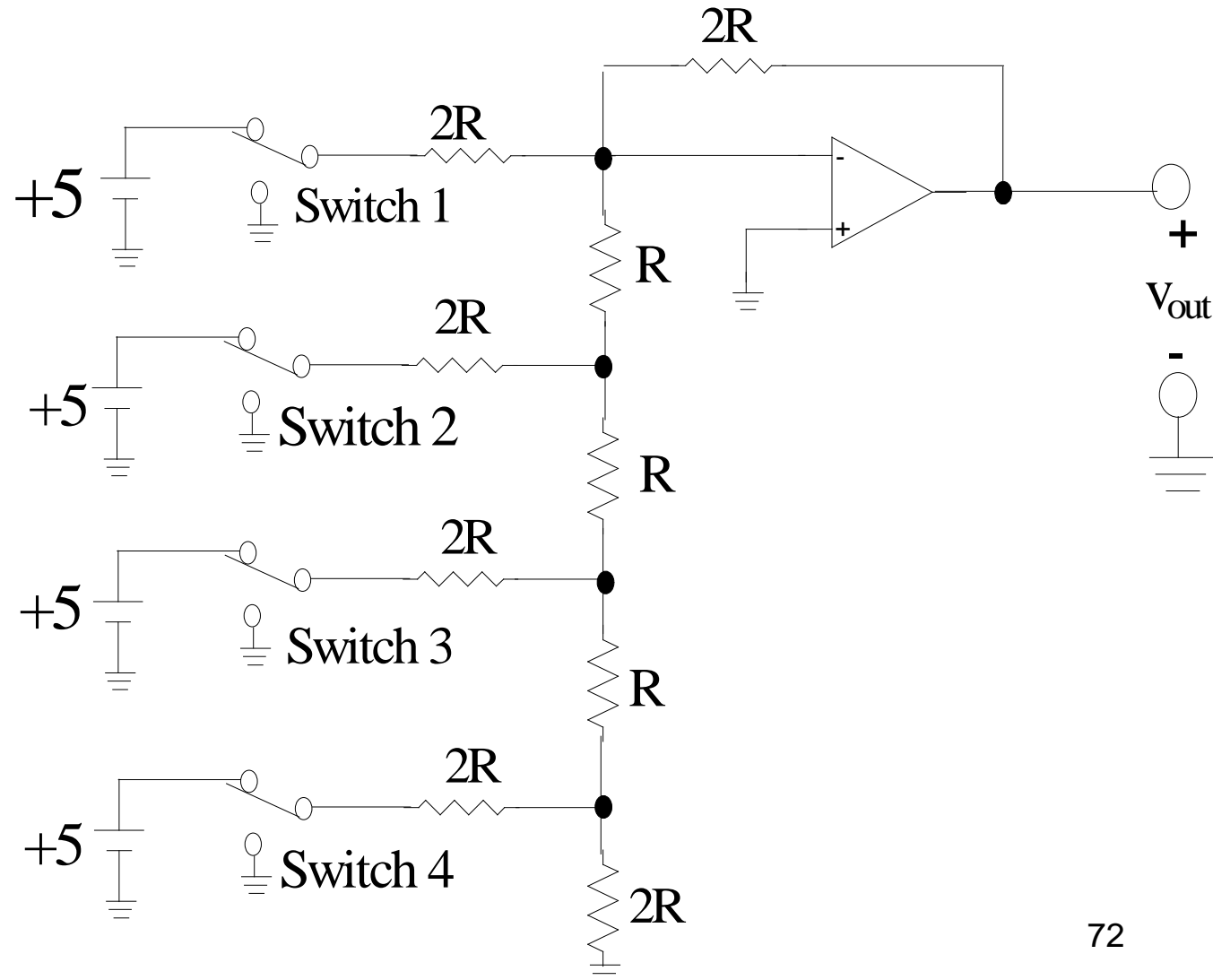
## R/2R ladder D/A

Has the Advantage Of only Needing Two resistor Values,  $2R$  and  $R$






# Digital to Analog Converters

## R/2R ladder D/A

Analysis:

We use the principle of superposition once again to solve  
This and we will need Thevenins Theorem

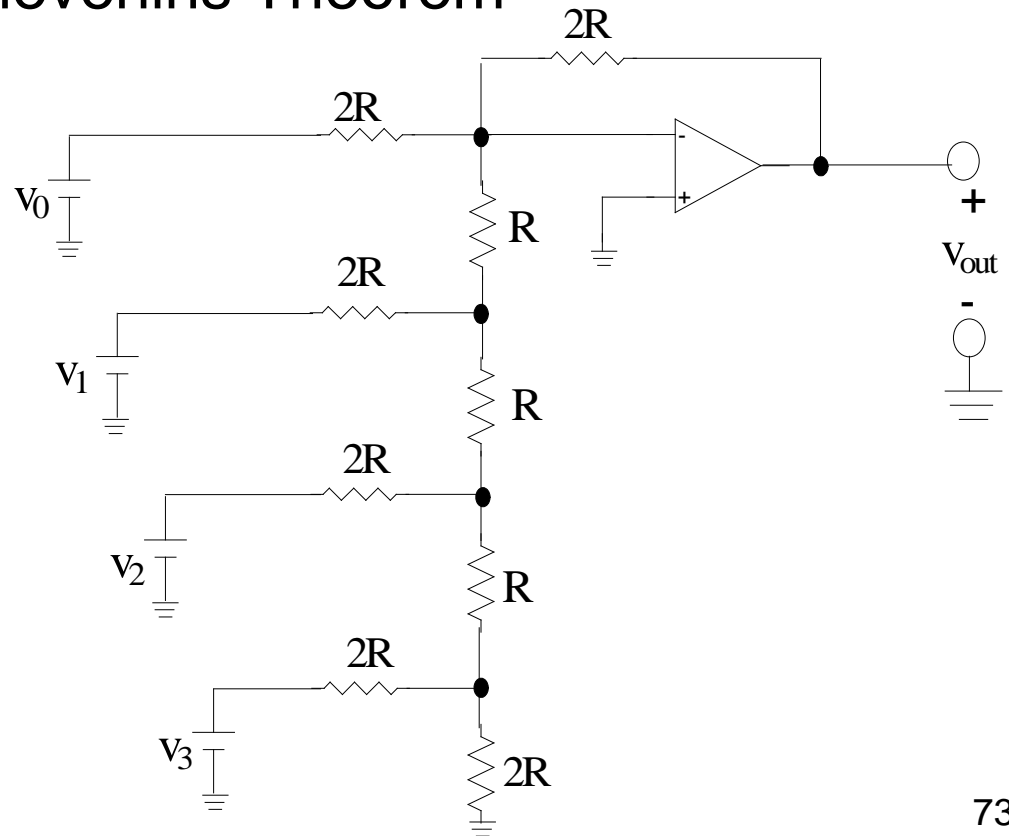Redrawing the circuit  
but now changing the  
switches to voltage  
Sources we get:




# Digital to Analog Converters

## R/2R ladder D/A

With  $v_1$ ,  $v_2$  &  $v_3$  suppressed:

We could stop here and  
Note that whatever the  
Resistance of the ladder  
Network is the virtual  
Ground makes this  
Resistance irrelevant,  
But for the next stage we  
Need to do this, so...

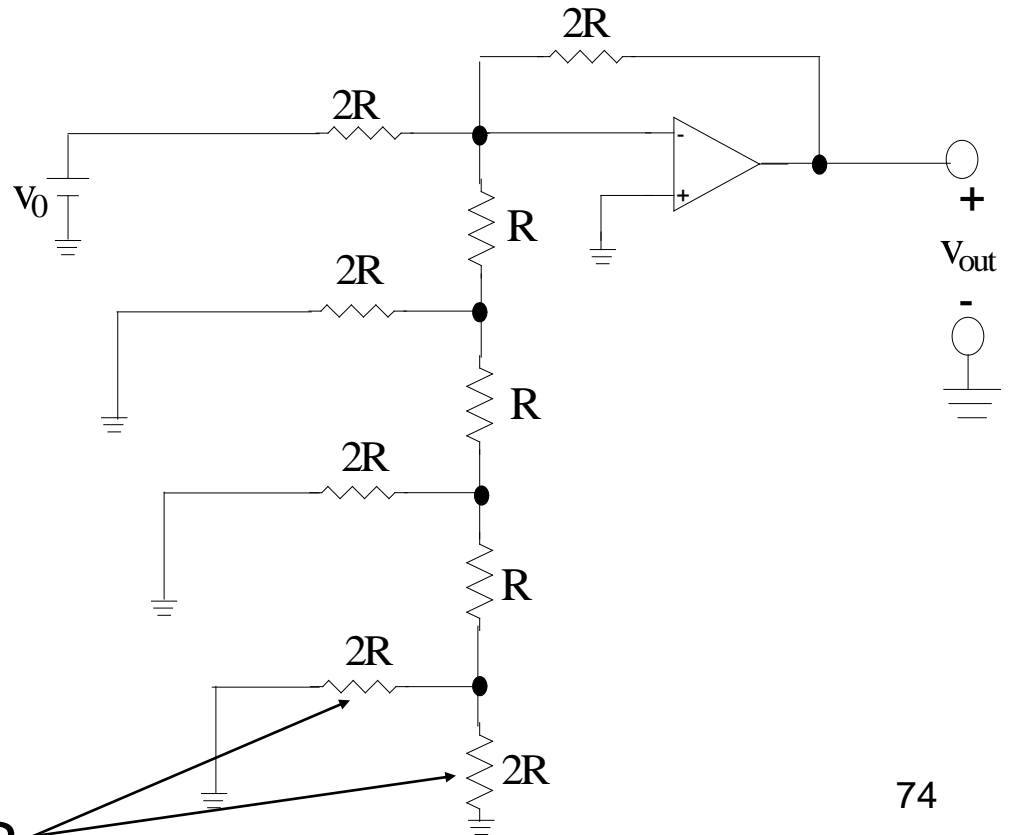
We now note that  
These two resistors  
Are in parallel ie  $2R \parallel 2R$



# Digital to Analog Converters

## R/2R ladder D/A


Which gives:

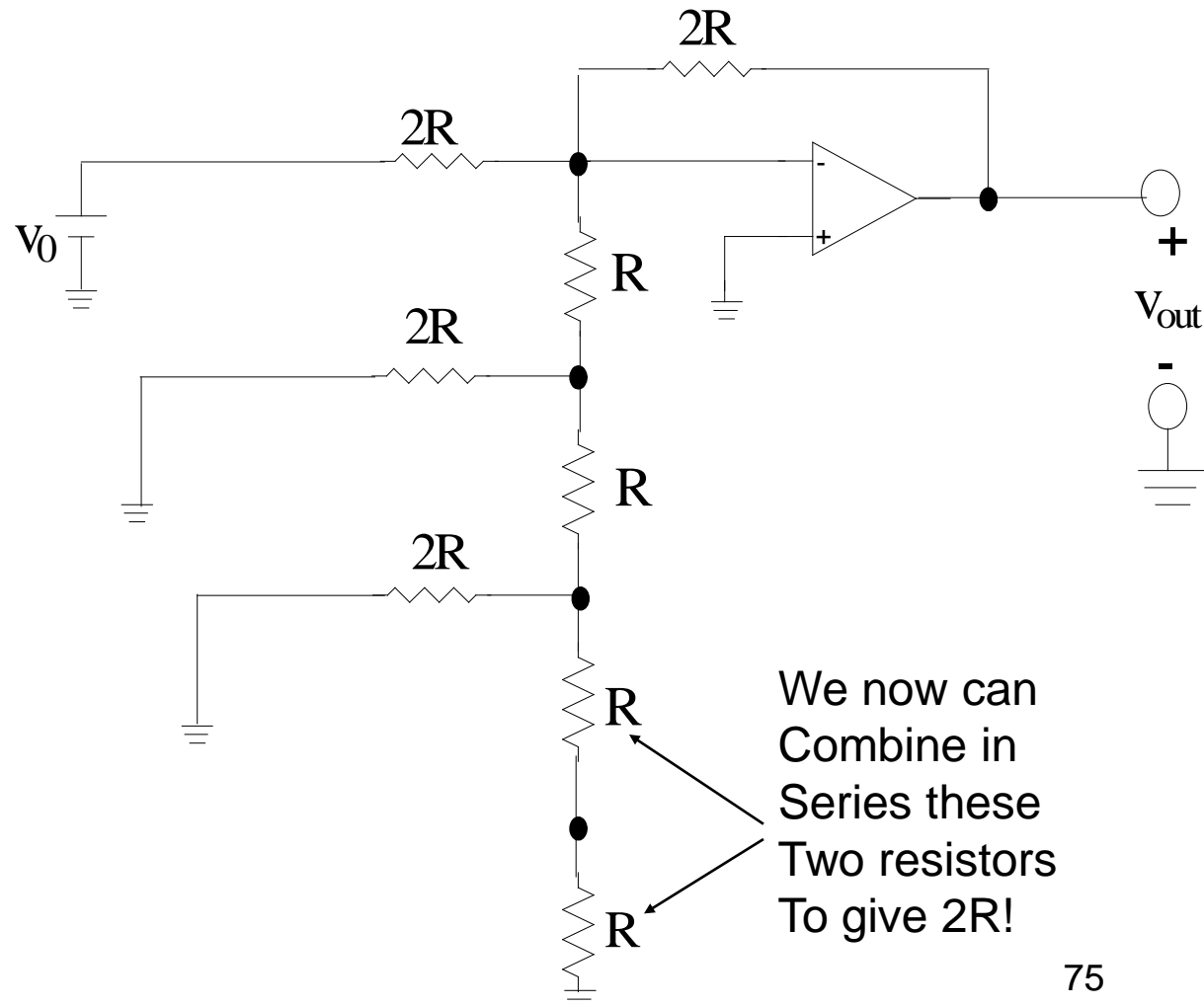

# Digital to Analog Converters

## R/2R ladder D/A

Which gives:

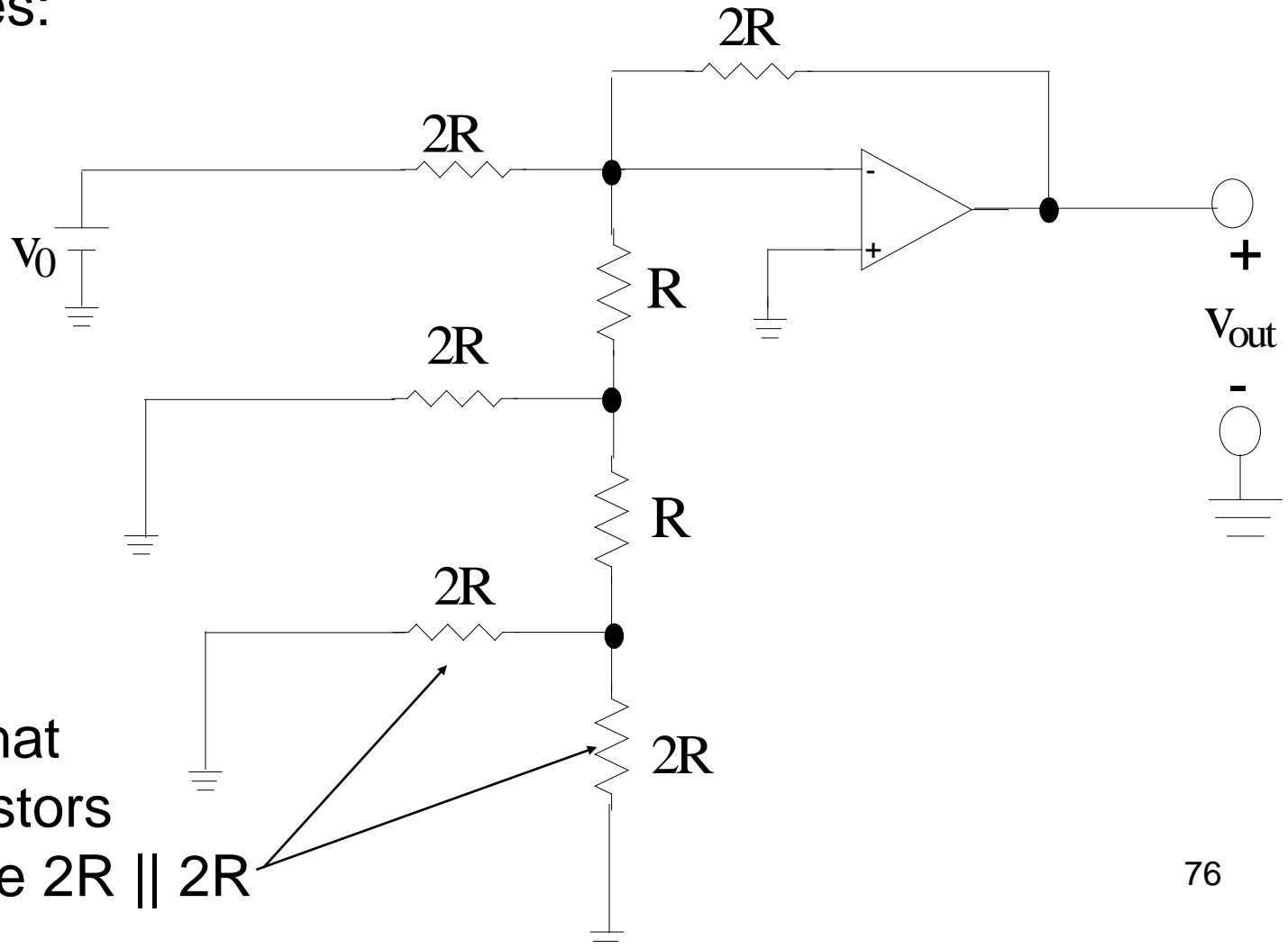


We now note that  
These two resistors  
Are in parallel ie  $2R \parallel 2R$

# Digital to Analog Converters

## R/2R ladder D/A


Which gives:

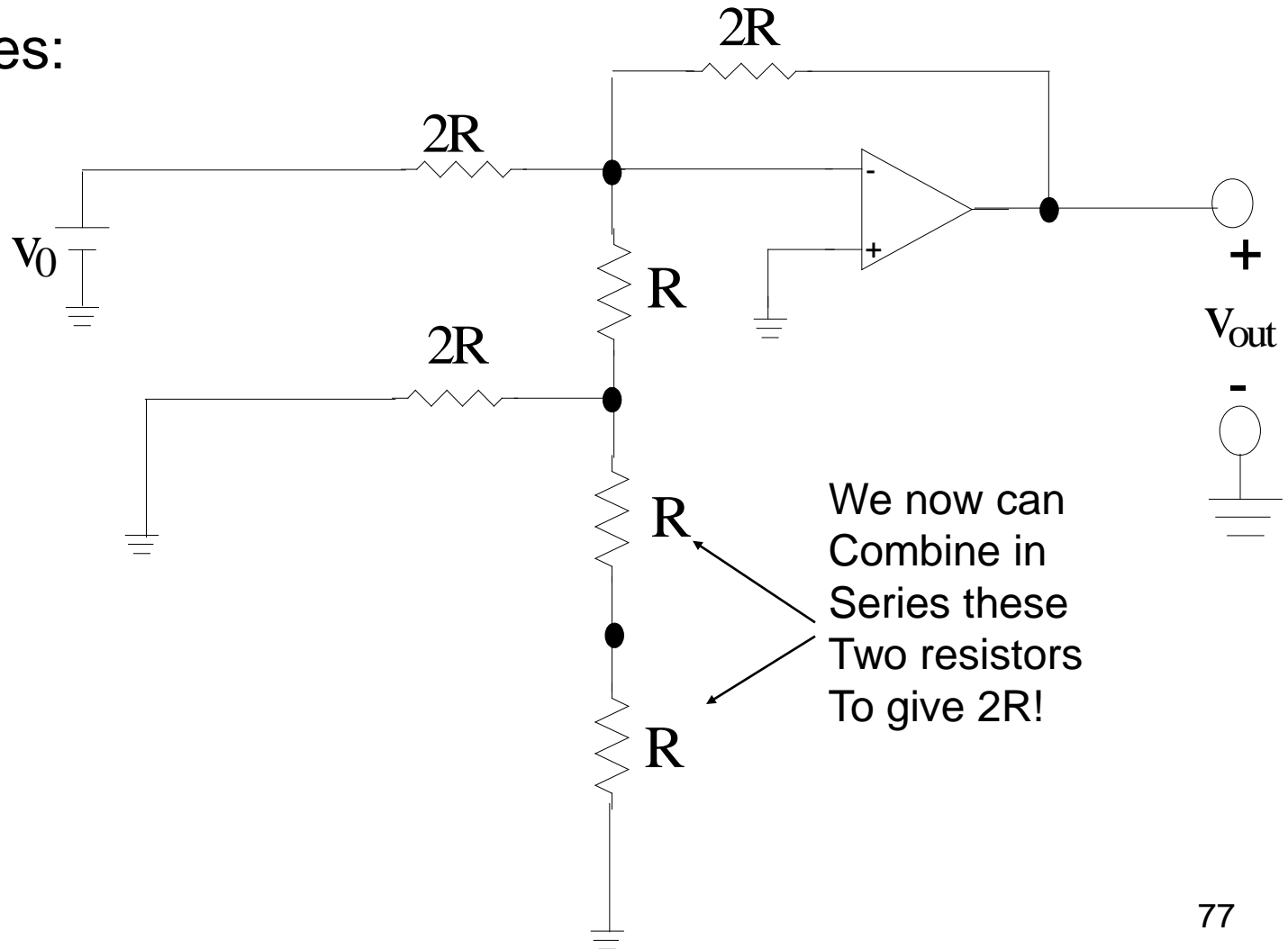

# Digital to Analog Converters

## R/2R ladder D/A


Which gives:

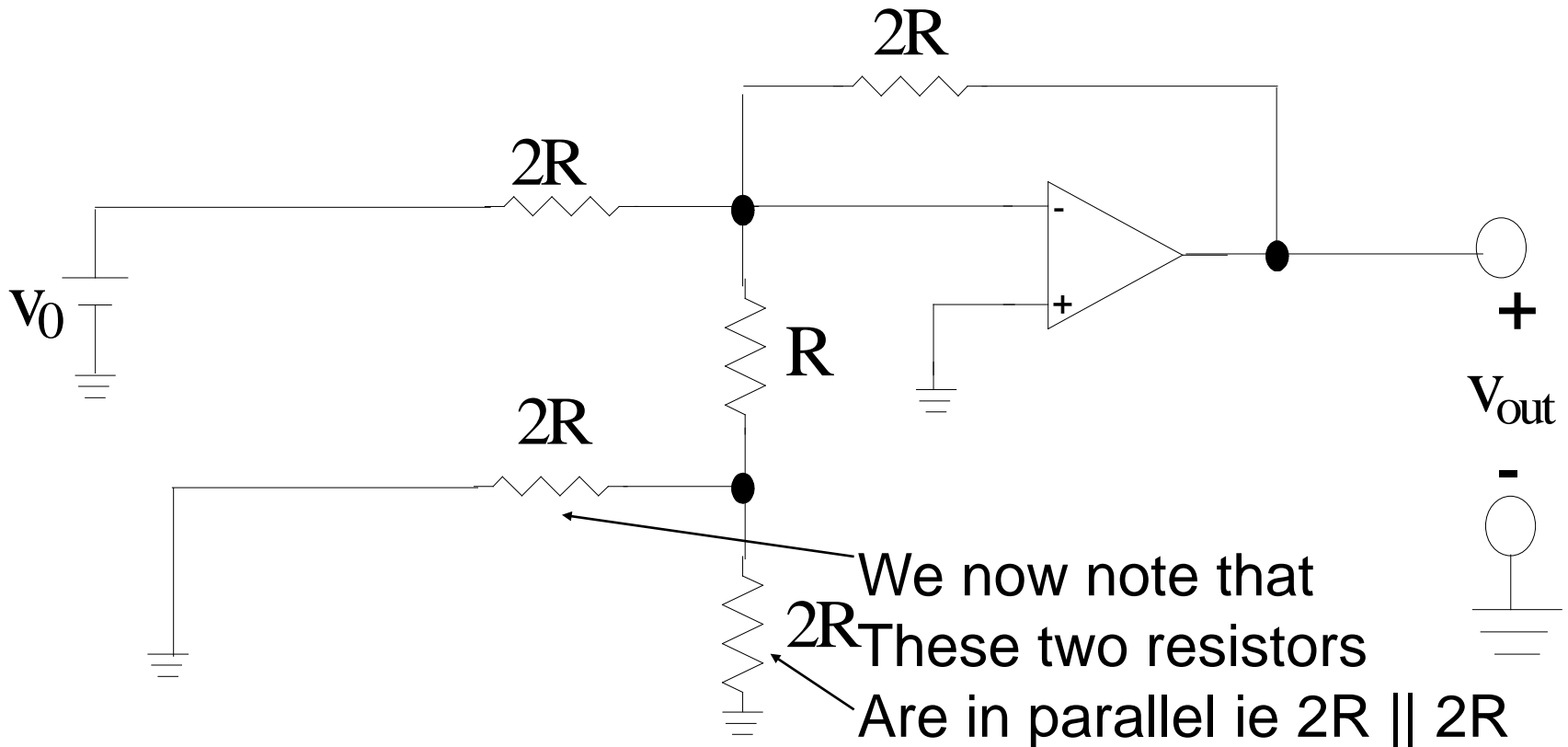

# Digital to Analog Converters

## R/2R ladder D/A


Which gives:

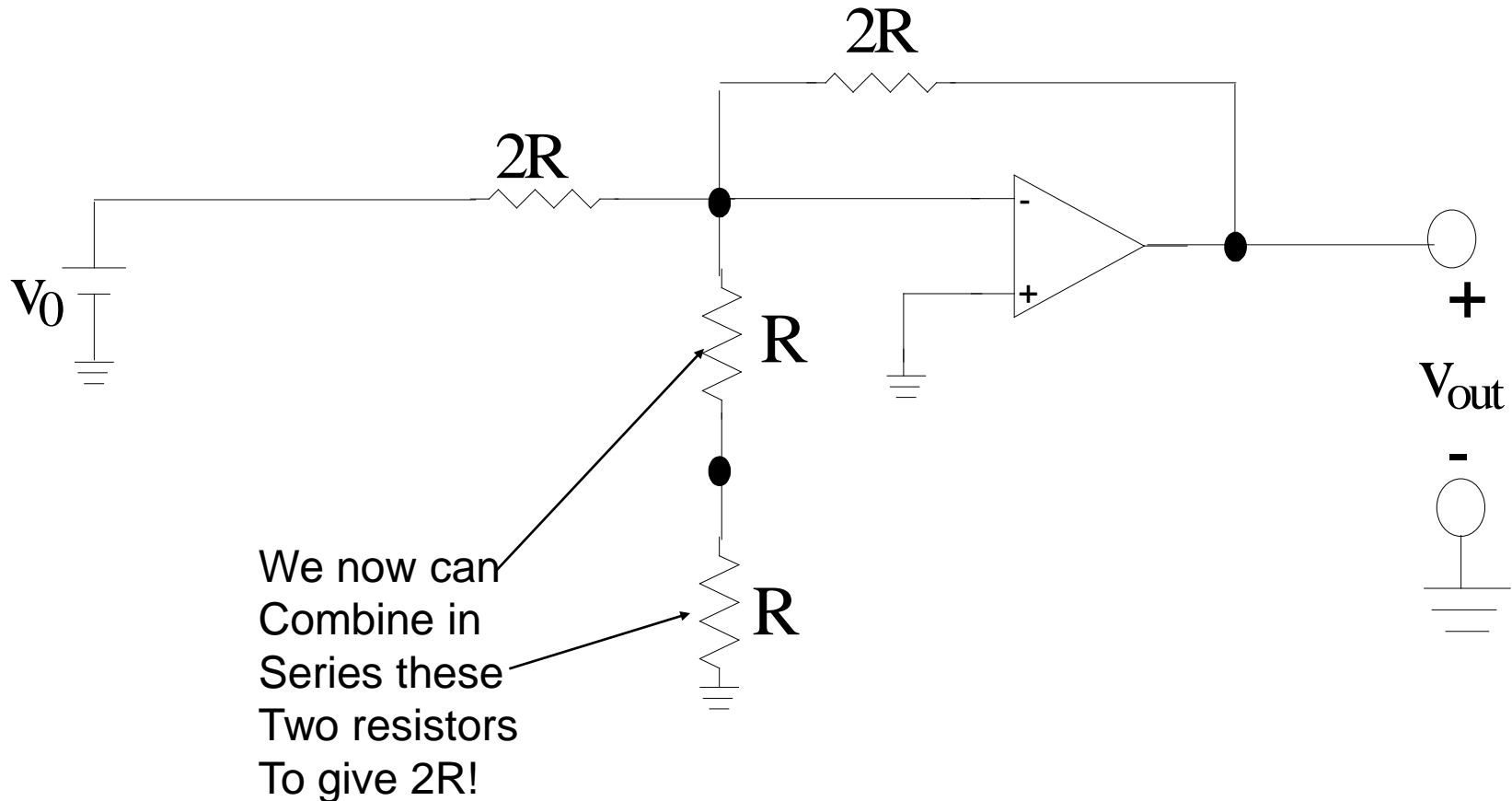

# Digital to Analog Converters

## R/2R ladder D/A

Which gives the  
Equivalent circuit:

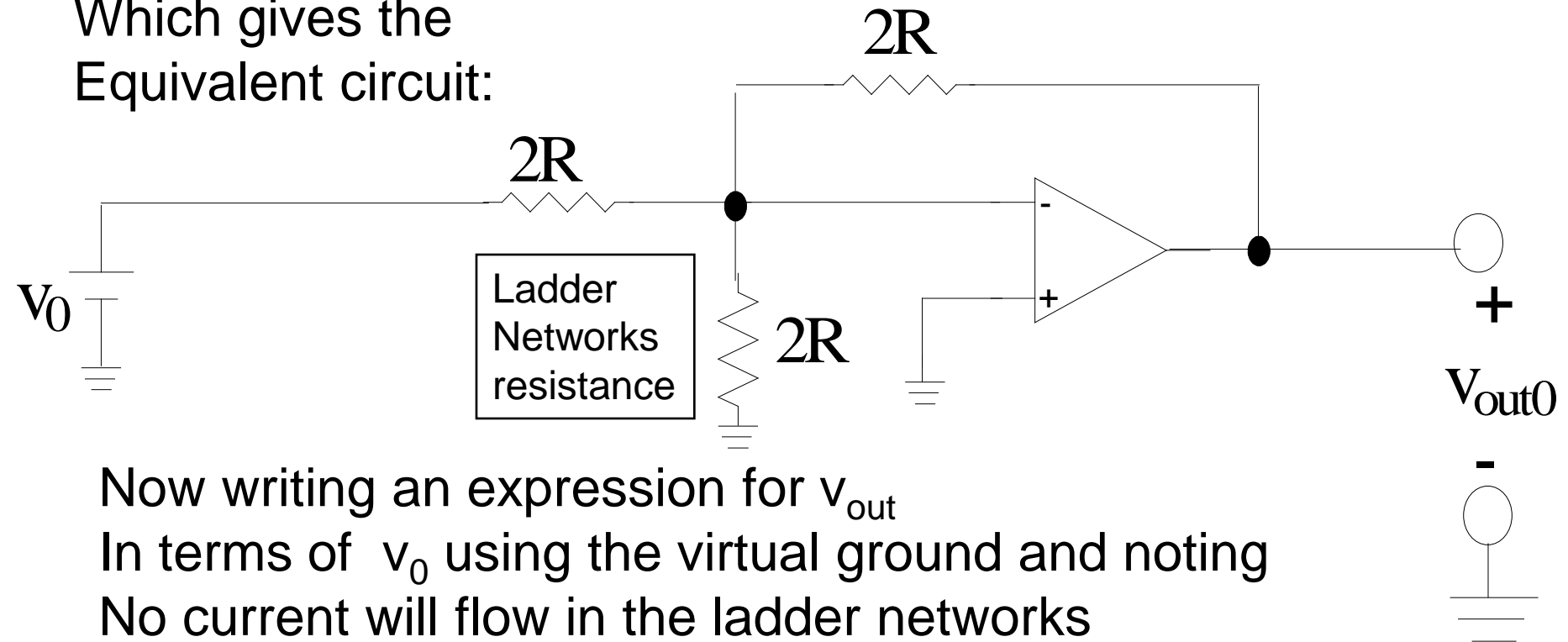

Now writing an expression for  $v_{out}$

In terms of  $v_0$  using the virtual ground and noting

No current will flow in the ladder networks

Resistor ( $2R$ ) we get:

$$v_{out} = v_{out0} = -\frac{2R}{2R} v_o = -v_o$$


$V_0$  is either +5V or 0V



# Digital to Analog Converters
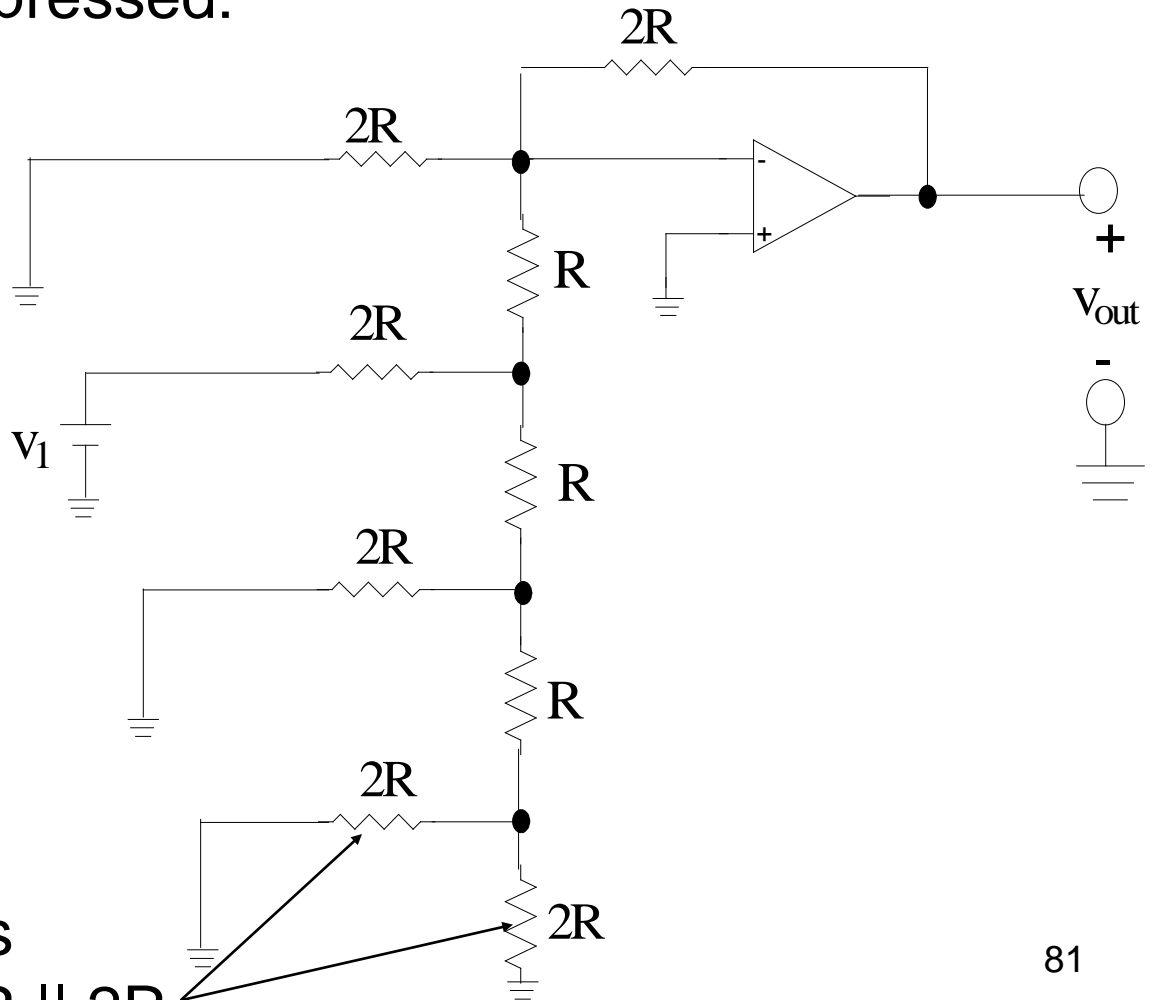
## R/2R ladder D/A

With  $v_0$ ,  $v_2$  &  $v_3$  suppressed:




We now note that  
These two resistors  
Are in parallel ie  $2R \parallel 2R$

# Digital to Analog Converters

## R/2R ladder D/A

Which gives

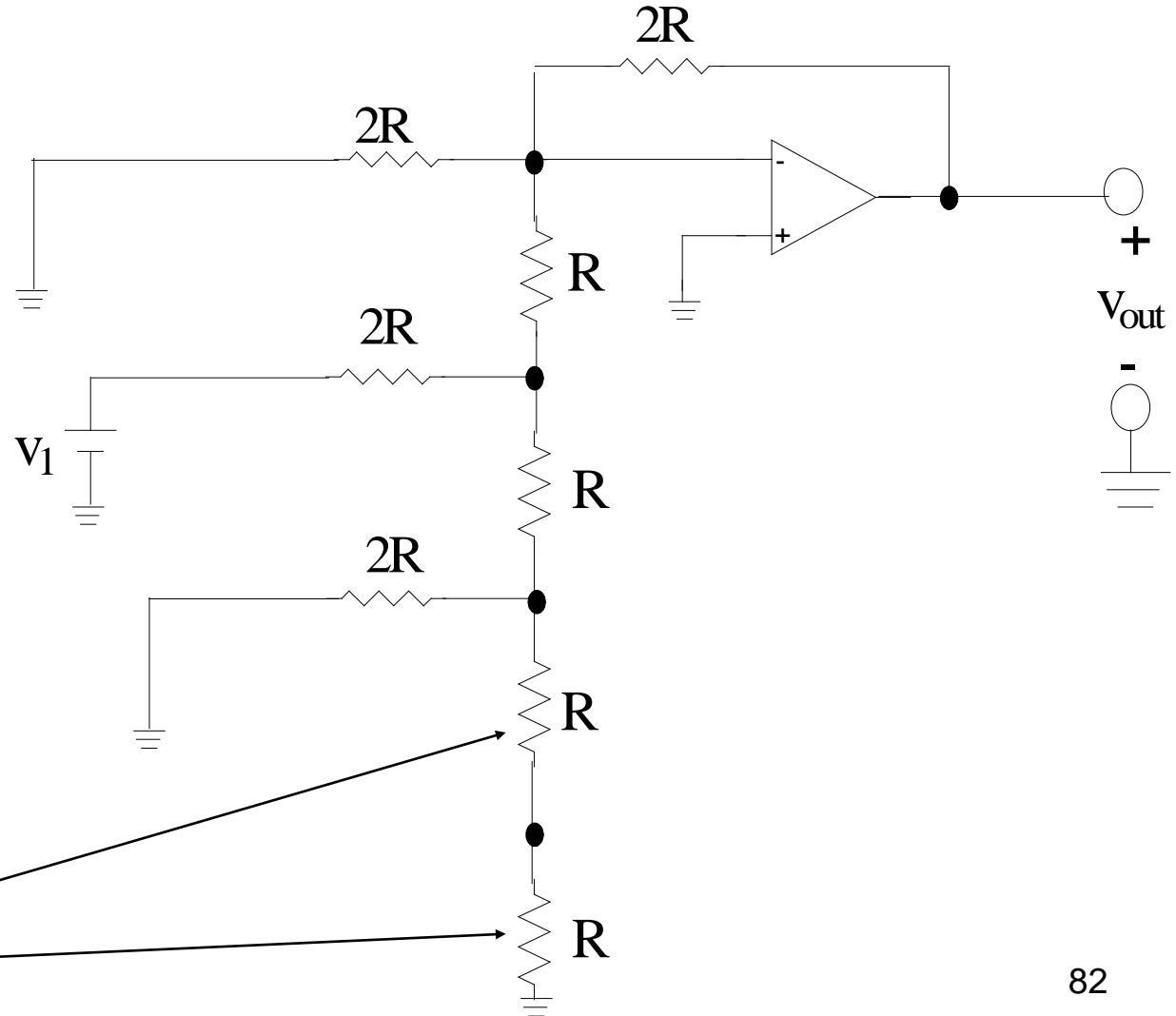


We now can  
Combine in  
Series these  
Two resistors  
To give  $2R$ !

# Digital to Analog Converters

## R/2R ladder D/A


Which gives

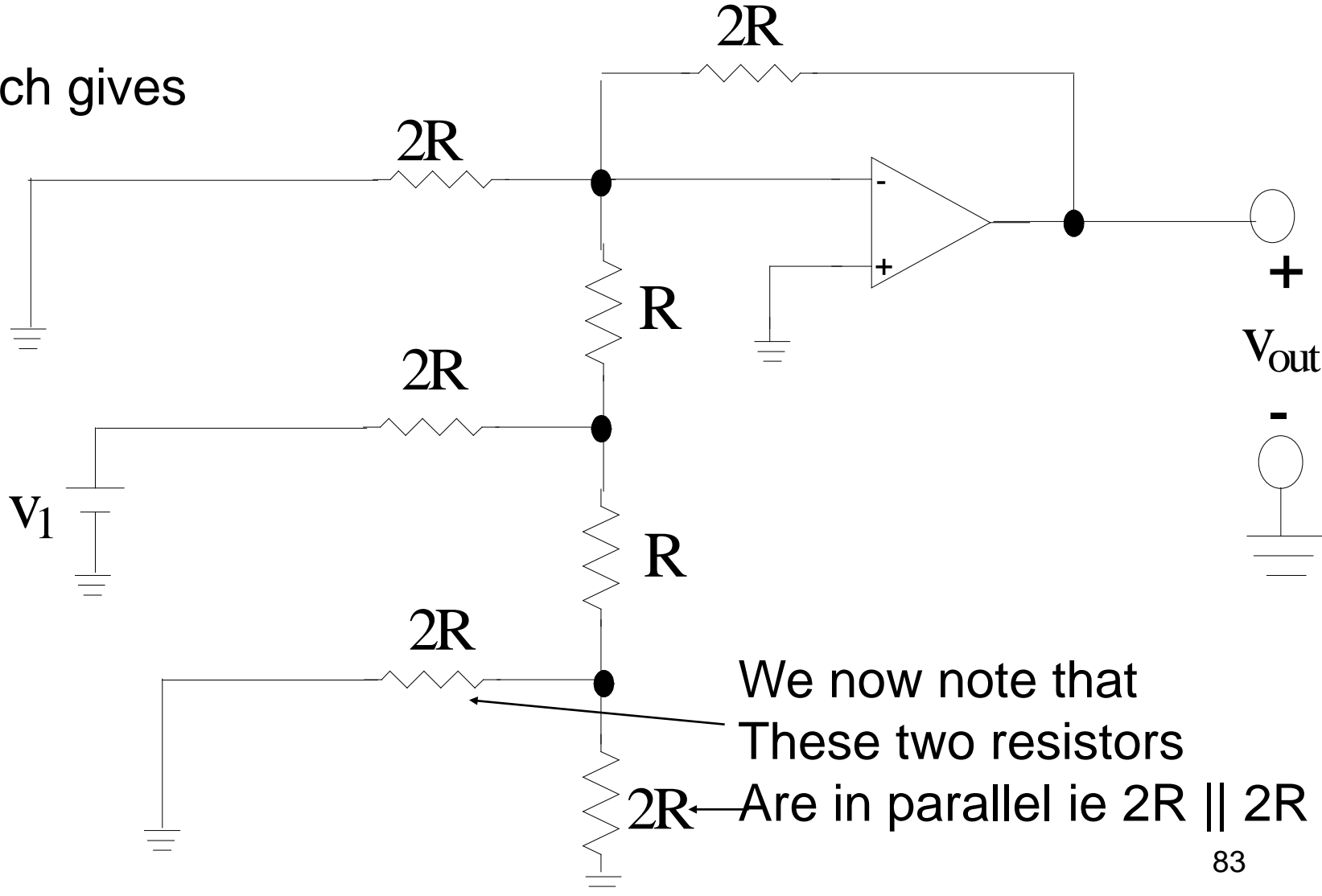

# Digital to Analog Converters

## R/2R ladder D/A

Which gives

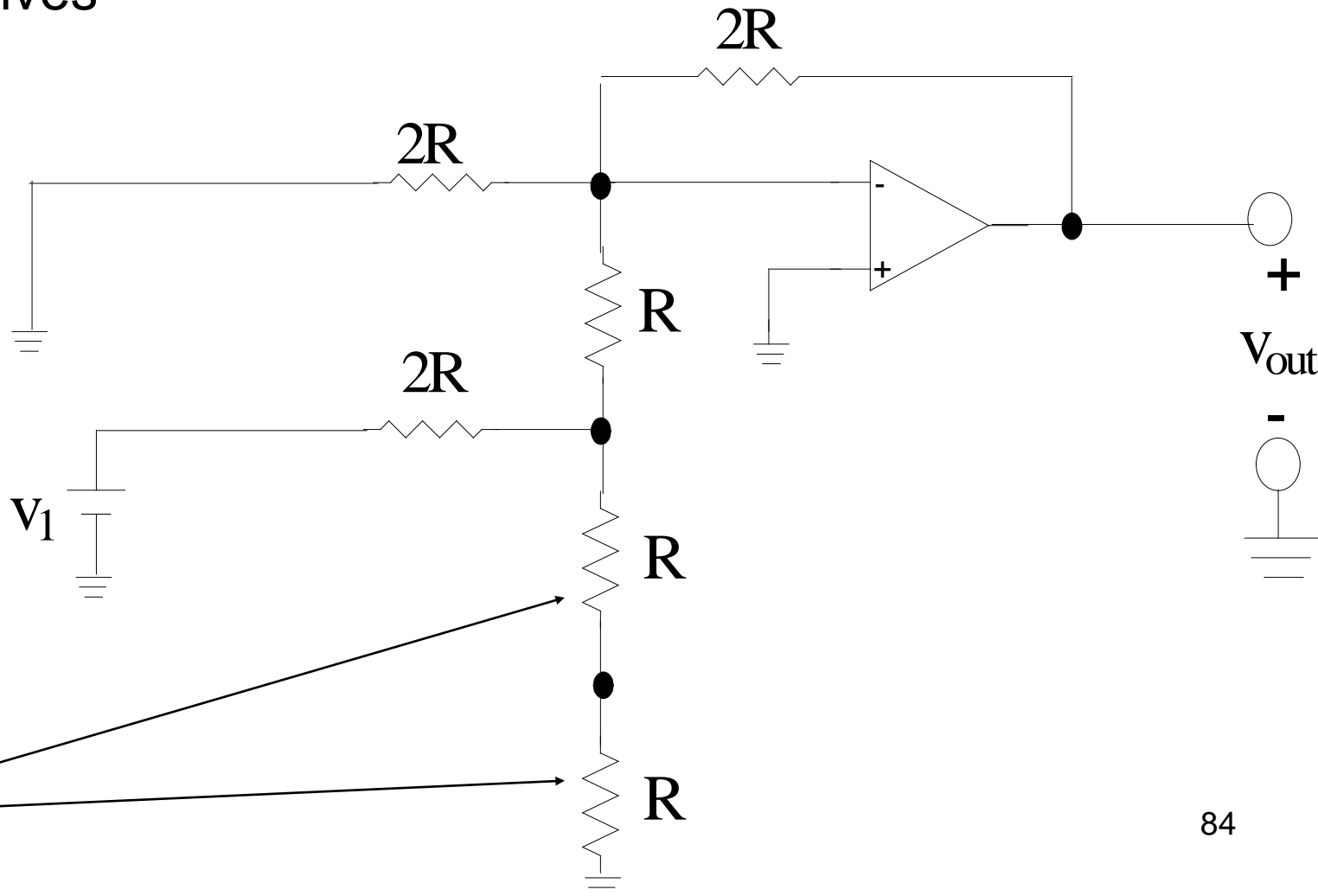


We now can  
Combine in  
Series these  
Two resistors  
To give  $2R$ !

# Digital to Analog Converters

## R/2R ladder D/A

Which gives

 


Using node 'a' to ground we need to calculate the Thevenin equivalent Voltage and Resistance!

# Digital to Analog Converters

## R/2R ladder D/A

Redrawing:

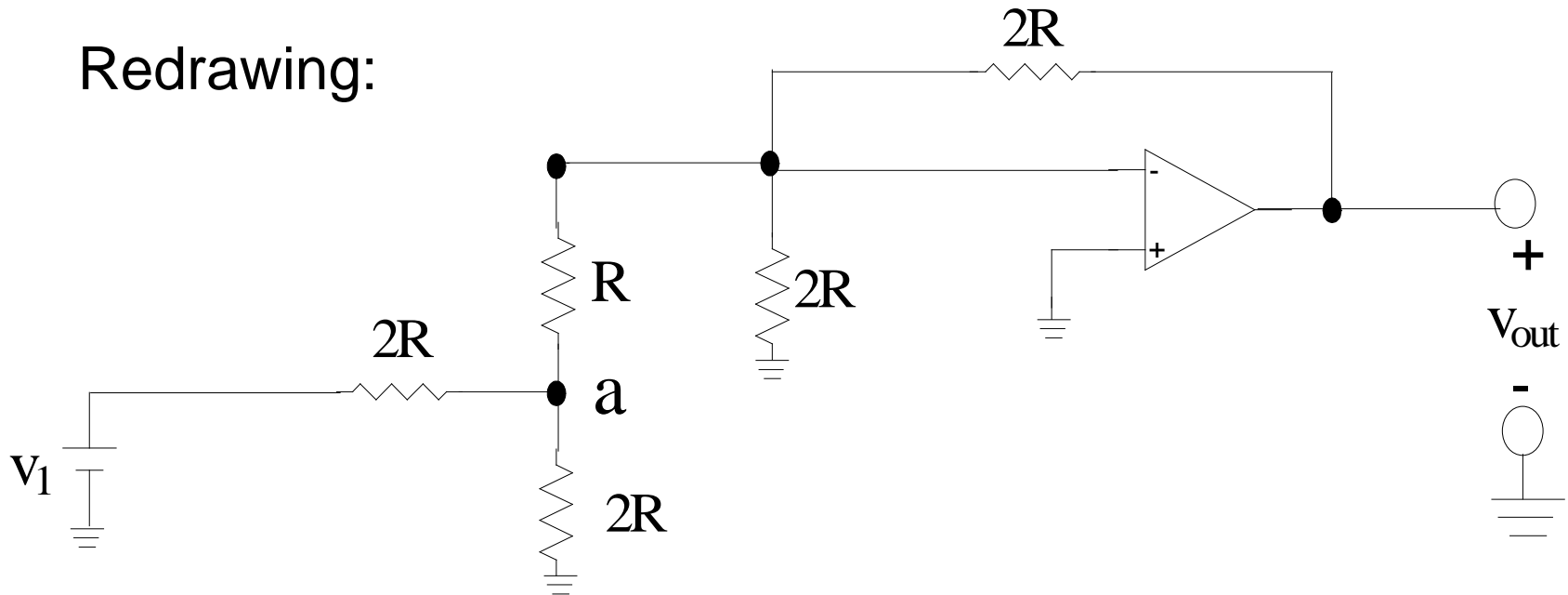

Thevenin voltage from node 'a' to ground is:

$$E_{Th} = \frac{2R}{2R + 2R} v_1 = \frac{v_1}{2}$$


Thevenin resistance from node 'a' to ground is (suppressing  $v_1$ ):

$$2R \parallel 2R = R = R_{Th}$$

# Digital to Analog Converters

## R/2R ladder D/A


Which gives

 

We now can  
Combine in  
Series these  
Two resistors  
To give  $2R$ !

# Digital to Analog Converters

## R/2R ladder D/A

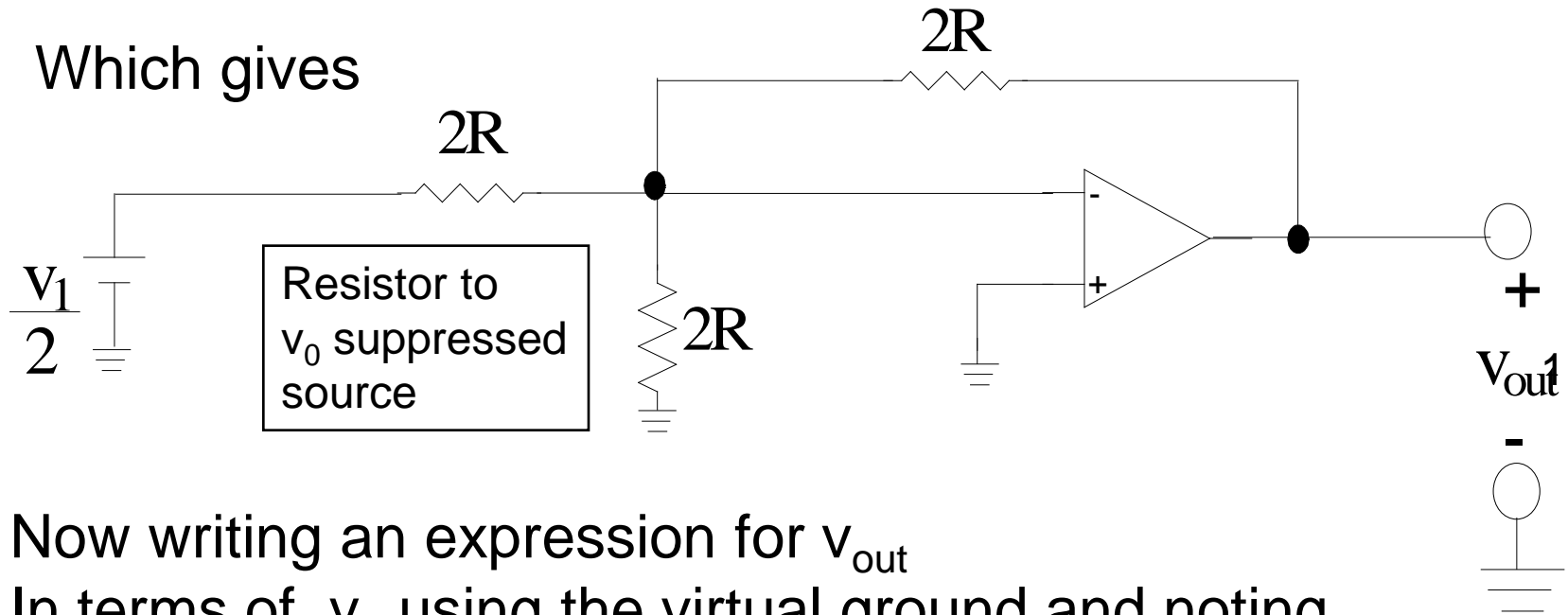

Now writing an expression for  $v_{out}$

In terms of  $v_1$  using the virtual ground and noting

No current will flow in the resistor to  $v_0$ 's

Suppressed source ( $2R$ ) we get:

$$v_{out} = v_{out1} = -\frac{2R}{2R} \frac{v_1}{2} = -\frac{v_1}{2}$$


$v_1$  is either +5V or 0V



# Digital to Analog Converters
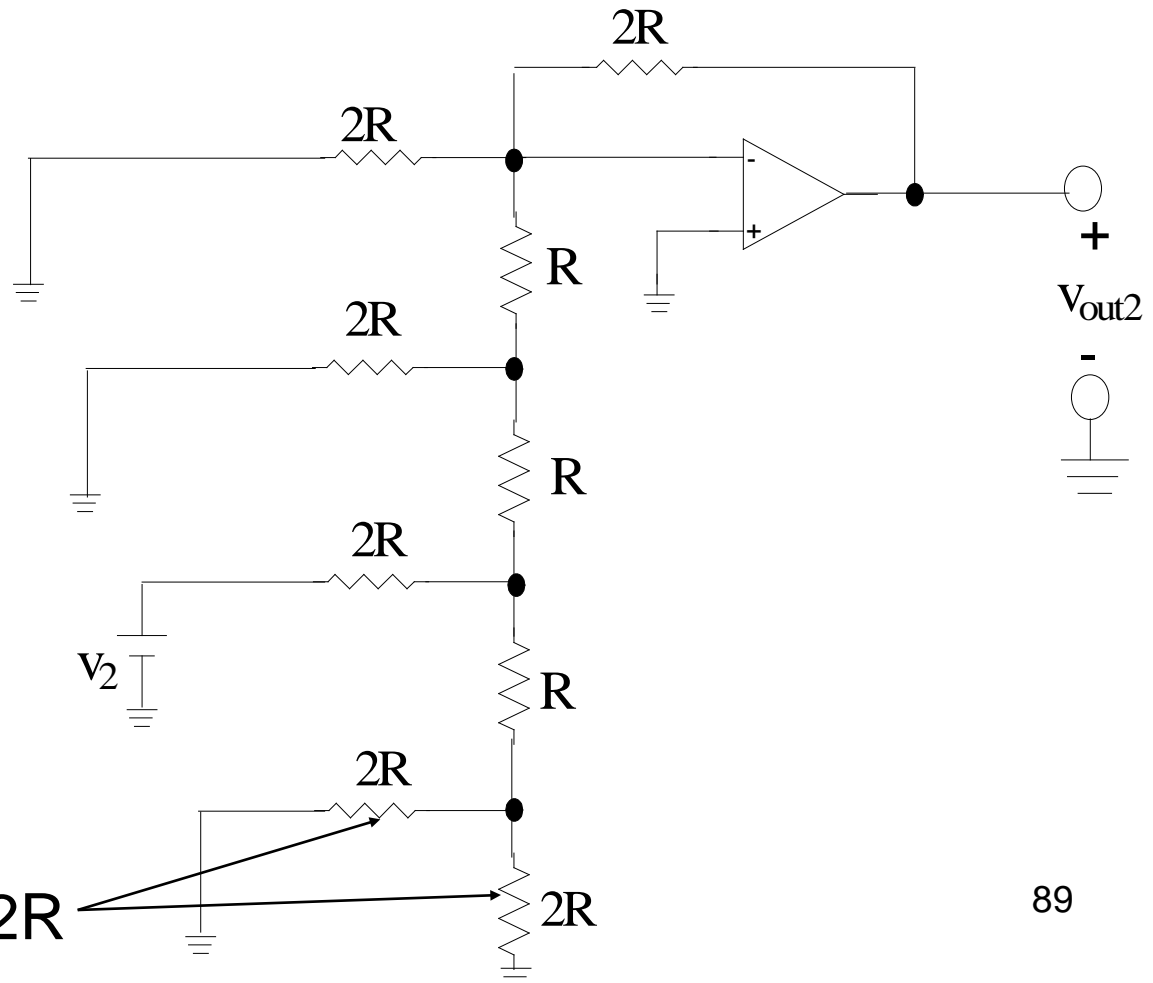
## R/2R ladder D/A

With  $v_0$ ,  $v_1$  &  $v_3$  suppressed:




We now note that  
These two resistors  
Are in parallel ie  $2R \parallel 2R$

# Digital to Analog Converters

## R/2R ladder D/A

Which gives

 


We now can  
Combine in  
Series these  
Two resistors  
To give  $2R$ !


# Digital to Analog Converters

## R/2R ladder D/A

Which gives

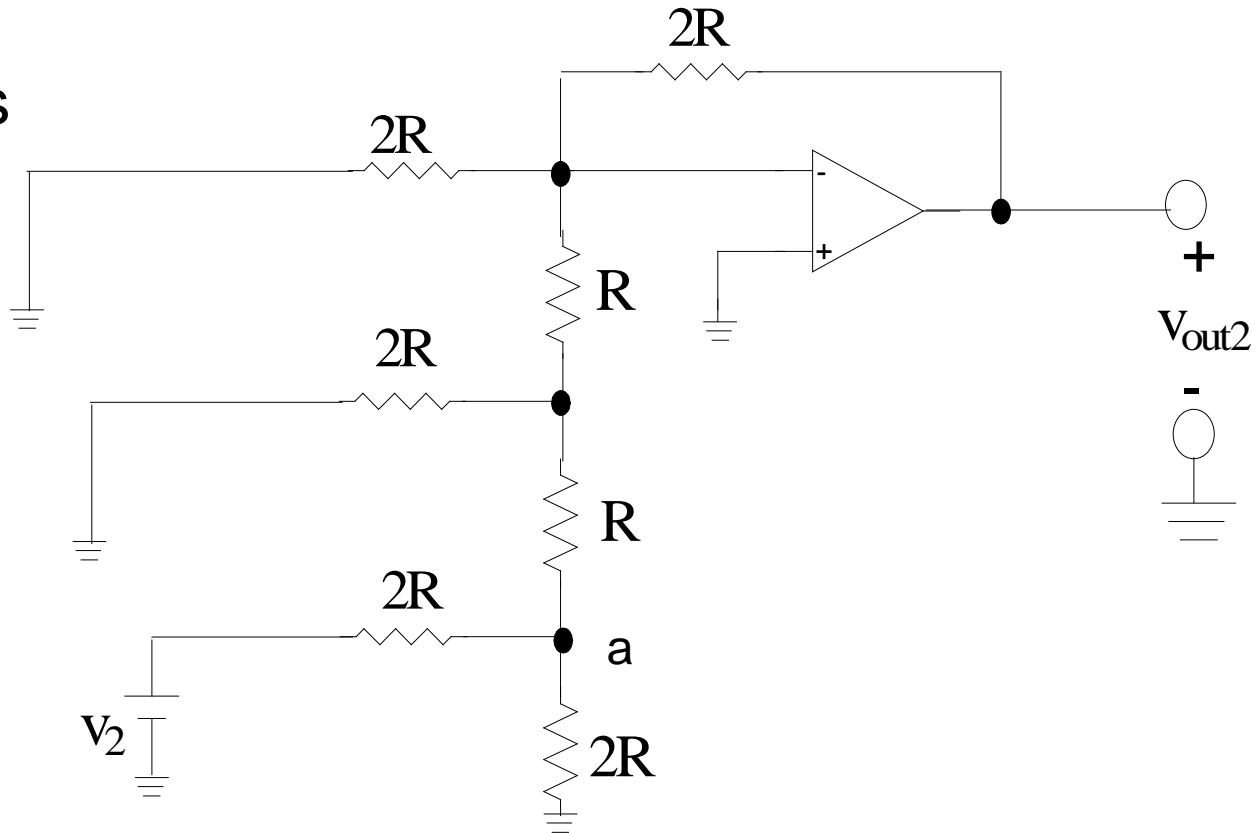

 Using node 'a' to ground we need to calculate the Thevenin equivalent Voltage and Resistance!




Thevenin voltage from node 'a' to ground is:


$$E_{Th} = \frac{2R}{2R + 2R} v_2 = \frac{v_2}{2}$$

Thevenin resistance from node 'a' to ground is (suppressing  $v_2$ ):

$$2R \parallel 2R = R = R_{Th}$$

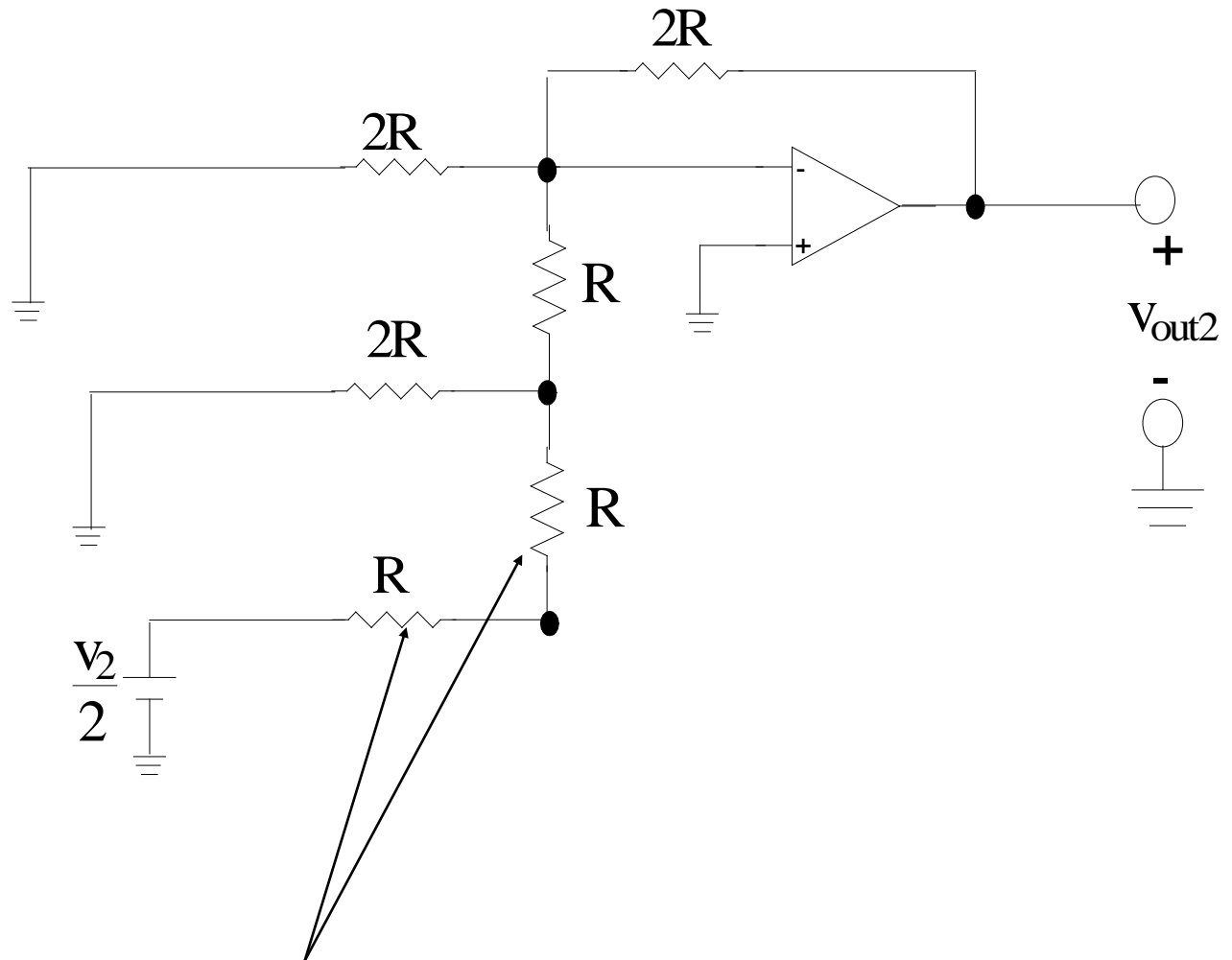

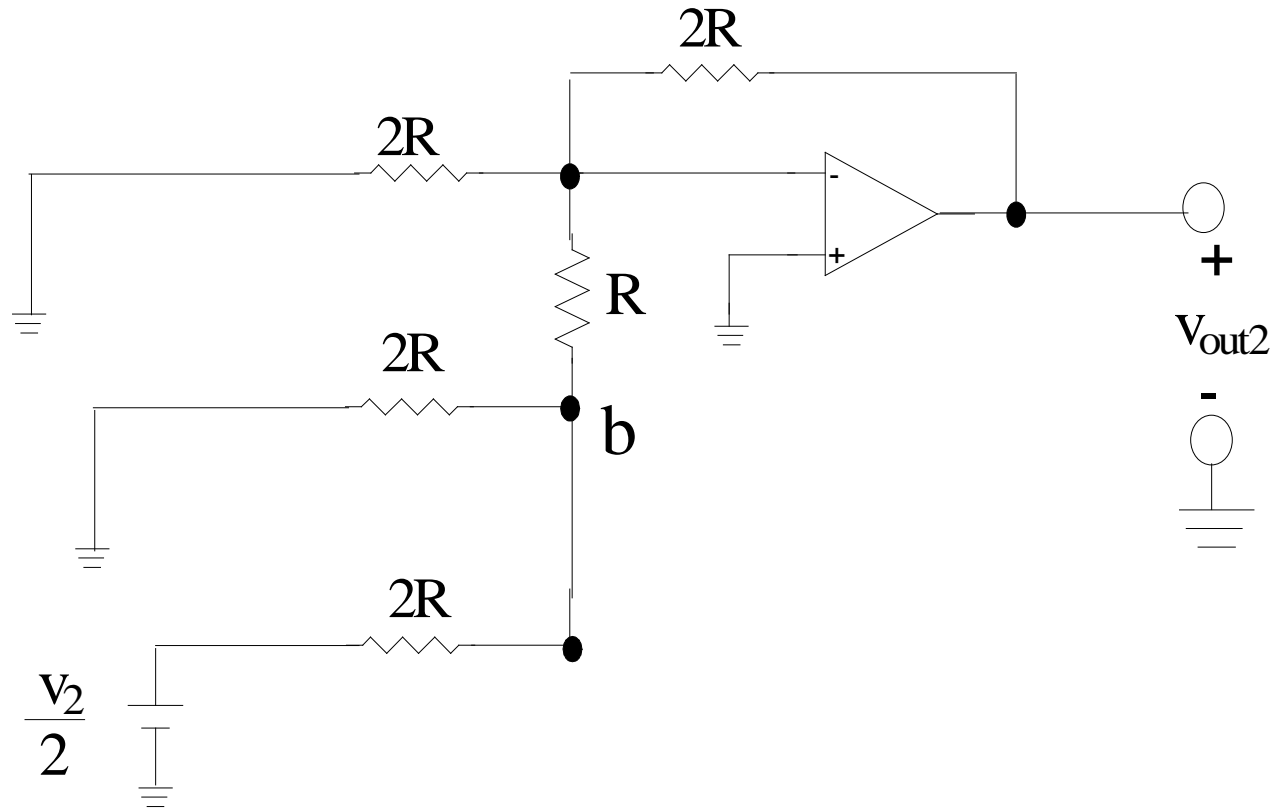We now can  
Combine in  
Series these  
Two resistors  
To give  $2R$ !




Thevenin voltage from node 'b' to ground is:


$$E_{Th} = \frac{2R}{2R + 2R} \frac{v_2}{2} = \frac{v_2}{4}$$

Thevenin resistance from node 'b' to ground is (suppressing  $v_2$ ):

$$2R \parallel 2R = R = R_{Th}$$

 

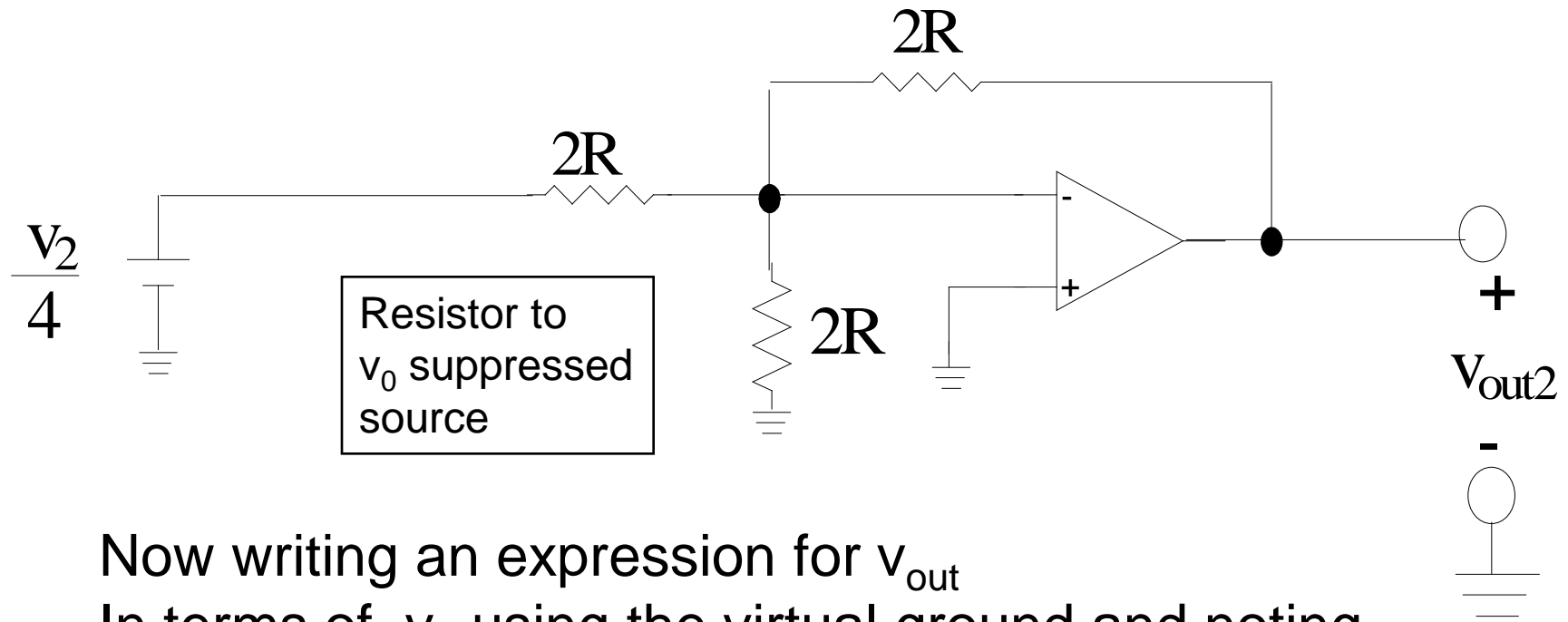We now can  
Combine in  
Series these  
Two resistors  
To give  $2R$ !



Now writing an expression for  $v_{out}$

In terms of  $v_2$  using the virtual ground and noting

No current will flow in the resistor to  $v_0$ 's

Suppressed source ( $2R$ ) we get:

$$v_{out} = v_{out2} = -\frac{2R}{2R} \frac{v_2}{4} = -\frac{v_2}{4}$$


$v_2$  is either +5V or 0V



# Digital to Analog Converters

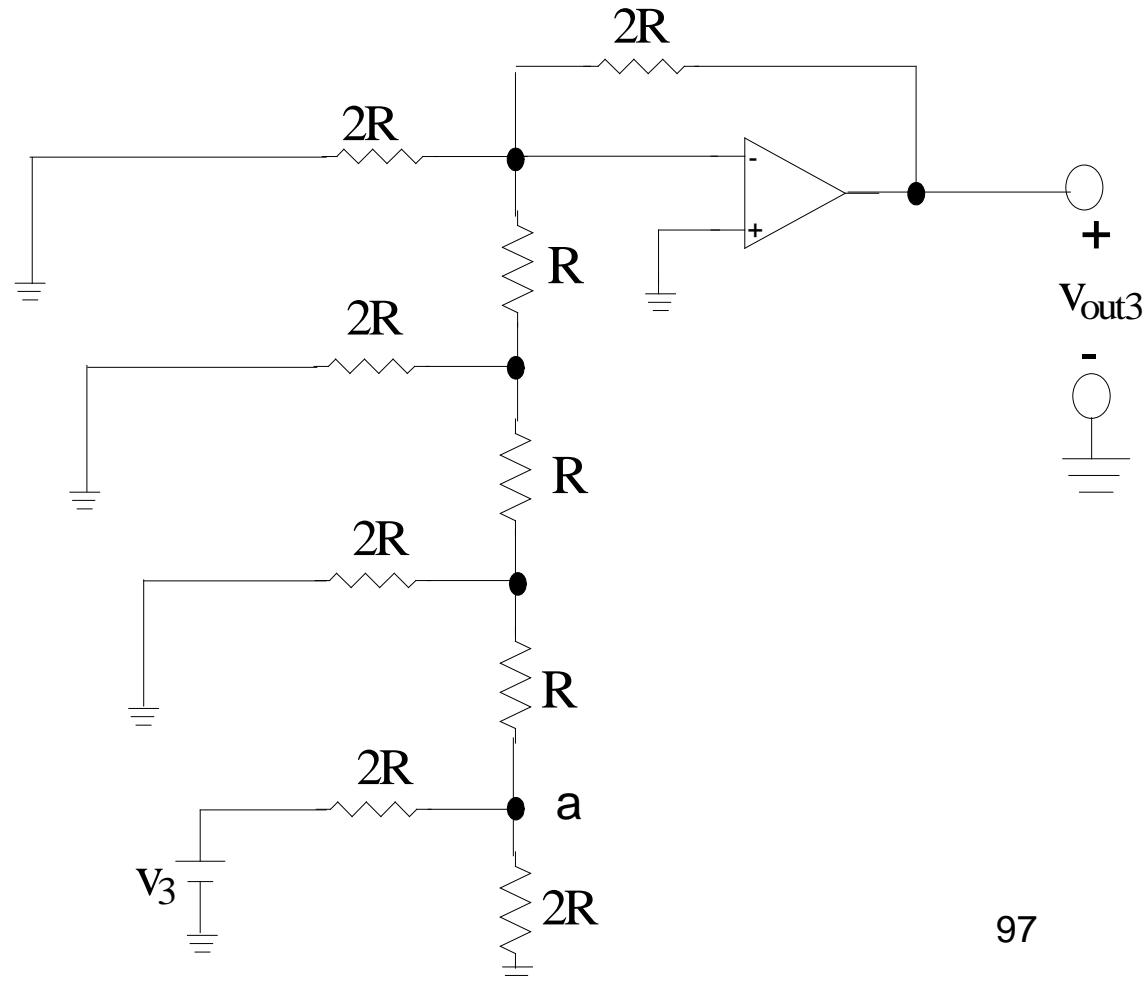
## R/2R ladder D/A

With  $v_0$ ,  $v_1$  &  $v_2$  suppressed:




Calculating Thevenin  
Equivalent at node 'a'  
To ground

Gives:

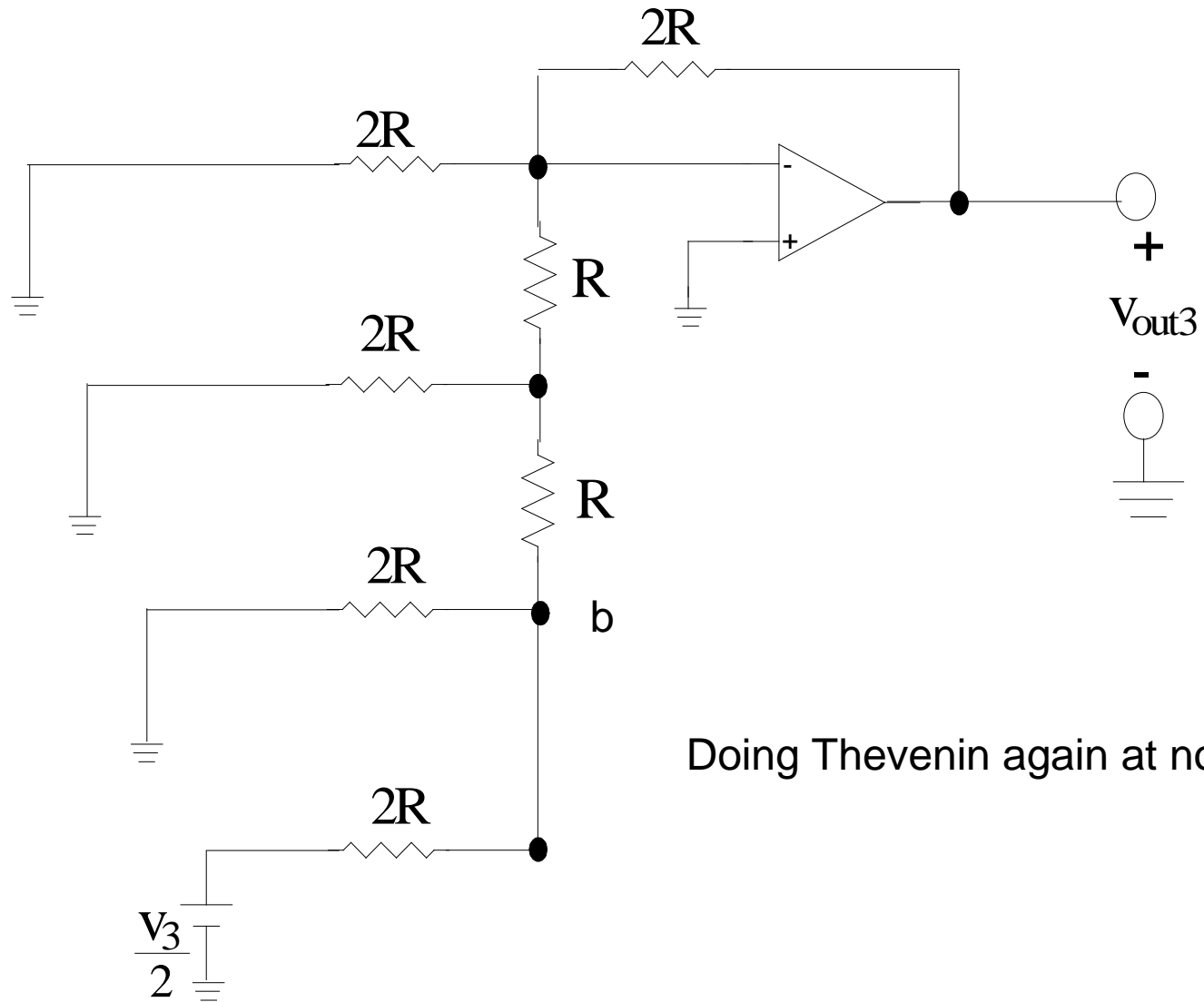


Doing Thevenin again at node 'b'


Gives:

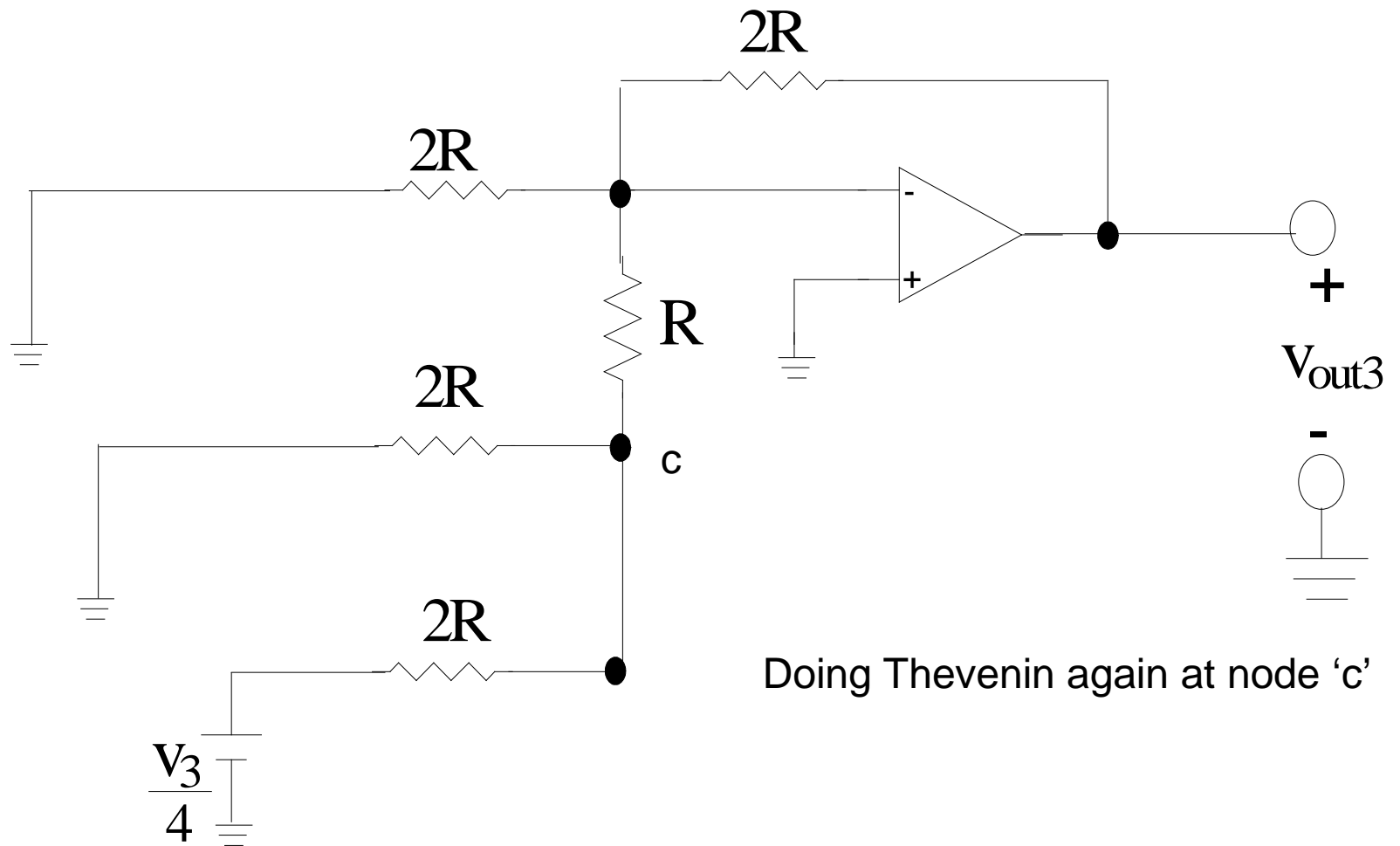

Gives:

 

Redrawing:

 

Now writing an expression for  $v_{out}$

In terms of  $v_3$  using the virtual ground and noting

No current will flow in the resistor to  $v_0$ 's

Suppressed source ( $2R$ ) we get:

$$v_{out} = v_{out3} = -\frac{2R}{2R} \frac{v_3}{8} = -\frac{v_3}{8}$$

$v_3$  is either +5V or 0V

# Digital to Analog Converters

## R/2R ladder D/A

Summing all the contributions we get:


$$v_{out} = v_{out0} + v_{out1} + v_{out2} + v_{out3}$$

$$v_{out} = -v_o - \frac{v_1}{2} - \frac{v_2}{4} - \frac{v_3}{8}$$


# Registers (see ECTE233)

- Registers can be considered to be groupings of flip flops/ bistables
- Each flip-flop in the register represents 1 bit
- When the flip flops state is changed this represents the storing of a bit (either its reset (0) or set(1))
- Thus each flip flop in a register of flip flops stores the data (for example 8 bits needing 8 flip flops) for some 'short' period of time (till the next Set or Reset command is received from another 'write' command)
- Of course using a lot of flip-flops would be wasteful, so registers and counters are available with the flip flops built in
- We should note that a **flip flop** on its own is an **asynchronous device** ie we do not know when the Set / Reset inputs will occur in time
- A system where we know when a state change is possible for a circuit element is known as a synchronous system and typically has a 'clocked' or periodic pulsed input

# Counters (see ECTE233)

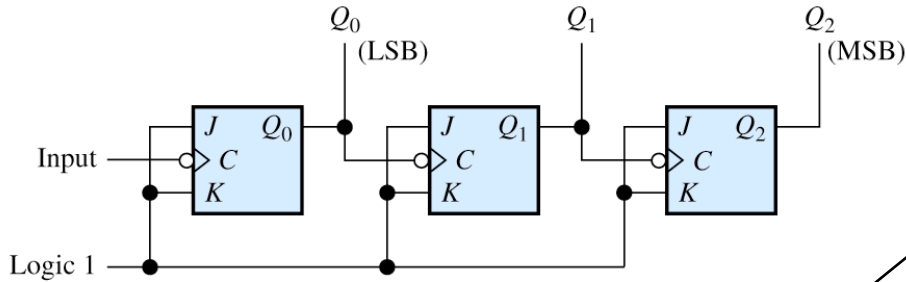

 Cousin of shift register as now  
We are counting clocked pulses  
On falling edge of clock!



Roll's over back to  
'000'

Ripple counter.




# Sampling Theorem

If a signal contains no components with frequencies higher than  $f_H$ , all of the information contained in the signal is present in its samples, provided that the sampling rate is selected to be more than twice  $f_H$ .

$$f_S \geq 2f_H$$
 
# **ANALOG-TO-DIGITAL CONVERSION**

Analog-to-digital conversion is a two-step process. First, the signal is sampled at uniformly spaced points in time. Second, the sample values are quantised so they can be represented by words of finite length, for example 8 bits.



When a 7-kHz sinusoid is sampled at 10 kHz, the sample values appear to be those of a 3-kHz sinusoid.

As a result before we sample any waveform  
We should ensure that the frequencies  
At the analog input are at most half frequency  
At which the signal is to be sampled!


We most often do this by using a Low Pass  
Filter as an **anti-aliasing filter**, ie we  
Filter out or attenuate all frequencies above  
Half the sampling frequency:



# ANALOG-TO-DIGITAL CONVERSION


- The analogue to digital converter (A/D converter or ADC) samples an analog signal to produce a digital output code
- Due to the process there is a significant delay between sampling the analog input signal and presentation of the resultant digital output code
- Often these are built into IC's
- A Common form for the ADC is the successive approx. device

# ANALOG-TO-DIGITAL CONVERSION

 


- Works by comparison of the analog input with the output of the Digital to Analog converter

# ANALOG-TO-DIGITAL CONVERSION

 

- The control unit has three inputs, a start command, the output of the comparator and a clock input
- It contains logic which is triggered by the start command (possibly a state machine with flip flops for memory of state)


# ANALOG-TO-DIGITAL CONVERSION

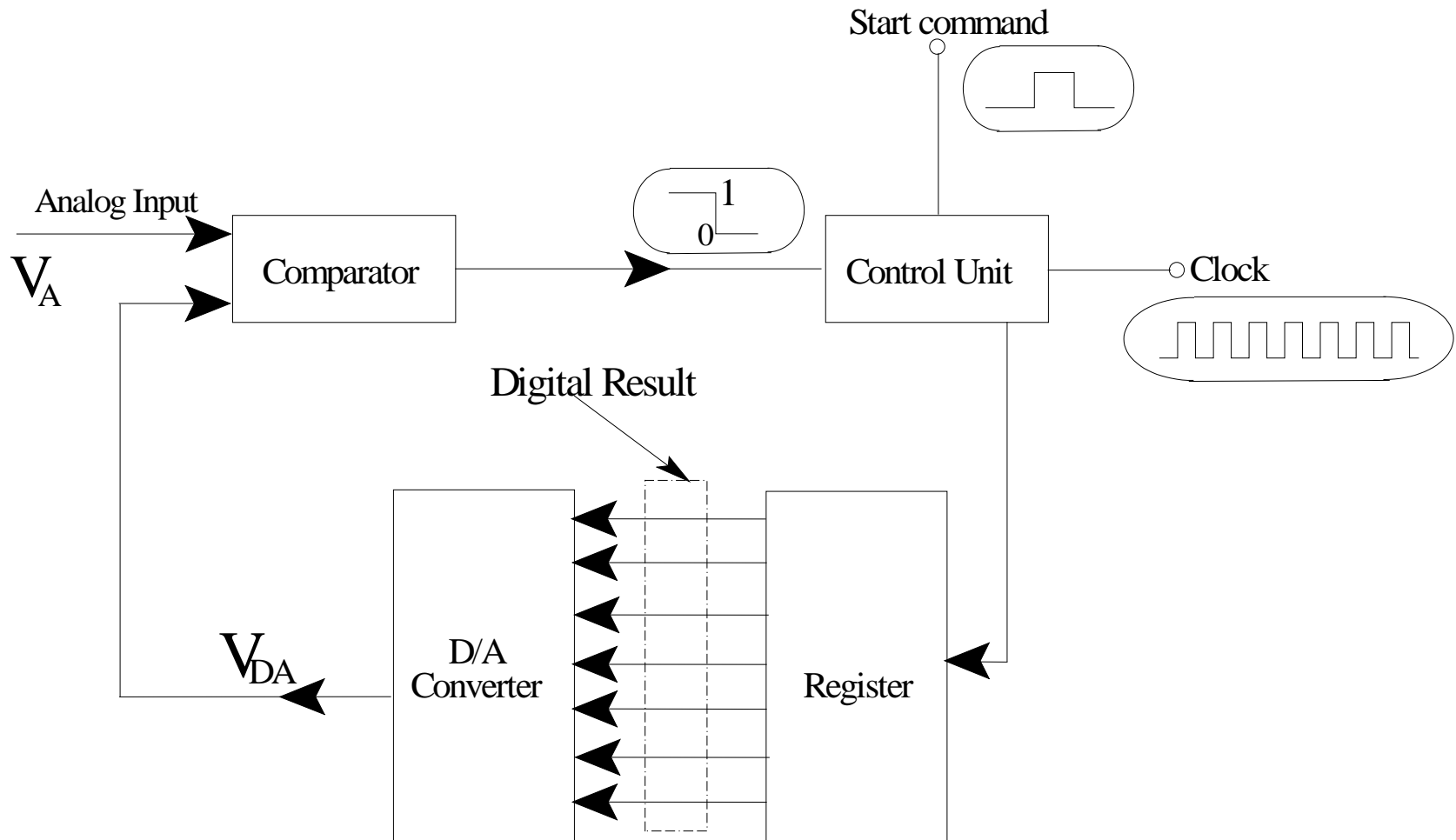

- The clock input determines the rate at which data is sent to the register which holds a binary number that is then both converted to an analog signal and used as the result when the comparator output indicates the process is complete



# ANALOG-TO-DIGITAL CONVERSION

 

For the comparator we can identify the following:

If  $V_{DA} < V_A$  the comparator output is HIGH


If  $V_{DA} = V_A$  the comparator output is LOW

If  $V_{DA} > V_A$  the comparator output is LOW



If the comparator output is LOW then the comparator Stops the process of modifying the binary number stored in the register!

# ANALOG-TO-DIGITAL CONVERSION

 

For the comparator we can identify the following:

If  $V_{DA} < V_A$  the comparator output is HIGH


If  $V_{DA} = V_A$  the comparator output is LOW

If  $V_{DA} > V_A$  the comparator output is LOW



If the comparator output is LOW then most likely the value in the Register is close to the analog Input value  $V_A$

# ANALOG-TO-DIGITAL CONVERSION

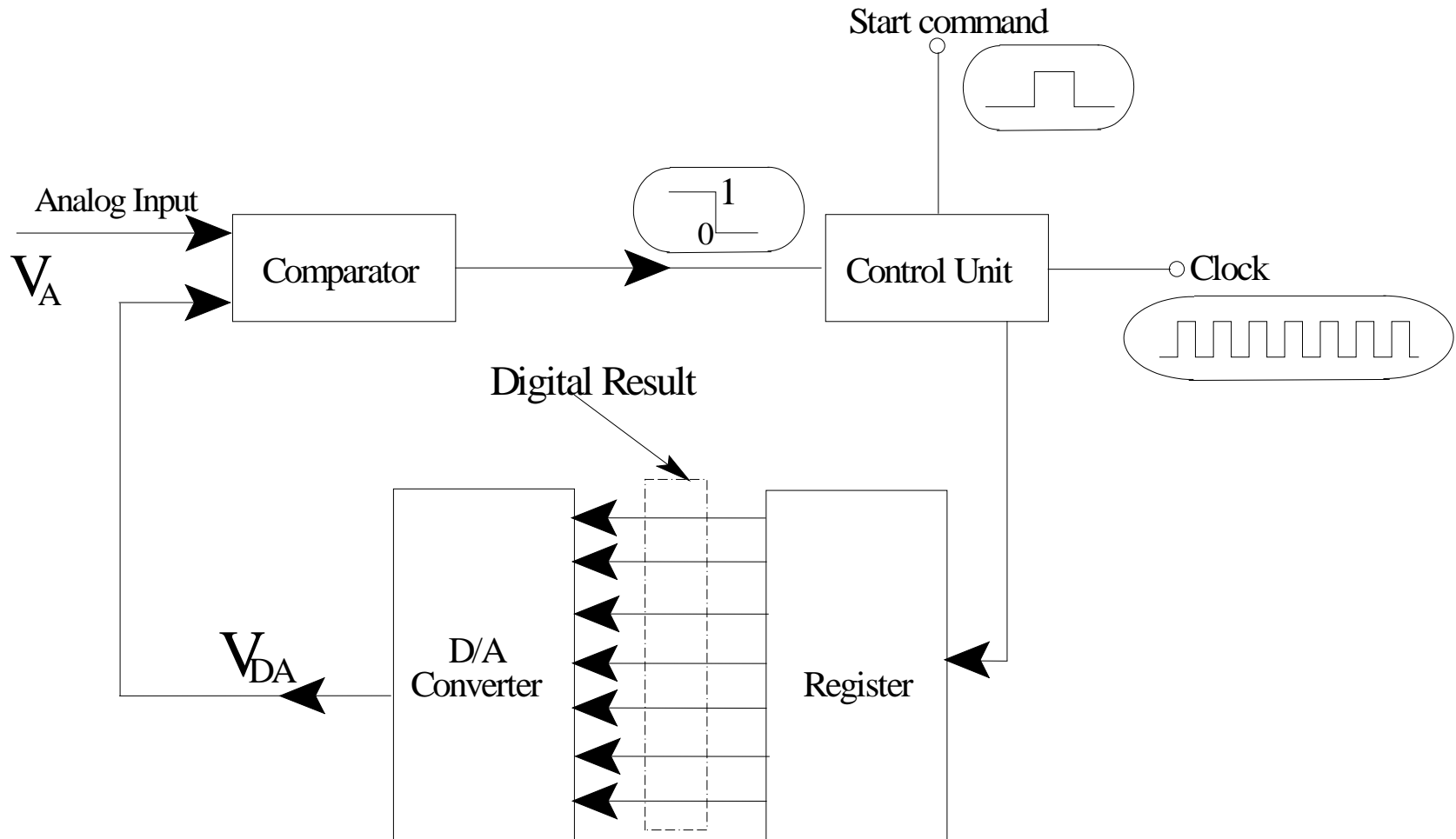

For the comparator we can identify the following:

If  $V_{DA} < V_A$  the comparator output is HIGH

If  $V_{DA} = V_A$  the comparator output is LOW


If  $V_{DA} > V_A$  the comparator output is LOW



If the comparator output is HIGH then the process of modifying the binary number stored in the Register continues

 
# Simple Comparator

- We can implement the comparator using an op-amp in its high gain differential mode
- High gain is important since we want to obtain the required output from the smallest possible input difference




 
# Simple Comparator

- For the circuit shown we would have an output of either +10 or -10 Volts for large gain  $A$  (in ideal case this is INFINITE!)
- This amplifies (in open loop) the difference between the two inputs (see week 10 lecture)
- When the difference between  $V_1$  and  $V_2$  is so small that the output lies between the two voltage rails we say that it is below the 'threshold voltage' ie the voltage where the output 'saturates' to the applied rail voltage



  
# Simple Comparator

- If the difference between  $V_1$  and  $V_2$  is less than the value of the threshold voltage then the output is equal to the open loop gain  $A$  times the difference between the input voltages
- Assuming  $A=10000$  we can draw the  $v_{out}$  vs  $V_1 - V_2$  characteristic:


 
# Simple Comparator: Example


A comparator has the output/input characteristic:



Determine:

- The threshold voltage
- The output voltage for  $V_1=7.5750\text{ V}$  and  $V_2=7.5745\text{ V}$
- The output voltage for  $V_1=6.550\text{ V}$  and  $V_2=6.600\text{ V}$

# Simple Comparator: Answer

 

a) The Threshold voltage is  $1\text{ mV}$  since  $V_{out}$  saturates at  $10\text{ V}$  when  $V_1 - V_2 \geq 1\text{ mV}$

b) Here

$V_1 - V_2 = 7.5750 - 7.5745 = 0.5\text{ mV}$  which is less than the threshold voltage, thus:

$$V_{out} = A(V_1 - V_2) = +5\text{ V}$$

c) Here


$V_1 - V_2 = 6.550 - 6.600 = -50\text{ mV}$  which is greater than the threshold voltage, thus:  $V_{out} = -10\text{ V}$



# Digital Ramp A/D Converter

- Based on Successive Approximate ADC but uses a counter instead of a Register
- Its output characteristic looks like a ramp
- Here we assume that the start pulse will also reset the counter
- An AND gate is used which will have three inputs, one from the start pulse ensures that the counter starts at zero and no false clock signals affect the counter while its being reset (to all zero count)
- The other input for the AND gate is the output of the comparator after the voltage has been changed to 0 to 5 Volt level by an interfacing circuit (using either a transistor or a Diode and Zener Diode with a voltage buffer as we will see in the EWB simulation)


# Digital Ramp A/D Converter

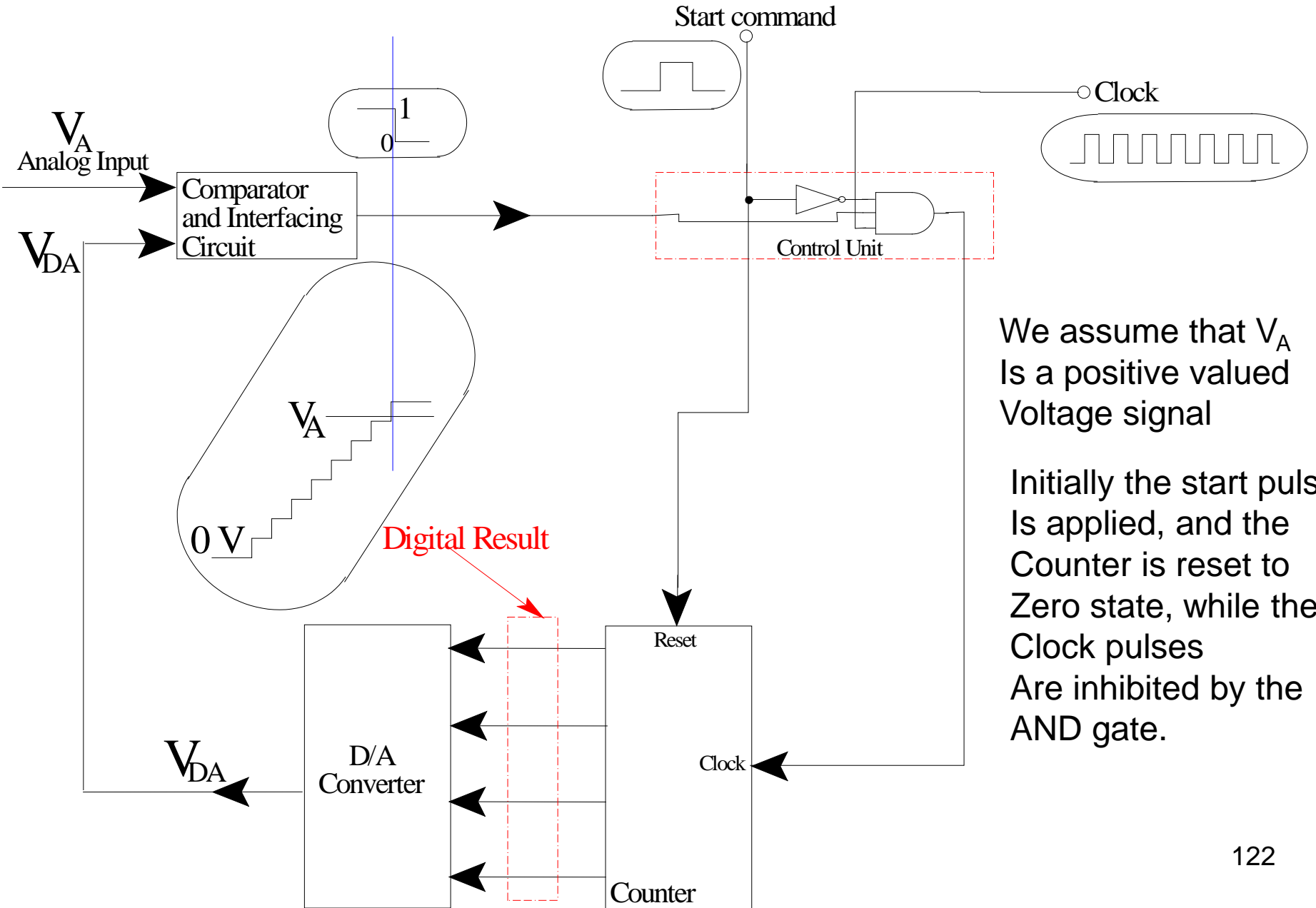


We assume that  $V_A$  Is a positive valued Voltage signal

Initially the start pulse Is applied, and the Counter is reset to Zero state, while the Clock pulses Are inhibited by the AND gate.


# Digital Ramp A/D Converter

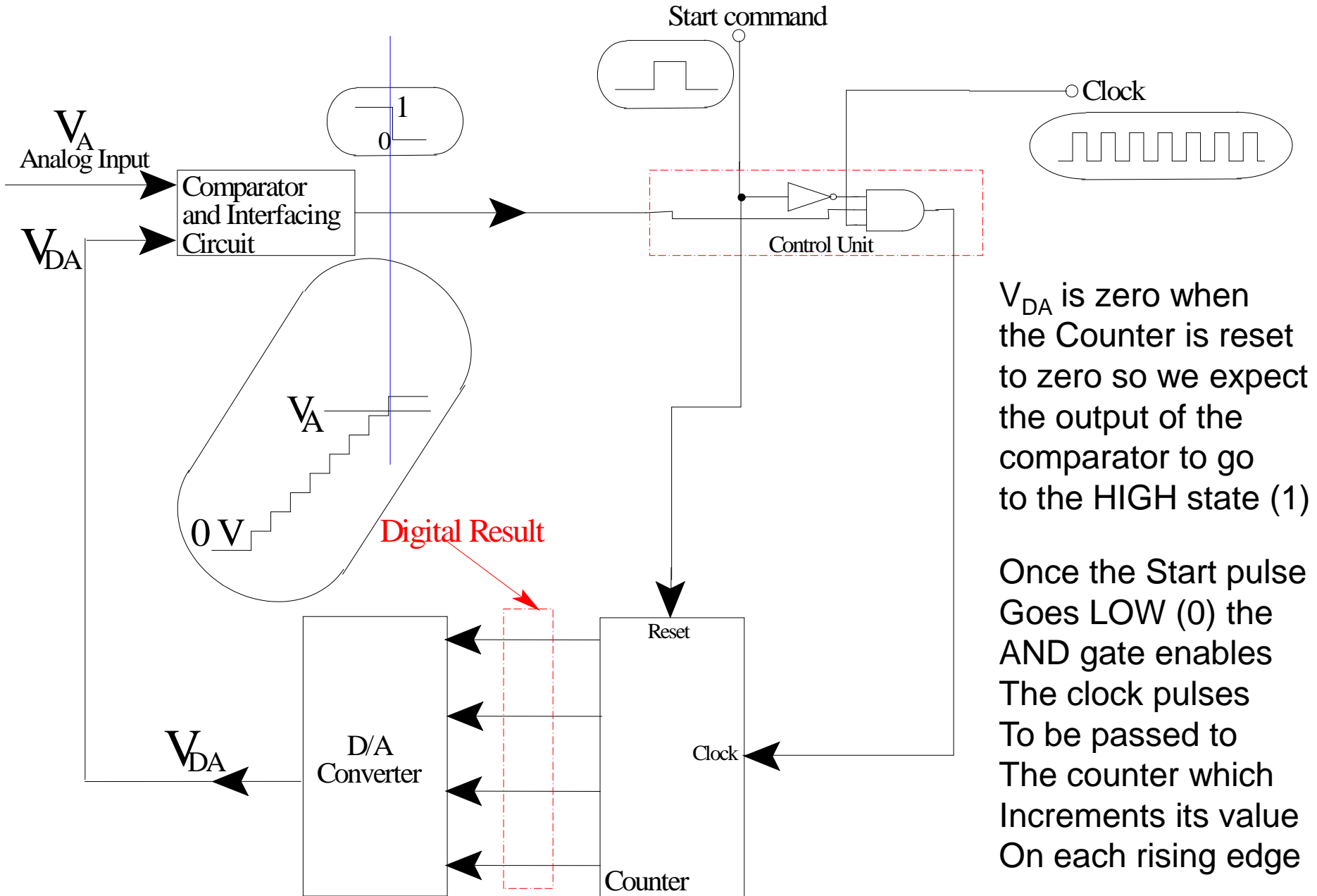

# Digital Ramp A/D Converter

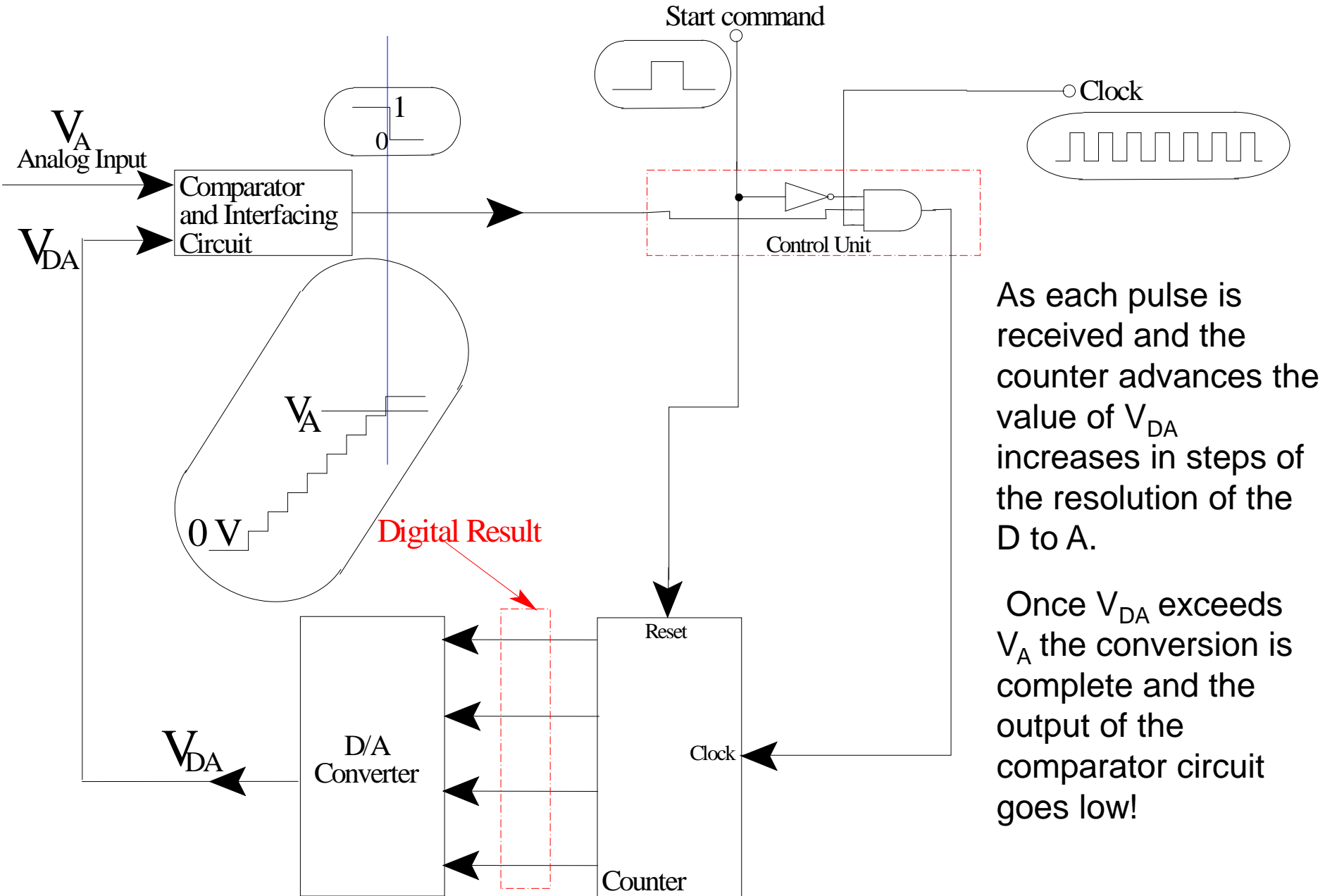

# Digital Ramp A/D Converter

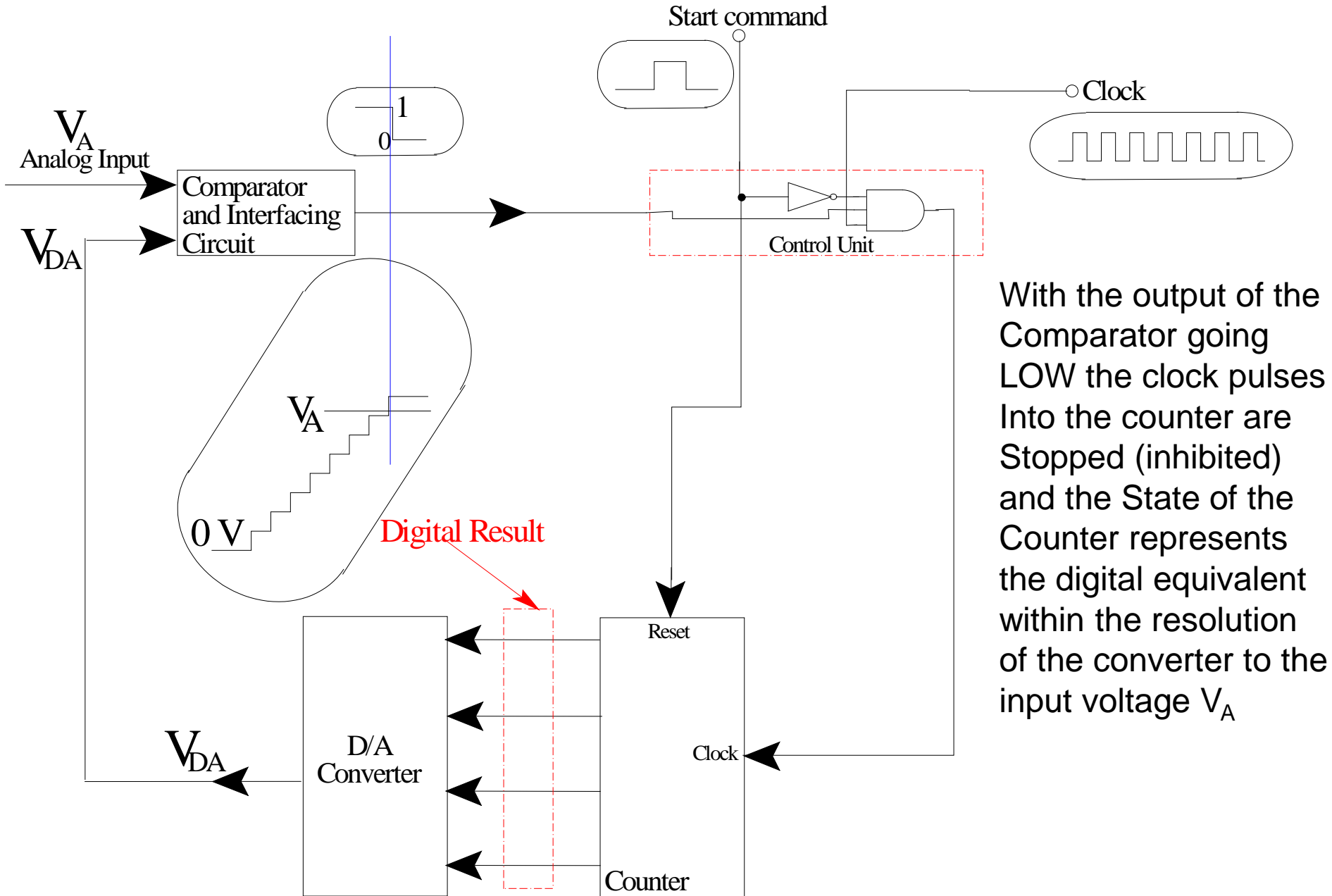

With the output of the Comparator going LOW the clock pulses Into the counter are Stopped (inhibited) and the State of the Counter represents the digital equivalent within the resolution of the converter to the input voltage  $V_A$

# Simulation: Digital Ramp A/D converter

- We have an EWB simulation to demonstrate!
- Name: \ewb5\comparatorforadcc.ewb
- 'R' resets the counter
- 'Space Bar' switches between 5V and 3V signal for  $V_A$

# Example

An A/D converter has a clock frequency of 100 kHz. The full scale output of the D/A is 8.255 Volts with a 8-bit input. The comparator threshold voltage is 1mV. If  $V_A=4.528$  Volts determine:

- a) The digital number obtained from the counter
- b) The conversion time
- c) The converter resolution

# Answer

a) The digital number obtained from the counter

We have an 8-bit input thus total possible steps is:

$$2^{n-1} - 1 = 2^{8-1} - 1 = 128 - 1 = 127$$

With the full scale voltage being 8.255 volts then step size

Is given by:

$$\frac{\text{full scale voltage}}{\text{number of steps}} = \frac{8255}{127} = 65 \text{ mV}$$

Given  $V_A = 4.528 \text{ V}$  and that the threshold voltage is 1mV then  $V_{DA}$  must be 4.529 V or more before a comparator change in state is possible, which means that the voltage will need to rise to the largest nearest multiple of 65mV which is 4550 mV and then the number of steps needed is:

$$\frac{4550}{65} = 70 \text{ steps}$$



# Answer

a) The digital number obtained from the counter

Hence the digital number at the output of the A/D will be 70  
or in 8 bit binary 01000110

b) The conversion time

We have a clock frequency of 100kHz or 10μsec between pulses, so the time taken is simply 70 times 10 μsec or 700 μsecs, the maximum time is the maximum count, which here Would be 127 times 10μsec or 1.27ms

c) The converter resolution

We find resolution from the step size of the D/A which here is 65mV. This can also be expressed as a percentage:

$$\frac{65}{8255} \times 100 = 0.79\%$$

Errors due to resolution have a  
Special name → Quantisation error!